

# CS 31: Introduction to Computer Systems

## 06: Computer Architecture

02-06-2025



# Reading Quiz

- Note the red border!
- 1 minute per question
- No talking, no laptops, phones during the quiz

## Check your frequency:

- Iclicker2: frequency AA
- Iclicker+: green light next to selection

For new devices this should be okay,  
For used you may need to reset frequency

## Reset:

1. hold down power button until blue light flashes (2secs)
2. Press the frequency code: AA  
vote status light will indicate success

# What we will learn this week

## 1. Introduction to C

- Data organization and strings
- Functions

## 2. Computer Architecture

- Machine memory models
- Digital signals
- Logic gates

# Functions: Specifying Types

Need to specify the **return type** of the function, and the **type of each parameter**:


```
<return type> <func name> ( <param list> ) {  
    // declare local variables first  
    // then function statements  
    return <expression>;  
}  
  
// my_function takes 2 int values and returns an int  
int my_function(int x, int y) {  
    int result;  
    result = x;  
    if(y > x) {  
        result = y+5;  
    }  
    return result*2;  
}
```

Compiler will yell at you if you try to pass the wrong type!

# Passing Arrays

- An array argument's value is its base address

```
int main(void){  
    int values[10];  
    foo(values, 10);  
}  
void foo(int arr[], int n){  
    arr[2] = 6;  
}
```




# Function Arguments

- Arguments are **passed by value**
  - The function gets a separate copy of the passed variable

```
int func(int a, int b) {  
    a = a + 5;  
    return a - b;  
}
```
 
```
int main(void) {  
    → int x, y; // declare two integers  
    x = 4;  
    y = 7;  
    y = func(x, y);  
    printf(“%d, %d”, x, y);  
}
```




# Function Arguments

- Arguments are **passed by value**
  - The function gets a separate copy of the passed variable

```
int func(int a, int b) {  
    a = a + 5;  
    return a - b;  
}
```

```
int main(void) {  
    int x, y; // declare two integers  
    x = 4;  
    y = 7;  
    y = func(x, y);  
    printf(“%d, %d”, x, y);  
}
```

 It doesn't matter what func does with a and b. The value of x in main doesn't change.




# Passing Arrays

- An array argument's value is its base address

```
int main(void){  
    int values[10];  
    foo(values, 10);  
}  
void foo(int arr[], int n){  
    arr[2] = 6;  
}
```

array base address

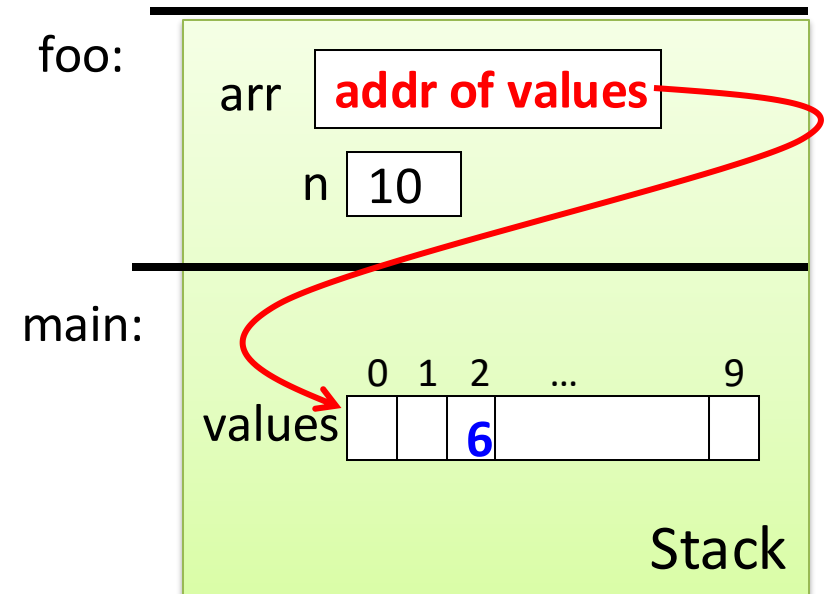



# Function Arguments

- Arguments can be pointers!
  - The function gets the address of the passed variable!

```
void func(int *a) {  
    *a = *a + 5;  
}
```

```
int main(void) {  
    int x = 4;  
  
    func(&x);  
    printf("%d", x);  
}
```

main:




Stack

# Function Arguments: passed by value

- Arguments are **passed by value**
  - The function gets a separate copy of the passed variable

It doesn't matter what func does with a and b. The value of x in main doesn't change.
 
```
int func(int a, int b) {  
    a = a + 5;  
    return a - b;  
}  
  
int main(void) {  
    → int x, y; // declare two integers  
    x = 4;  
    y = 7;  
    y = func(x, y);  
    printf("%d, %d", x, y);  
}
```



# Function Arguments: passed by memory address


- Arguments are **passed by memory address**
  - The function gets the address of the passed variable

```
int func(?, ?)
{
    //computations adding 4 to x
    return //x-y ;
}
```

```
int main(void) {
    int x, y, z;
    x = 4;
    y = 7;
    z = func(&x, &y);
    printf(“%d, %d”, x, y);
}
```

what data type are a and b?  
they can't be integers. Recall  
we have passed in a memory  
address in the function call.

main:

 

Stack


# Function Arguments: passed by memory address

- Arguments are **passed by memory address**
  - The function gets the address of the passed variable

```
int func(<memory addresss of int> a, <memory addresss of int> b) {  
    //computations adding 4 to x  
    return //x-y ;  
}
```

```
int main(void) {  
    int x, y, z; // declare three integers  
    x = 4;  
    y = 7;  
    z = func(&x, &y);  
    printf(“%d, %d”, x, y);  
}
```

 what data type are a and b?  
they can't be an integers.  
they are type **memory addresses of an int**




Stack

# Function Arguments: passed by memory address

- Arguments are **passed by memory address**
  - The function gets the address of the passed variable

```
int func(<memory address of int> a, <memory address of int> b) {  
    //computations adding 4 to x  
    return //x-y ;  
}
```
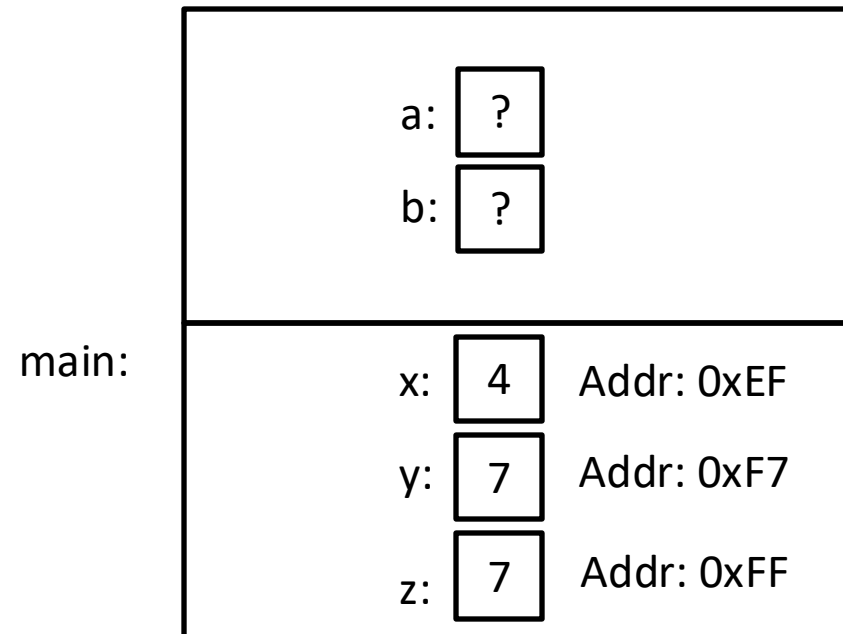
```
int main(void) {  
    int x, y, z; // declare three integers  
    x = 4;  
    y = 7;  
    z = func(&x, &y);  
    printf(“%d, %d”, x, y);  
}
```



Stack


# Function Arguments: passed by memory address

- Arguments are **passed by memory address**
  - The function gets the address of the passed variable

In func, we want to add 4 to x. How do we do that?

```
int func(<memory address of int> a, <memory address of int> b) {  
    //computations adding 4 to x  
    return //x-y ;  
}
```
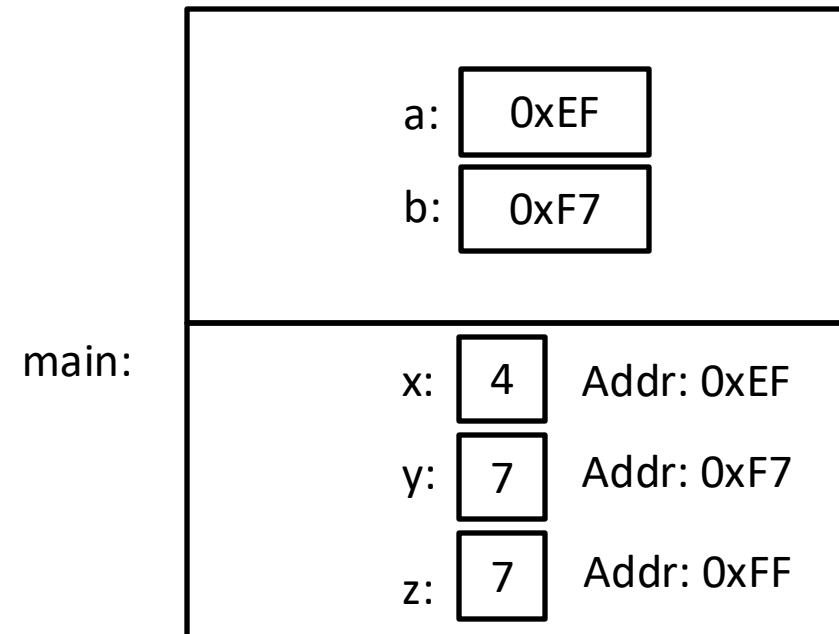
```
int main(void) {  
    int x, y, z; // declare three integers  
    x = 4;  
    y = 7;  
    z = func(&x, &y);  
    printf(“%d, %d”, x, y);  
}
```



Stack


# Function Arguments: passed by memory address

- Arguments are **passed by memory address**
  - The function gets the address of the passed variable

We need the value at the memory address of a.

```
int func(<memory address of int> a, <memory address of int> b) {  
    //computations adding 4 to x  
    return //x-y ;  
}
```
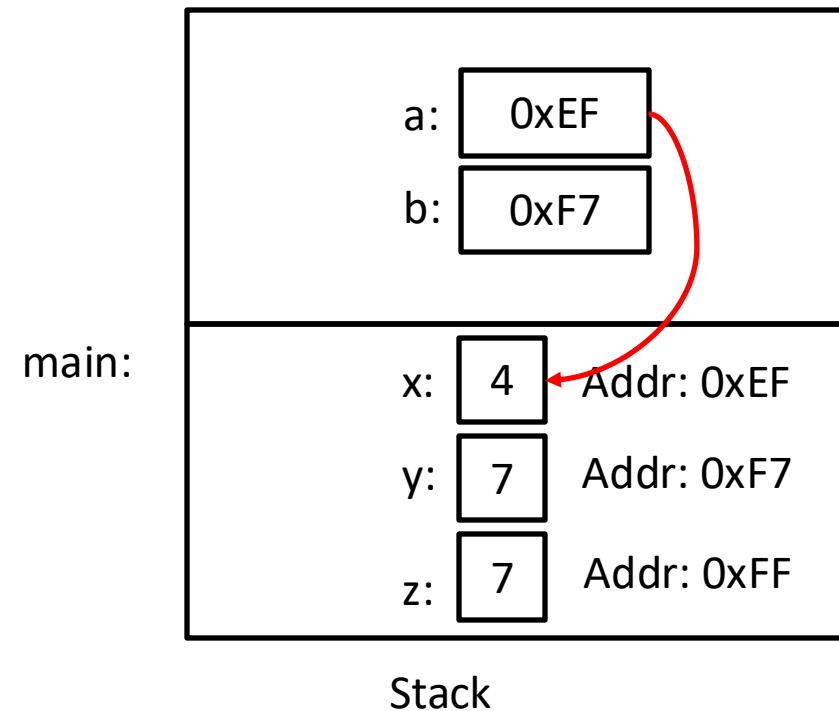
```
int main(void) {  
    int x, y, z; // declare three integers  
    x = 4;  
    y = 7;  
    z = func(&x, &y);  
    printf(“%d, %d”, x, y);  
}
```




# Function Arguments: passed by memory address

- Arguments are **passed by memory address**
  - The function gets the address of the passed variable

We need the value at the memory address of a and the value at the memory address of b

```
int func(<memory address of int> a, <memory address of int> b) {  
    <value at addr a> += 5;  
    return <value at addr a> - <value at addr b>  
}
```

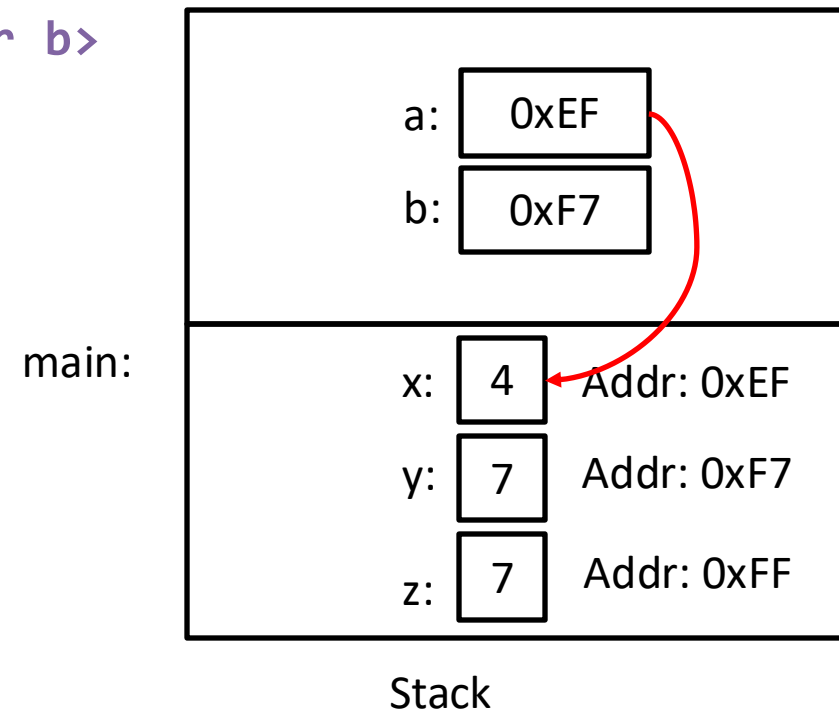
```
int main(void) {  
    int x, y, z; // declare three integers  
    x = 4;  
    y = 7;  
    z = func(&x, &y);  
    printf(“%d, %d”, x, y);  
}
```






# Hardware Models (1940's)

- Harvard Architecture:

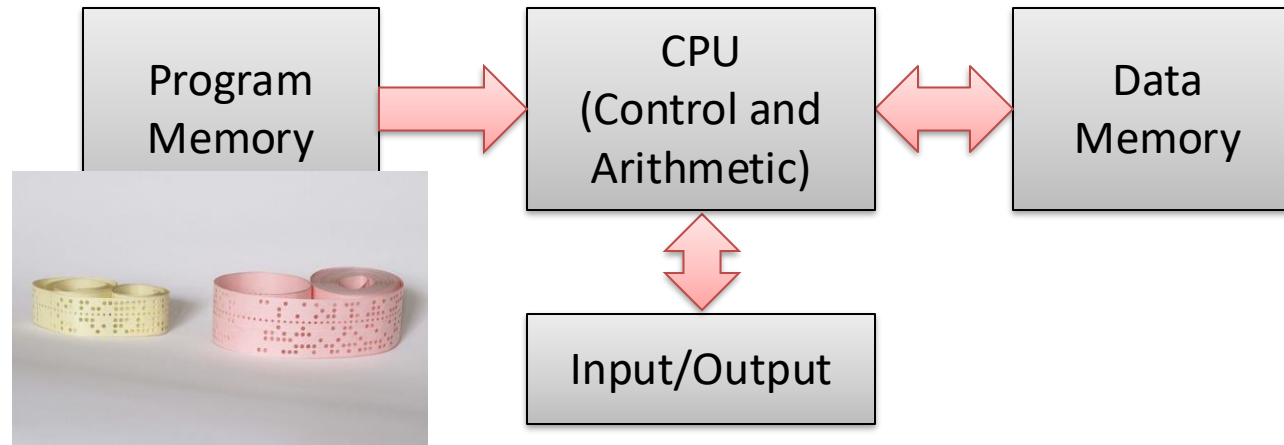

- Von Neumann Architecture:

 

# Von Neumann Architecture 1945

Computer is a generic computing machine

- Can be used to compute anything that is computable
- Based on Alan Turing's Universal Turing Machine


Uses a stored program model

- both program & data loaded into computer memory
- No distinction between data & instructions in memory
  - Earlier computers used fixed program encoded on machine, data loaded and run by fixed program

*All modern computers based on the Von Neumann model*
 
# Von Neumann Model

5 units **connected** by buses (wires) to communicate



## Processing & Control Units:

- implement CPU \execute program instructions on program data

**Memory:** stores program instructions and data


- memory is addressable: addr 0, 1, 2, ...

**Input, Output:** interface to compute

- trigger actions: load program, initiate execution, ...
- display/store results: to terminal, save to disk, ...
 
# Our Goal: Build a CPU (model)


Start with very simple functionality, and add complexity


 
# Logic Gates

**Input:** Boolean value(s) (high and low voltages for 1 and 0)



**Output:** Boolean value result of Boolean function  
Always present, but may change when input changes



A	B	A & B	A   B	~A
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0
  
# More Logic Gates

Note the circle on the output. This circle means bitwise “not” (flip bits).




A	B
0	0
0	1
1	0
1	1

A	NAND	B
0	1	
0	1	
1	1	
1	0	

A	NOR	B
0	1	
0	0	
1	0	
1	0	





 
# Combinational Logic Circuits

- Build up higher level processor functionality from basic gates



- Outputs are boolean functions of inputs
- Outputs continuously respond to changes to inputs

# What does this circuit output?

 
 
 
 
 


Clicker Choices

X	Y	Out <sub>A</sub>	Out <sub>B</sub>	Out <sub>C</sub>	Out <sub>D</sub>	Out <sub>E</sub>
0	0	0	1	0	1	0
0	1	0	1	0	0	1
1	0	1	0	1	1	1
1	1	0	0	1	1	0



# What does this circuit output?

     

Clicker Choices

X	Y	Out <sub>A</sub>	Out <sub>B</sub>	Out <sub>C</sub>	Out <sub>D</sub>	Out <sub>E</sub>
0	0	0	1	0	1	0
0	1	0	1	0	0	1
1	0	1	0	1	1	1
1	1	0	0	1	1	0

## Building more interesting circuits...

- Build-up XOR from basic gates (AND, OR, NOT)

A	B	$A \wedge B$
0	0	0
0	1	1
1	0	1
1	1	0

- Q: When is  $A \wedge B == 1$ ?




## Building more interesting circuits...

- Build-up XOR from basic gates (AND, OR, NOT)

A	B	$A \wedge B$
0	0	0
0	1	1
1	0	1
1	1	0

- Q: When is  $A \wedge B == 1$ ?

# Which of these is an XOR circuit?

 
 
 


General strategy:

1. Determine truth table (given inputs)
2. Find rows with output = 1
  - express these in terms of input values A, B combined with AND, NOT
  - then, combine each row expression with OR
3. Translate expression to a circuit

A	B	$A \wedge B$
0	0	0
0	1	1
1	0	1
1	1	0

# Which of these is an XOR circuit?

 
 
 


Draw an XOR circuit using AND, OR, and NOT gates.

I'll show you the clicker options after you've had some time.

A	B	$A \wedge B$
0	0	0
0	1	1
1	0	1
1	1	0

# Which of these is an XOR circuit?

   

General strategy:





1. Determine truth table (given inputs)
2. Find rows with output = 1
  - express these in terms of input values A, B combined with AND, NOT
  - then, combine each row expression with OR
3. Translate expression to a circuit

A	B	A ^ B
0	0	0
0	1	1
1	0	1
1	1	0

Use  $A \wedge B == (\sim A \ \& \ B) \ | \ (A \ \& \ \sim B)$

# Which of these is an XOR circuit?





$$\text{Use } A \wedge B == (\sim A \ \& \ B) \ | \ (A \ \& \ \sim B)$$

    

E: None of these are XOR.
    
# Which of these is an XOR circuit?

$$\text{Use } A \wedge B == (\sim A \ \& \ B) \mid (A \ \& \ \sim B)$$




E: None of these are XOR.



# XOR Circuit: Abstraction

$$A \oplus B == (\sim A \ \& \ B) \ | \ (A \ \& \ \sim B)$$

 

A:0 B:0 A^B:


A:0 B:1 A^B:

A:1 B:0 A^B:

A:1 B:1 A^B:

# XOR Circuit: Abstraction!

$$A \wedge B == (\sim A \ \& \ B) \ | \ (A \ \& \ \sim B)$$

 

Treat XOR Circuit as a building block for other circuits!


# Abstraction!

- Hide away the complex internals of how the system functions, and focus on what functionality we expect. I.e., the guaranteed output of a system given the set of allowed inputs, and treating the functionality of the system as a black box.
- What are examples of abstractions you have experienced in daily life?

# Recall Goal: Build a CPU (model)

## Three main classifications of hardware circuits:

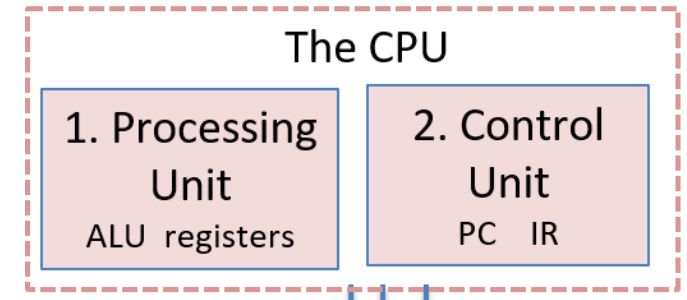1. ALU: implement arithmetic & logic functionality
  - Example: adder circuit to add two values together
2. Storage: to store binary values
  - Example: set of CPU registers (“register file”) to store temporary values
3. Control: support/coordinate instruction execution
  - Example: circuitry to fetch the next instruction from memory and decode it




# Recall Goal: Build a CPU (model)

Three main classifications of hardware circuits:

1. **ALU: implement arithmetic & logic functionality**
  - Example: adder circuit to add two values together

Start with ALU components (e.g., adder circuit, bitwise operator circuits)


Combine component circuits into ALU!

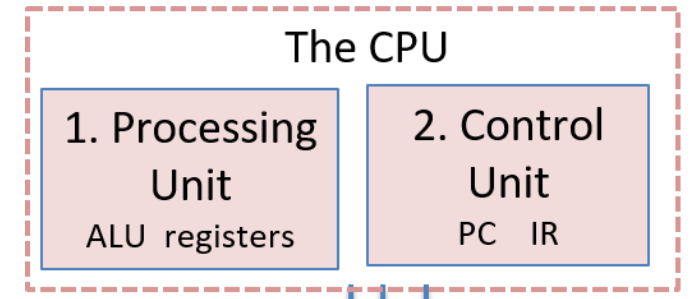

# Digital Circuits - Building a CPU

Start with building an ALU:

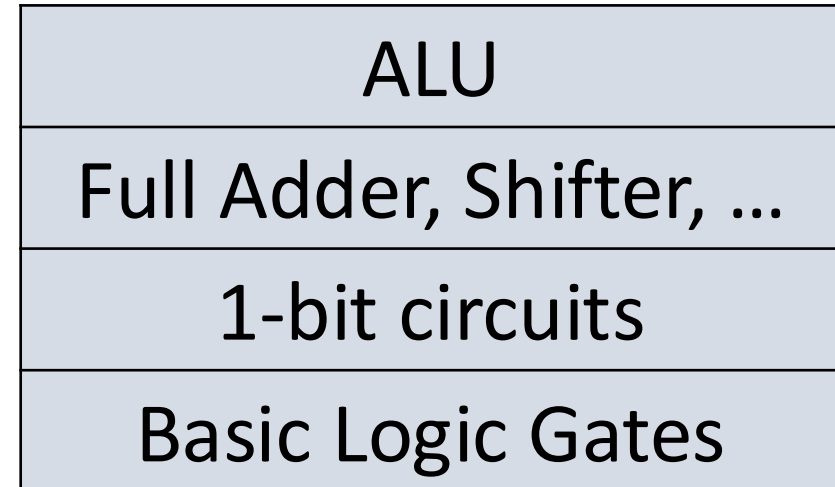1. Individual components from basic logic gates  
Adder, Subtractor, Bit shifter, Bit-wise OR, ...
2. Combine them together into ALU!



# Arithmetic Circuits

- 1 bit adder:  $A+B$

- Two outputs:

1. Obvious one: the sum

2. Other one: ??

A	B	Sum (A + B)	$C_{out}$
0	0		
0	1		
1	0		
1	1		

# Arithmetic Circuits

- 1 bit adder:  $A+B$

- Two outputs:

1. Obvious one: the sum





2. Other one: ??

A	B	Sum (A + B)	$C_{out}$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



# Which of these circuits is a one-bit adder?



A	B	Sum (A + B)	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 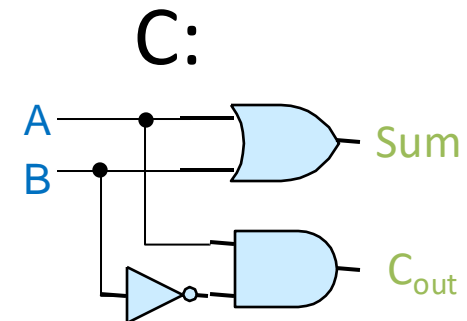  



A	B	Sum (A + B)	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# Which of these circuits is a one-bit adder?

A	B	Sum (A + B)	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

  

A	B	Sum (A + B)	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

  

## More than one bit addition?

- When adding, sometimes have *carry in* too

$$\begin{array}{r} 0011010 \\ + \underline{0001111} \\ \hline \end{array}$$

## More than one bit?

- When adding, sometimes have *carry in* too

$$\begin{array}{r} 1111 \\ 0011010 \\ + \underline{0001111} \end{array}$$

Write Boolean expressions for

$$\text{Sum} = 1 \text{ and } C_{\text{out}} = 1$$

When is Sum 1?

When is  $C_{\text{out}}$  1?

A	B	$C_{\text{in}}$	Sum	$C_{\text{out}}$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Write Boolean expressions for

Sum = 1 and  $C_{out} = 1$

A	B	$C_{in}$	Sum	$C_{out}$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

When is Sum 1?

$$\sim C_{in} \ \& \ (A \wedge B) \ | \ C_{in} \ \& \ \sim (A \wedge B) \ == \ (C_{in} \ \wedge \ (A \wedge B))$$

When is  $C_{out}$  1?

Write Boolean expressions for

Sum = 1 and  $C_{out} = 1$

A	B	$C_{in}$	Sum	$C_{out}$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

When is Sum 1?

$$\sim C_{in} \ \& \ (A \wedge B) \ | \ C_{in} \ \& \ \sim (A \wedge B) \ == \ (C_{in} \ \wedge \ (A \wedge B))$$

When is  $C_{out}$  1?

$$(A \ \& \ B) \ | \ ((A \wedge B) \ \& \ C_{in})$$

Write Boolean expressions for

Sum = 1 and  $C_{out} = 1$


A	B	$C_{in}$	Sum	$C_{out}$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

When is Sum 1?

$$\sim C_{in} \ \& \ (A \wedge B) \ | \ C_{in} \ \& \ \sim (A \wedge B) \ == \ (C_{in} \ \wedge \ (A \wedge B))$$

When is  $C_{out}$  1?


$$(A \ \& \ B) \ | \ ((A \wedge B) \ \& \ C_{in})$$

 



 
# One-bit (full) adder


- Need to include:  
**carry-in** and **carry-out**




A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

 

# Multi-bit Adder (Ripple-carry Adder)

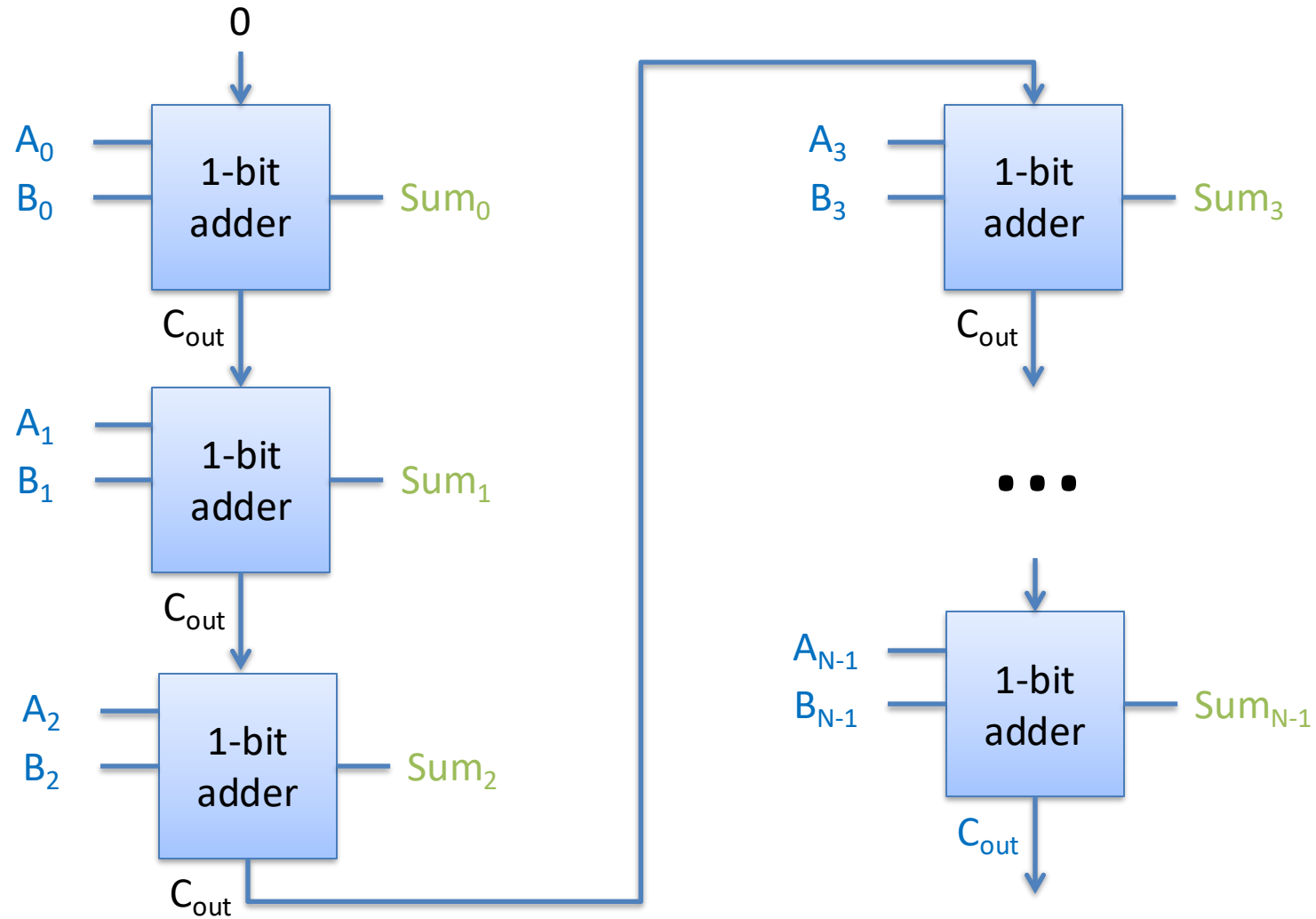

# Three-bit Adder (Ripple-carry Adder)

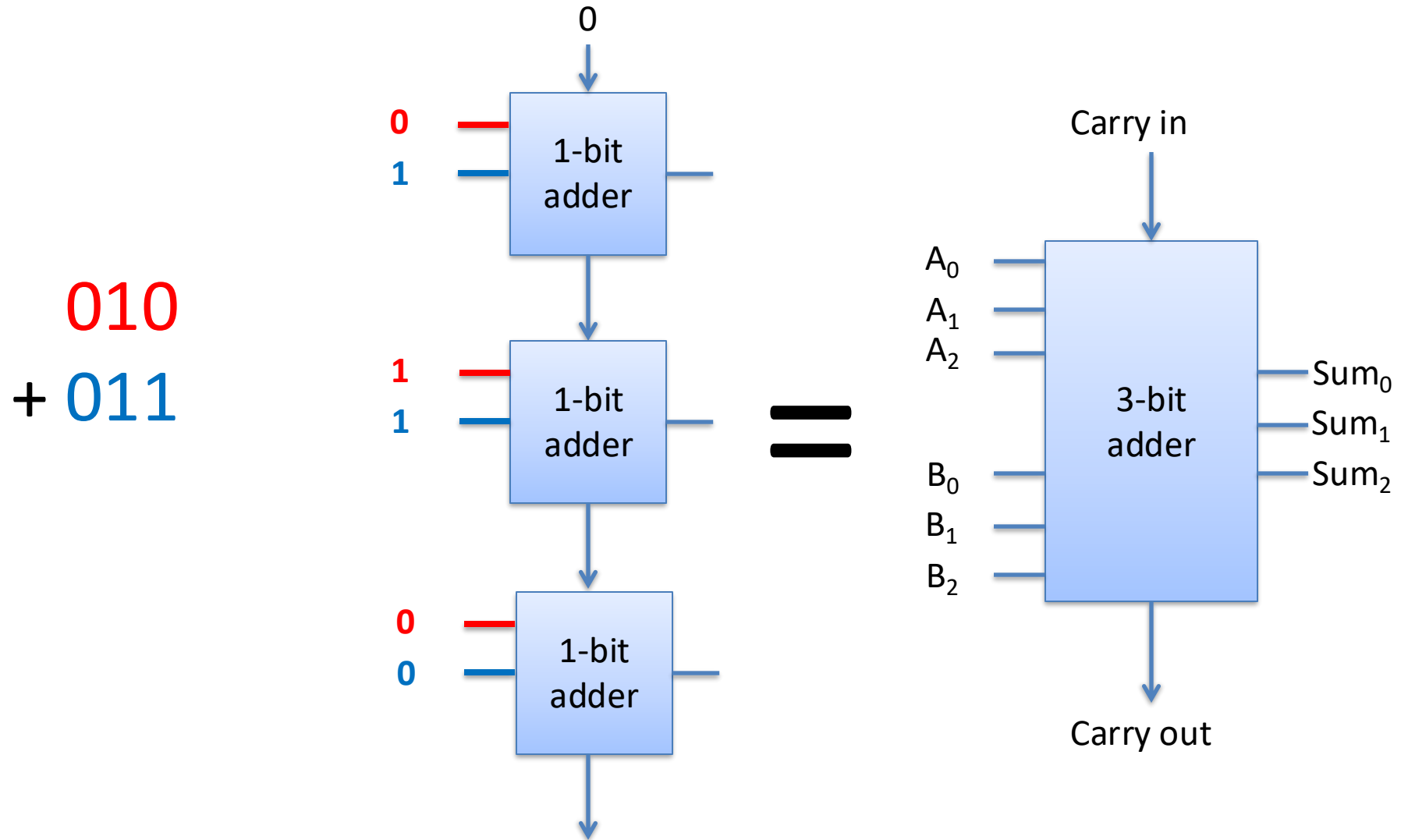

# Arithmetic Logic Unit (ALU)

- One component that knows how to manipulate bits in multiple ways
  - Addition
  - Subtraction
  - Multiplication / Division
  - Bitwise AND, OR, NOT, etc.
- Built by combining components
  - Take advantage of sharing HW when possible (e.g., subtraction using adder)

# Simple 3-bit ALU: Add and bitwise OR

3-bit inputs

A and B:

$A_0$

$A_1$

$A_2$

$B_0$


$B_1$

$B_2$

$Out_0$


$Out_1$

$Out_2$

 

# Simple 3-bit ALU: Add and bitwise OR


3-bit  
inputs  
A and B:

 




# Simple 3-bit ALU: Add and bitwise OR

Extra input: control signal to select Sum vs. OR

3-bit  
inputs  
A and B:



 


   Which of these circuits lets us select between two inputs?





  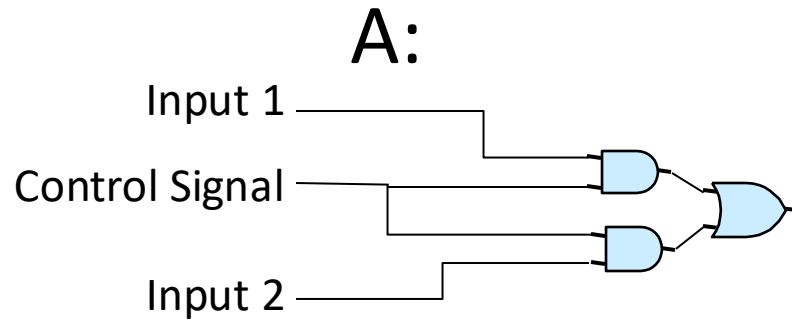
Which of these circuits lets us select between two inputs?


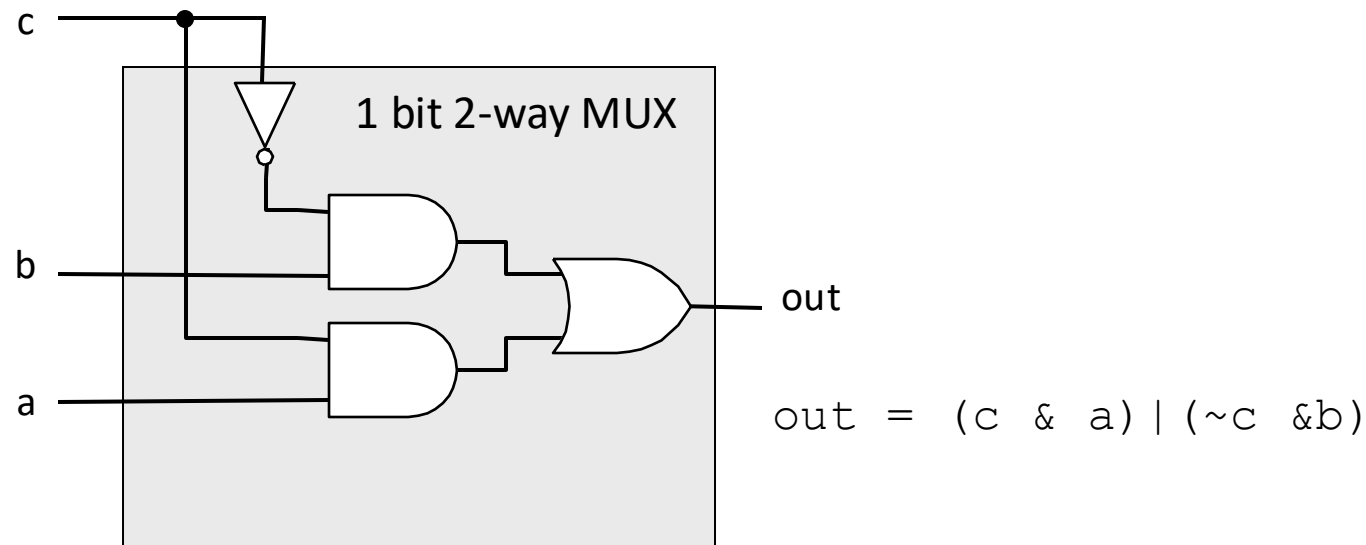
# Multiplexor: Chooses an input value

Inputs:  $2^N$  data inputs,  $N$  signal bits


Output: is one of the  $2^N$  input values




- Control signal  $c$ , chooses the input for output
  - When  $c$  is 1: choose  $a$ , when  $c$  is 0: choose  $b$
 
# N-Way Multiplexor

Choose one of N inputs, need  $\log_2 N$  select bits




$c_1$	$c_2$	Output
0	0	D0
0	1	D1
1	0	D2
1	1	D3

 

 
# Example 1-bit, 4-way MUX

- When select input is 2 (0b10): C chosen as output



=

 


S	Out
0	A
1	B
2	C
3	D

# Simple 3-bit ALU: Add and bitwise OR


3-bit inputs

A and B:

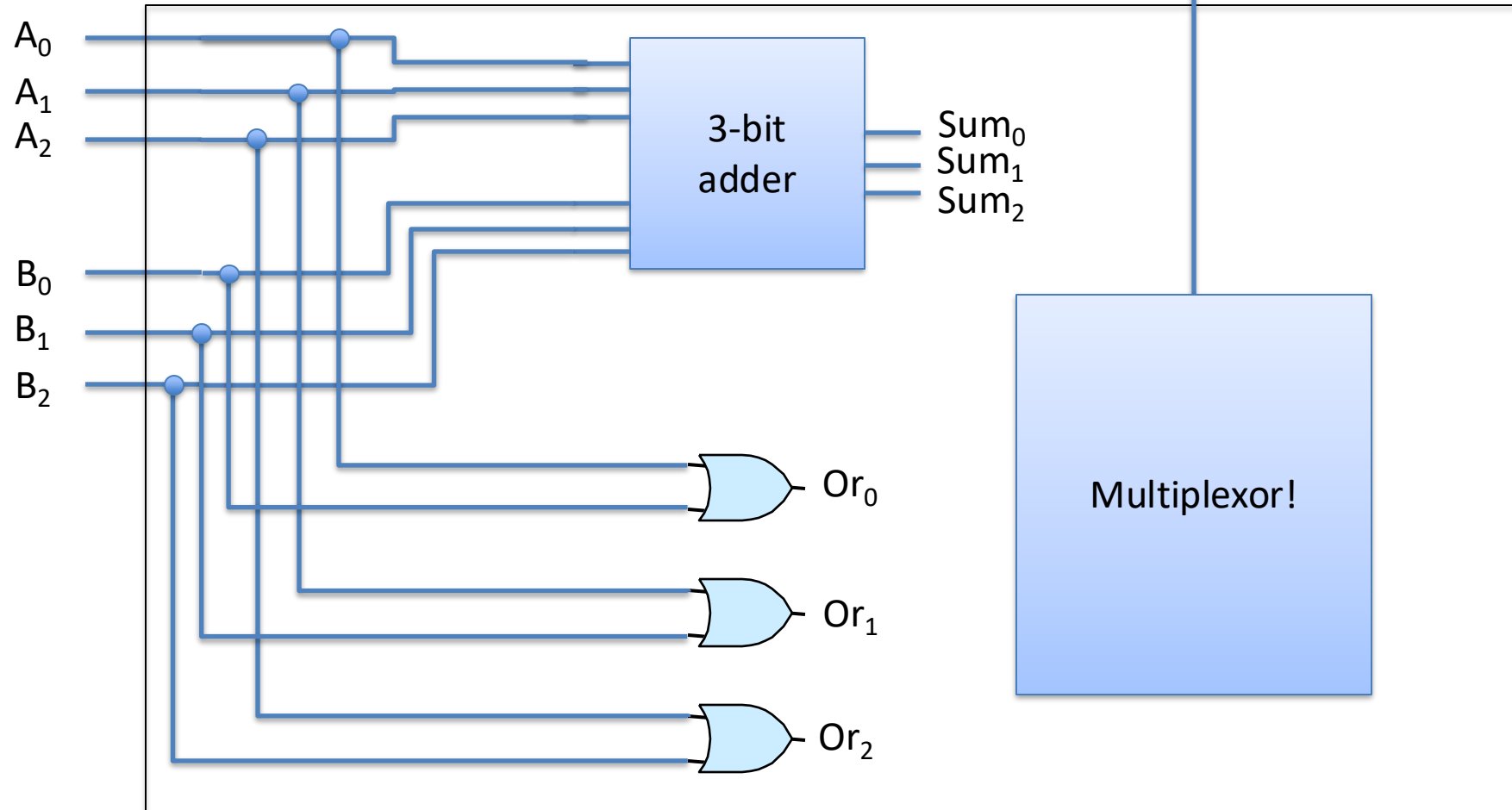Extra input: control signal to select Sum vs. OR



# ALU: Arithmetic Logic Unit

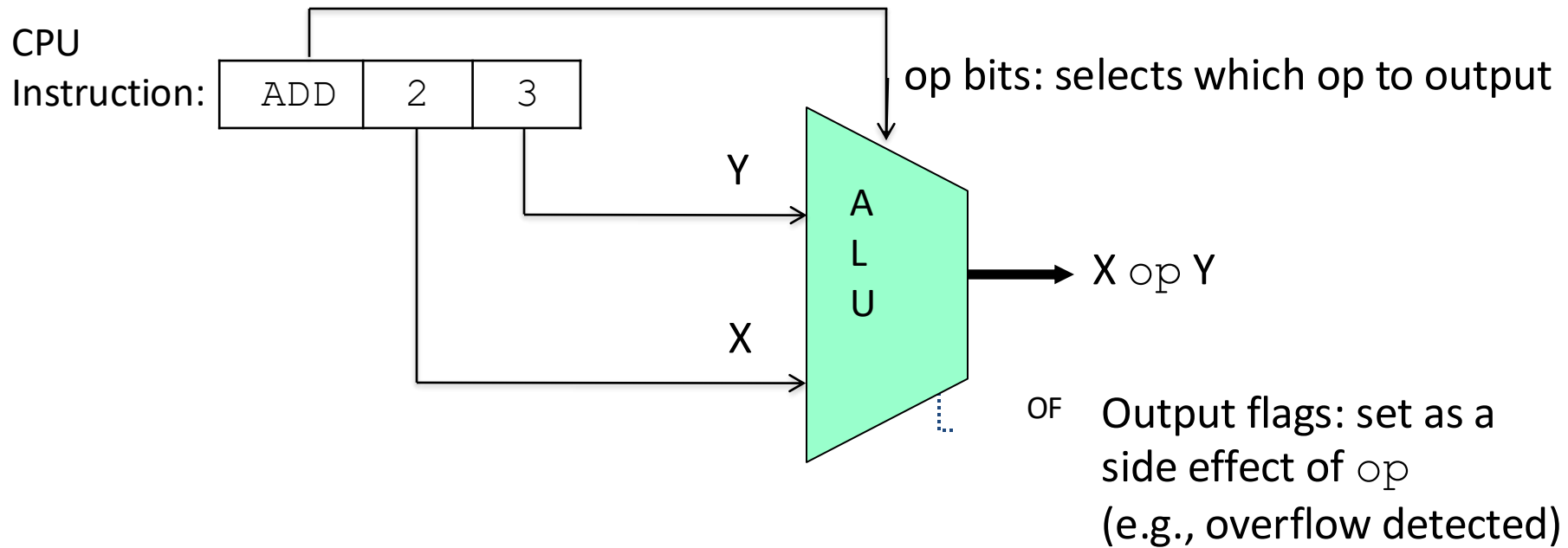


- Arithmetic and logic circuits: ADD, SUB, NOT, ...
- Control circuits: use op bits to select output
- Circuits around ALU:
  - Select input values X and Y from instruction or register
  - Select op bits from instruction to feed into ALU
  - Feed output somewhere


# Goal: Build a CPU (model)

## Three main classifications of hardware circuits:

 1. ALU: implement arithmetic & logic functionality
  - Example: adder circuit to add two values together
2. Storage: to store binary values
  - Example: set of CPU registers (“register file”) to store temporary values
3. Control: support/coordinate instruction execution
  - Example: circuitry to fetch the next instruction from memory and decode it



# Goal: Build a CPU (model)

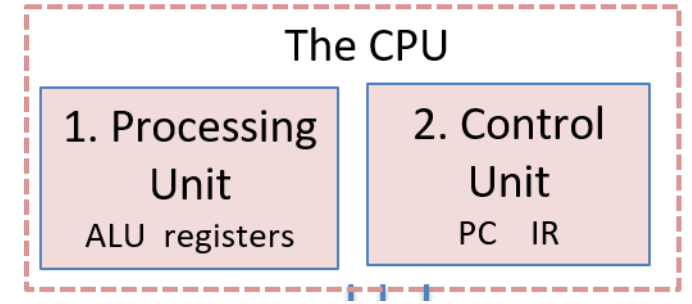

Three main classifications of hardware circuits:

2. Storage: to store binary values


– Example: set of CPU registers (“register file”) to store temporary values

Give the CPU a “scratch space” to perform calculations and keep track of the state its in.


 
## CPU so far...

- We can perform arithmetic!
- Storage questions:
  - Where do the ALU input values come from?
  - Where do we store the result?
  - What does this “register” thing mean?




# Memory Circuit Goals: Starting Small

- Store a 0 or 1
- Retrieve the 0 or 1 value on demand (read)
- Set the 0 or 1 value on demand (write)

# R-S Latch: Stores Value Q

When R and S are both 1: Maintain a value


R and S are never both simultaneously 0

 

- To write a new value:
  - Set S to 0 momentarily (R stays at 1): to write a 1
  - Set R to 0 momentarily (S stays at 1): to write a 0
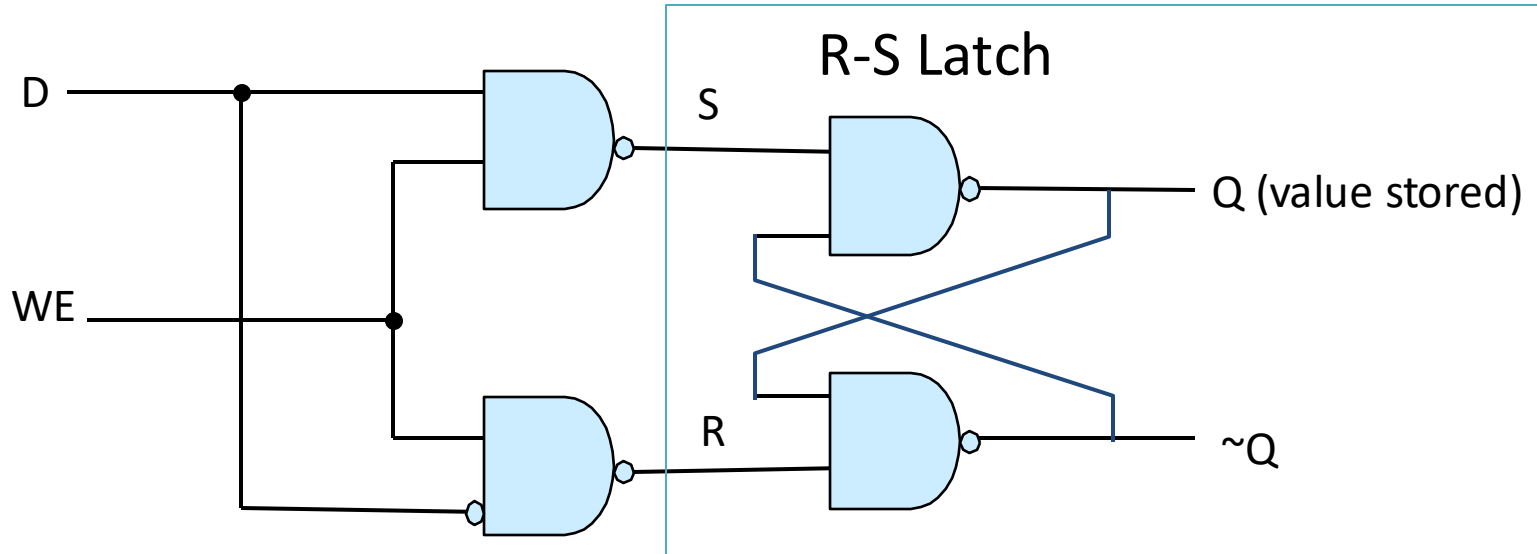
# Gated D Latch

Controls S-R latch writing, ensures S & R never both 0




D: into top NAND,  $\sim D$  into bottom NAND

WE: write-enabled, when set, latch is set to value of D

Latches used in registers (up next) and SRAM (caches, later)


Fast, not very dense, expensive

DRAM: capacitor-based:

 
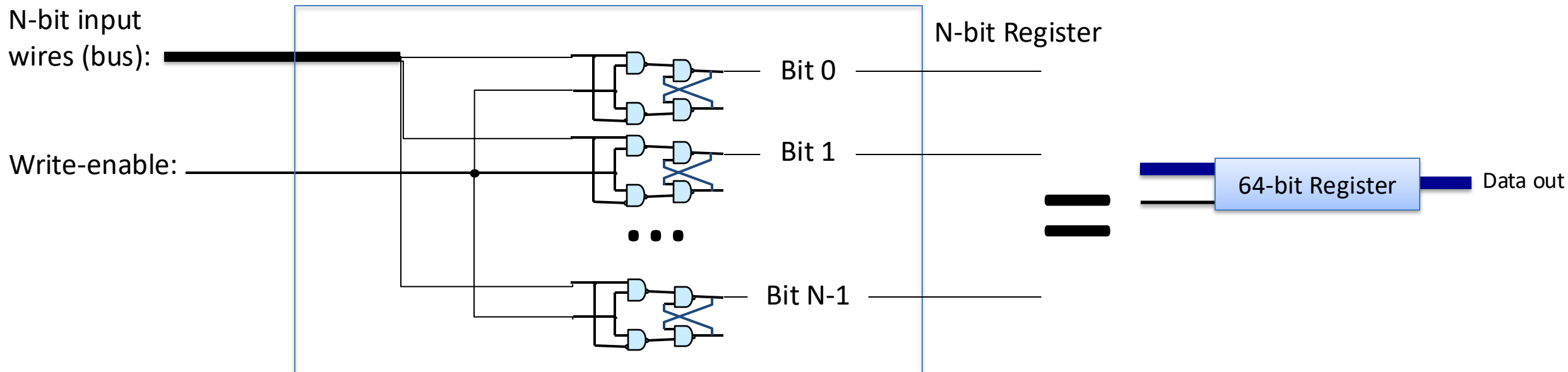
# An N-bit Register


- Fixed-size storage (8-bit, 32-bit, 64-bit, etc.)
- Gated D latch lets us store one bit
  - Connect N of them to the same write-enable wire!


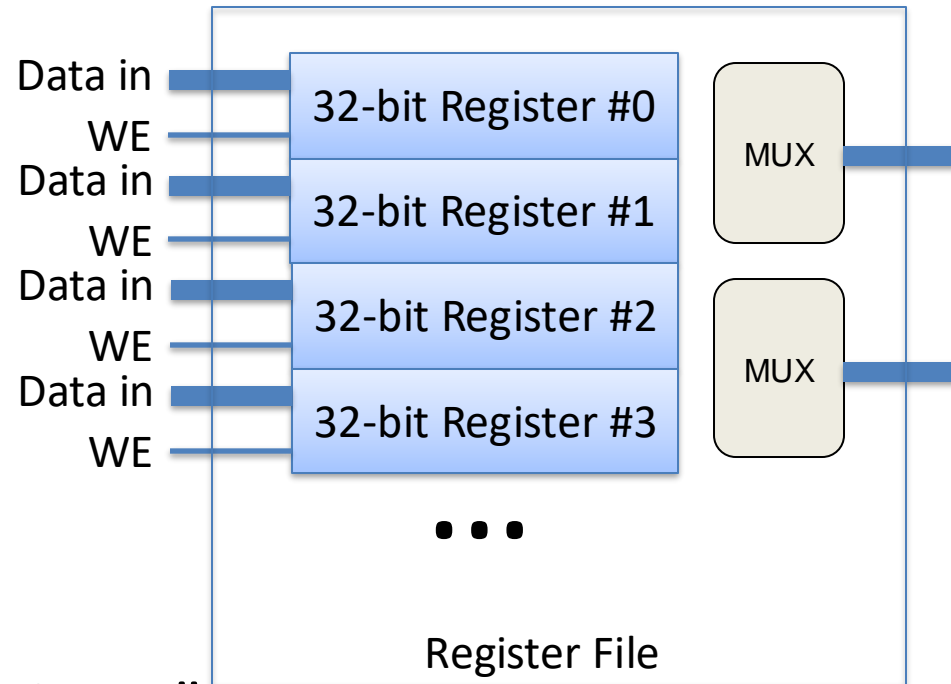
# “Register file”

- A set of registers for the CPU to store temporary values.

- This is (finally) something you will interact with!



- Instructions of form:
  - “add R1 + R2, store result in R3”

# Memory Circuit Summary

- Lots of abstraction going on here!
  - Gates hide the details of transistors.
  - Build R-S Latches out of gates to store one bit.
  - Combining multiple latches gives us N-bit register.
  - Grouping N-bit registers gives us register file.
- Register file's simple interface:
  - Read  $R_x$ 's value, use for calculation
  - Write  $R_y$ 's value to store result