

## **Welcome! *Do now:***

Set your clicker to frequency AA:

- hold the power button till lights flash
- press A twice
- lights should flash again

# Announcements

- Lab 1 grades posted — y'all did well! But <please> don't get complacent.
- Clickers:
  - Present/absent: answered more than 50% of the questions
  - Correctness: check+ (>50% correct), check (<50% correct), 0 (absent)
  - IGNORE what you see on iClicker Cloud! (\*raises fists at developers\*)

# Revisiting...

- Left and Right shift
- Overflow: signed vs unsigned

# Why did the US decide to ban exports of certain computer chips to China?

- A. To slow down China's military capabilities
- B. To slow down China's manufacturing industry
- C. To slow down China's AI industry
- D. Xenophobia
- E. None of these


Why did the US decide to ban exports of certain computer chips to China?

- A. To slow down China's military capabilities
- B. To slow down China's manufacturing industry
- C. To slow down China's AI industry**
- D. Xenophobia
- E. None of these

# Moore's Law: The number of transistors on microchips doubles every two years

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important for other aspects of technological progress in computing – such as processing speed or the price of computers.

## Transistor count

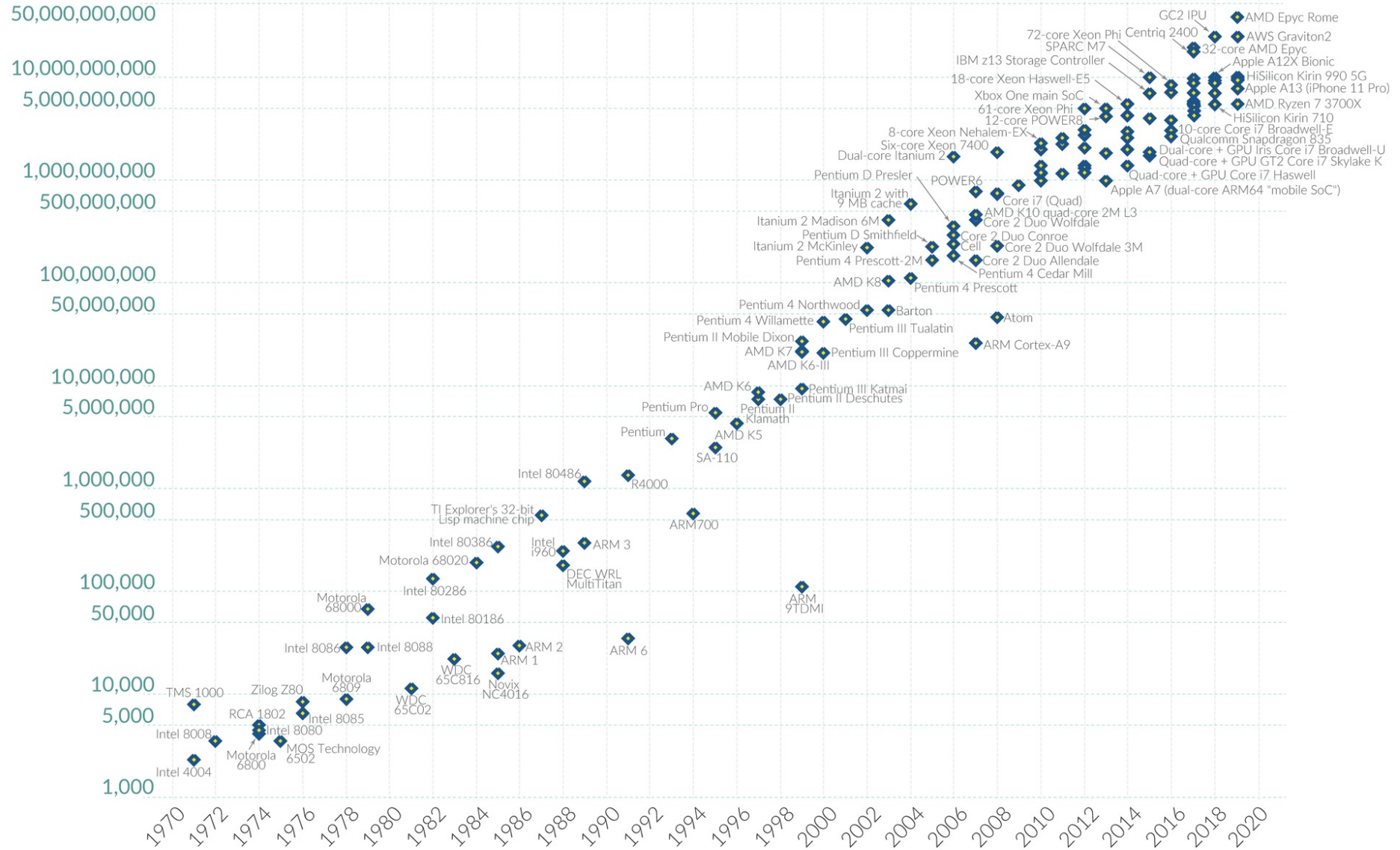

Data source: Wikipedia ([wikipedia.org/wiki/Transistor\\_count](https://wikipedia.org/wiki/Transistor_count))

# Moore's Law

- In 1965: Intel co-founder Gordon Moore **predicted** a doubling of transistors every year for the next 10 years in his original paper published in 1965.
- Today: An **observation** that the number of transistors on a microchip roughly doubles every two years, while cost is halved over the same time period.

Your mission, if you choose to accept it:

**Build a CPU**

This message will self-destruct in...



# Abstraction

User / Programmer  
Wants low complexity




Applications  
Specific functionality




Software library  
Reusable functionality




Operating system  
Manage resources

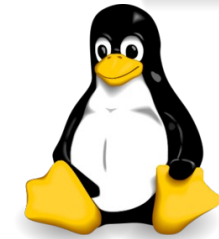

Complex devices  
Compute & I/O

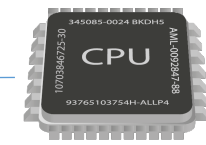

# Abstraction

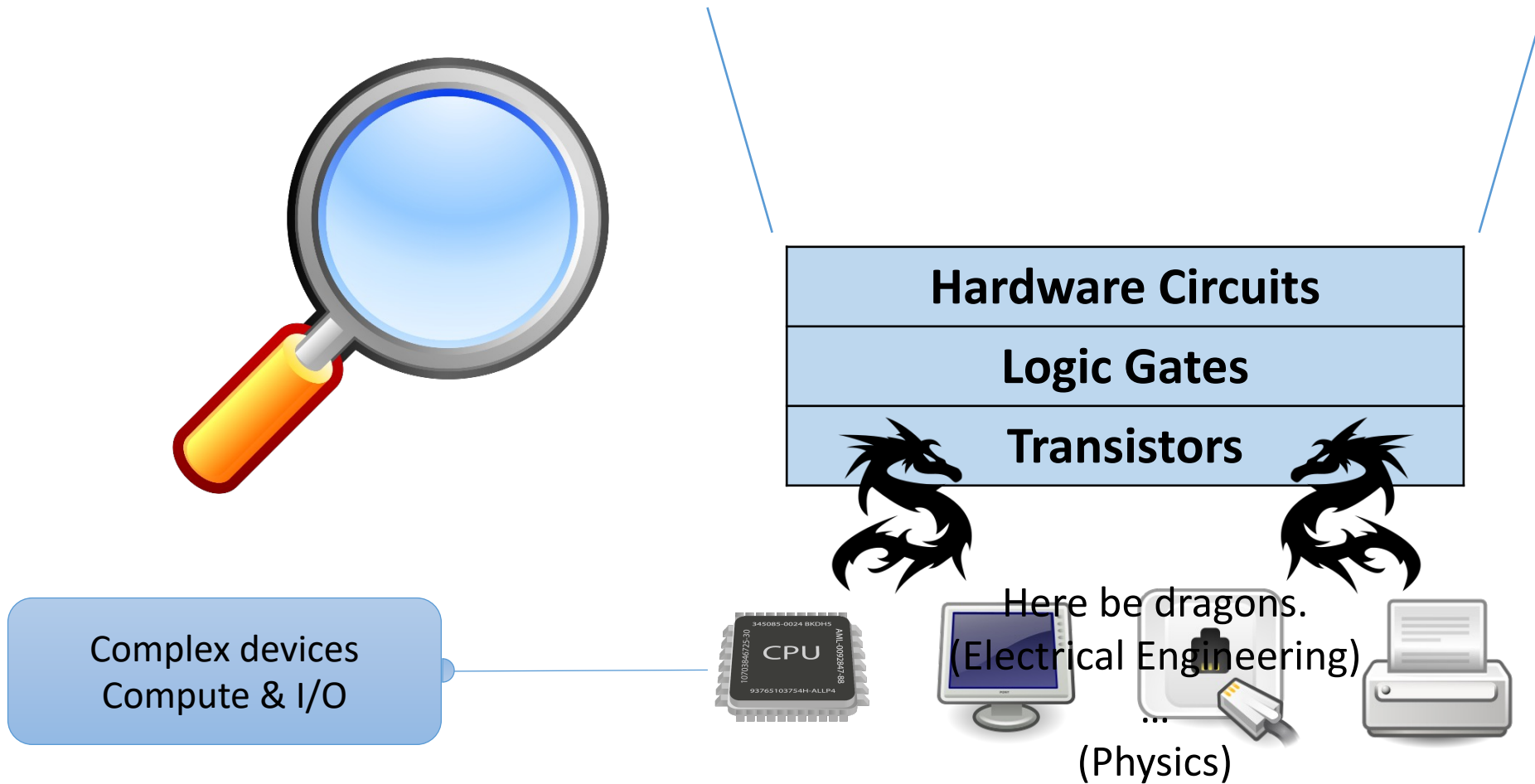

# Abstraction Towards a CPU



Transistors

Logic Gates

Simple Circuits


Arithmetic & Logic Circuits

Data Storage Circuits (Latches)

ALU & MUX

Registers

CPU

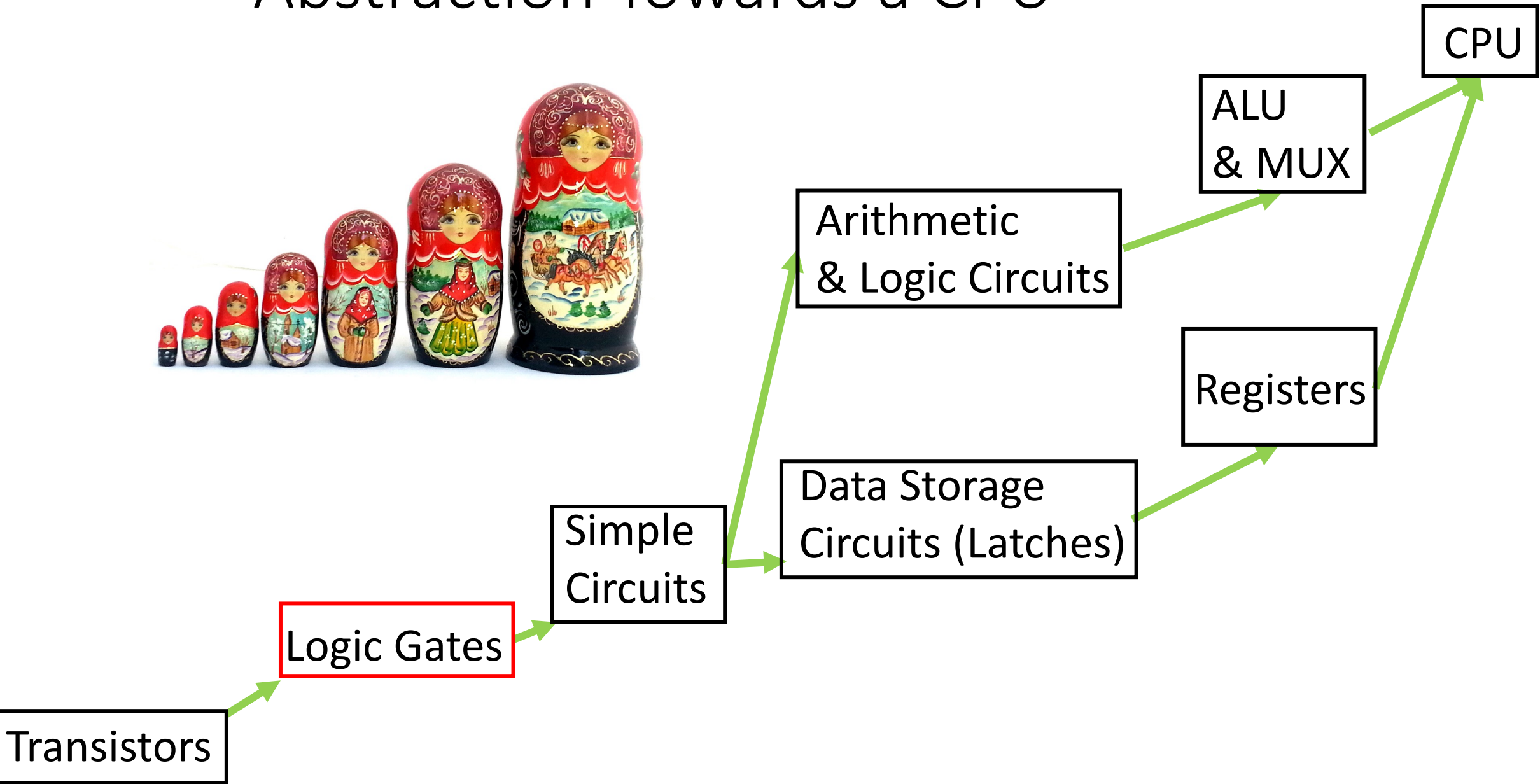


# Logic Gates

Input: Boolean value(s) (high and low voltages for 1 and 0)



Output: Boolean value result of Boolean function

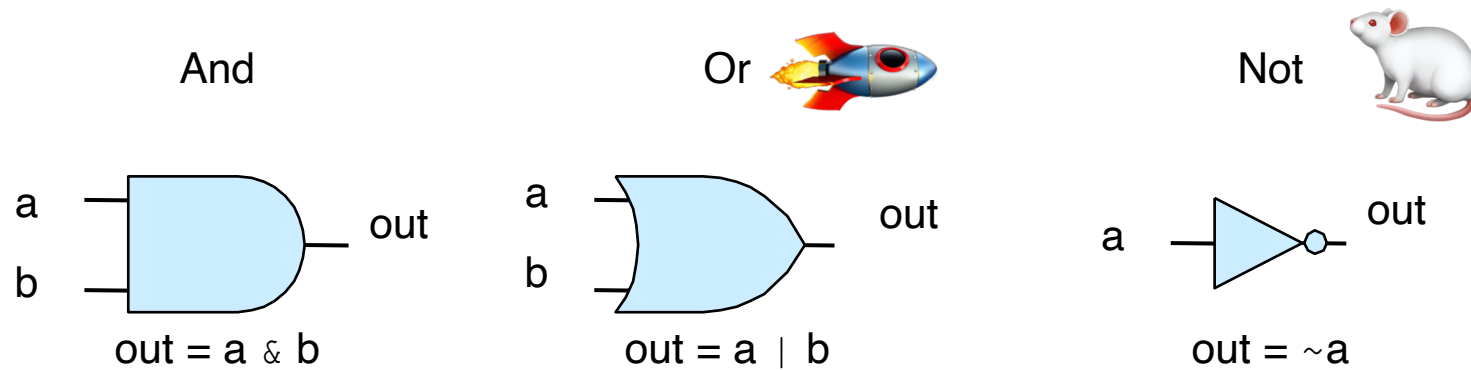Always present, but may change when input changes



A	B	A & B	A   B	~A
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0

# More Logic Gates

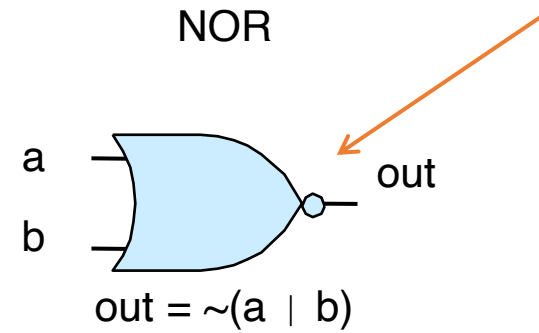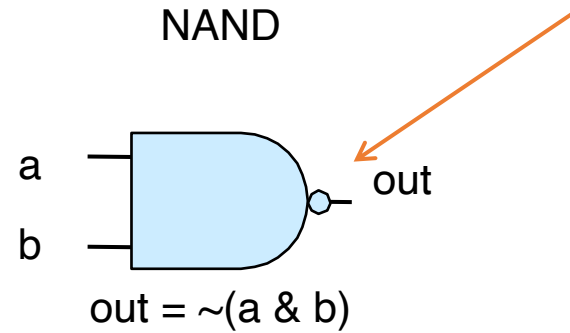


Note the circle on the output. This circle means bitwise "not" (flip bits).

A	B	A NAND B	A NOR B
0	0	1	1
0	1	1	0
1	0	1	0
1	1	0	0




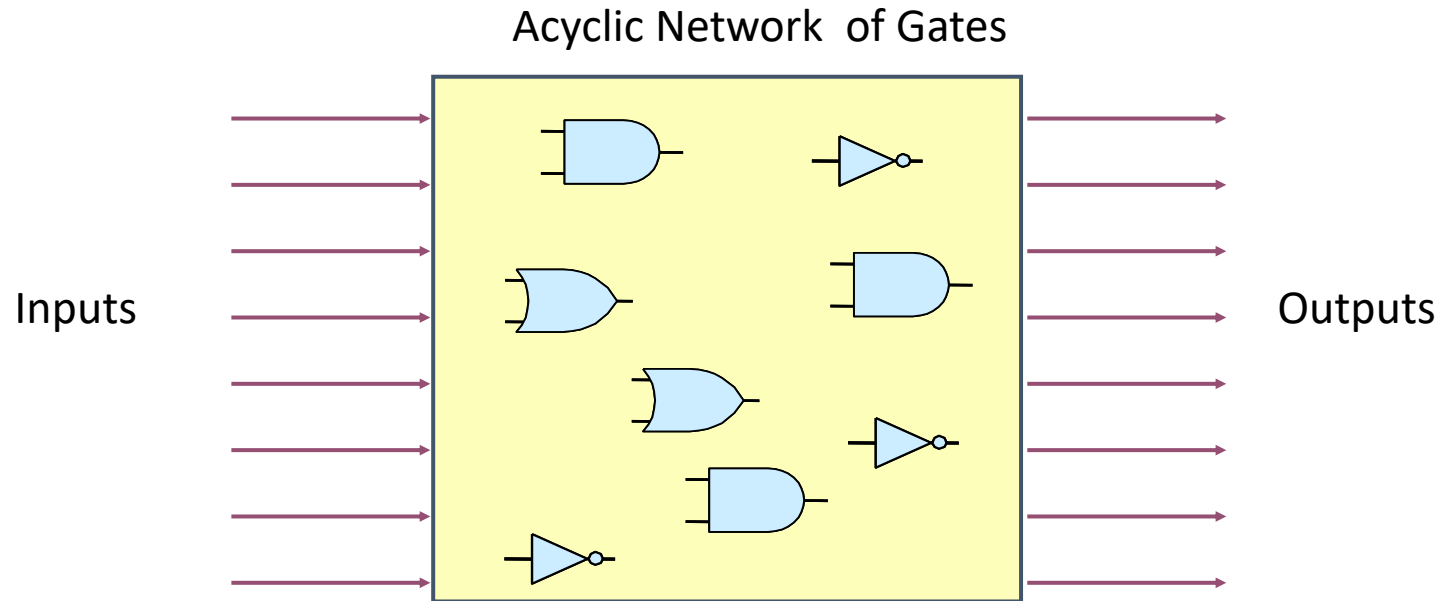
# Combinational Logic Circuits

- Build up higher level processor functionality from basic gates



- Outputs are boolean functions of inputs
- Outputs continuously respond to changes to inputs



# What does this circuit output?

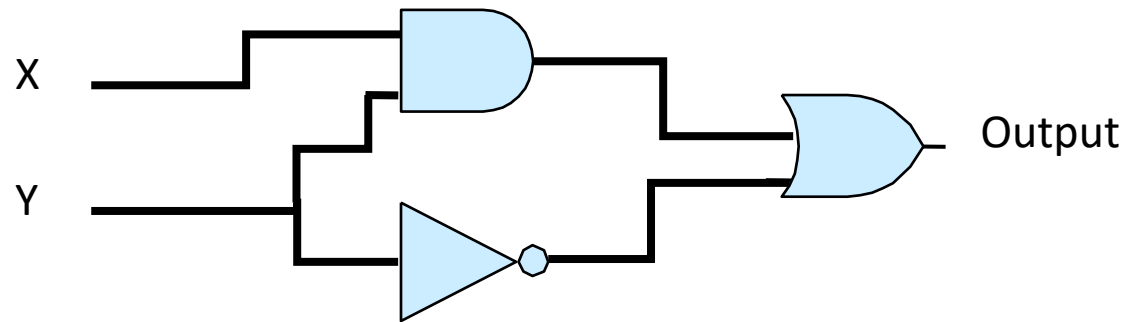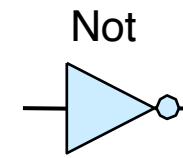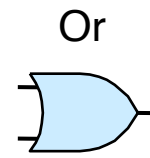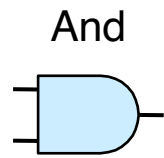

Clicker Choices

X	Y
0	0
0	1
1	0
1	1

# What does this circuit output?

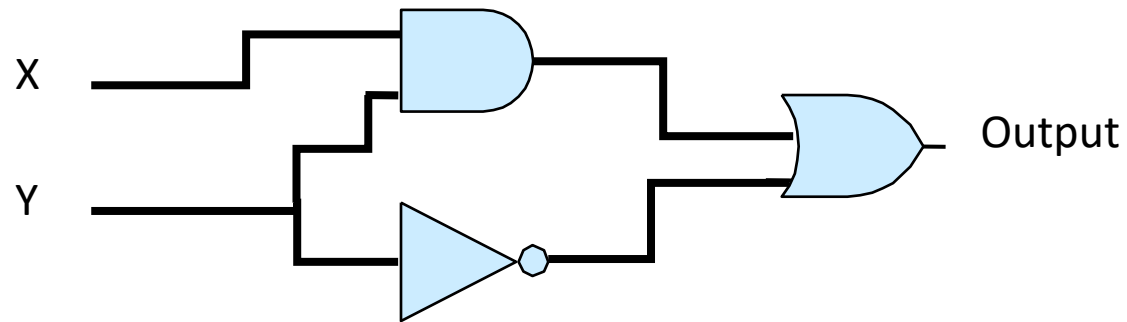
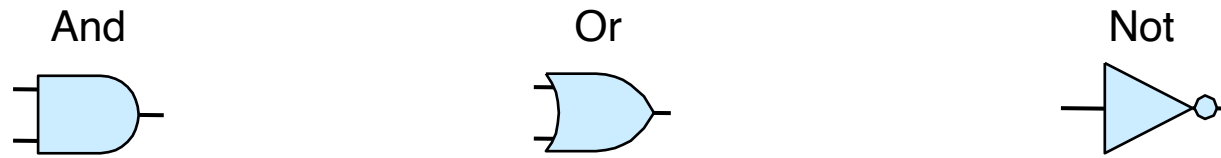


Clicker Choices

X	Y	Out <sub>A</sub>	Out <sub>B</sub>	Out <sub>C</sub>	Out <sub>D</sub>	Out <sub>E</sub>
0	0	0	1	0	1	0
0	1	0	1	0	0	1
1	0	1	0	1	1	1
1	1	0	0	1	1	0



# What does this circuit output?

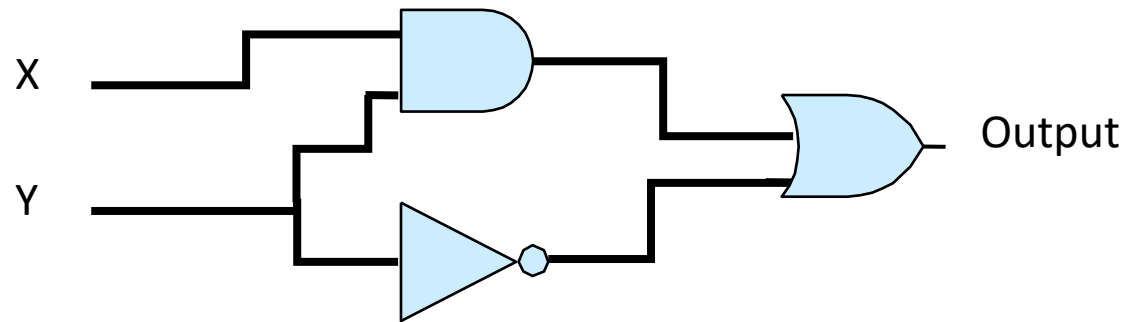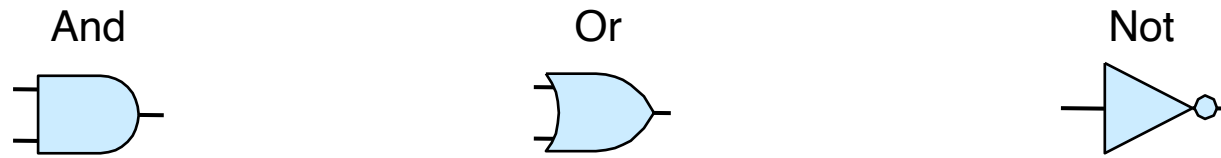

Clicker Choices

X	Y	Out <sub>A</sub>	Out <sub>B</sub>	Out <sub>C</sub>	Out <sub>D</sub>	Out <sub>E</sub>
0	0	0	1	0	1	0
0	1	0	1	0	0	1
1	0	1	0	1	1	1
1	1	0	0	1	1	0


# Building more interesting circuits...

- Build-up XOR from basic gates (AND, OR, NOT)




A	B	$A \wedge B$
0	0	0
0	1	1
1	0	1
1	1	0

- Q: When is  $A \wedge B == 1$ ?

# Abstraction Towards a CPU

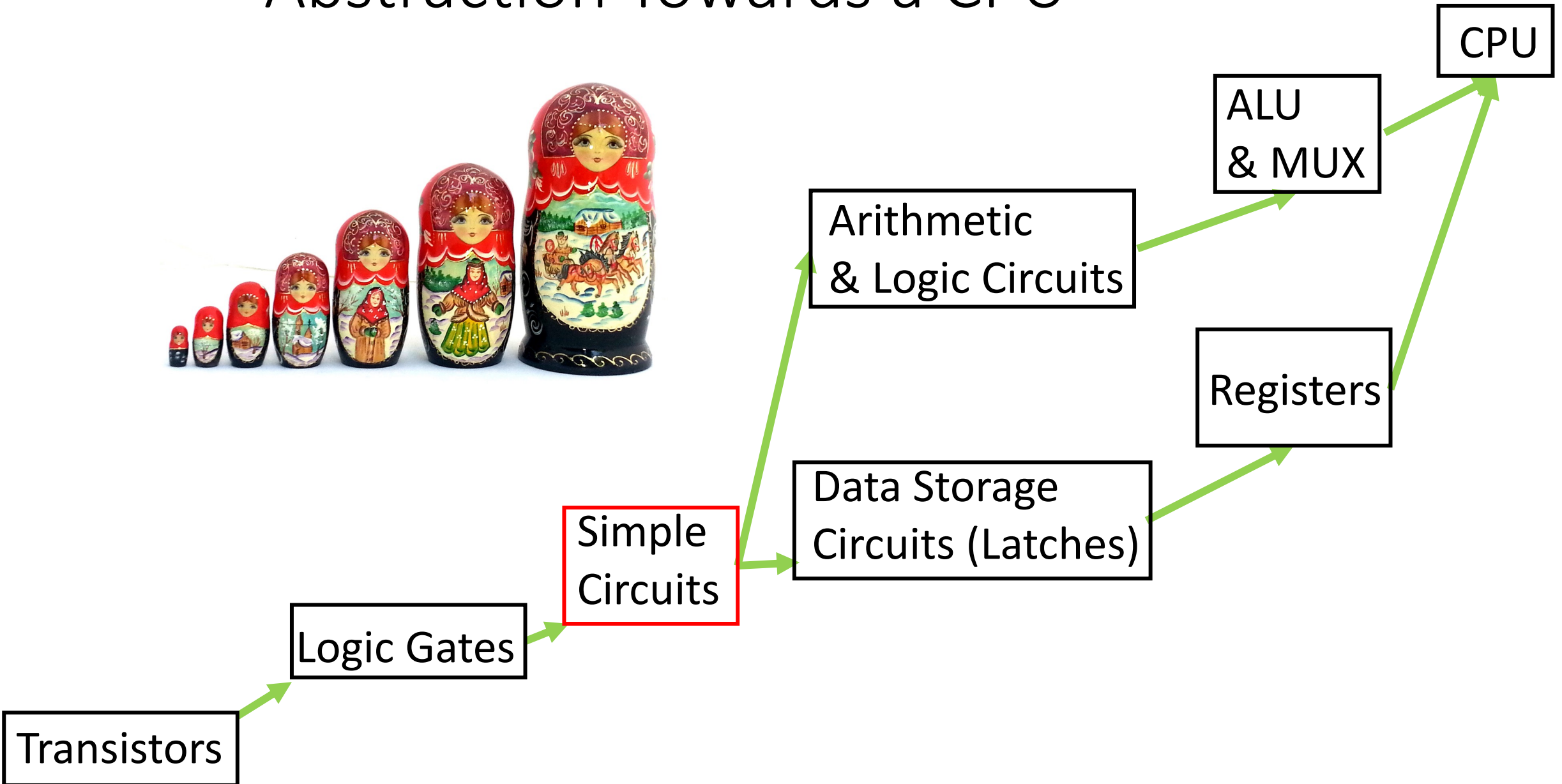

# Building an XOR circuit

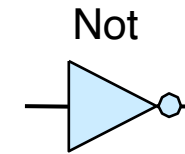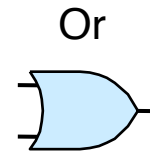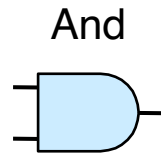

- General strategy:

1. Determine truth table (given ->)




2. Determine for which rows the result is 1

- express each row with 1 result in terms of input values A, B combined with AND, NOT
- combine each row expression with OR

3. Translate expression to a circuit

A	B	$A \wedge B$
0	0	0
0	1	1
1	0	1
1	1	0

# Which of these is an XOR circuit?


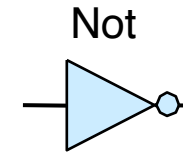
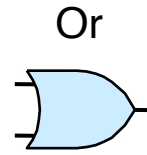
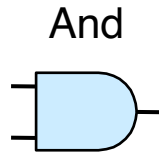


Draw an XOR circuit using AND, OR, and NOT gates.

I'll show you the clicker options after you've had some time.





A	B	$A \wedge B$
0	0	0
0	1	1
1	0	1
1	1	0

# Which of these is an XOR circuit?

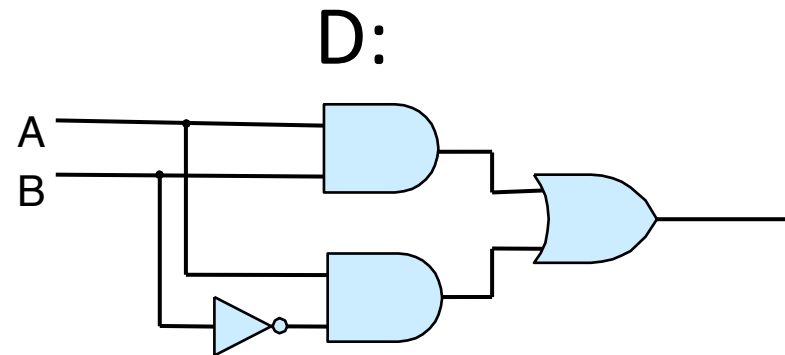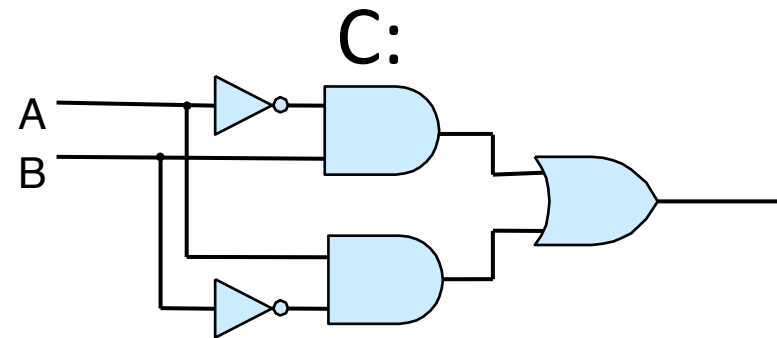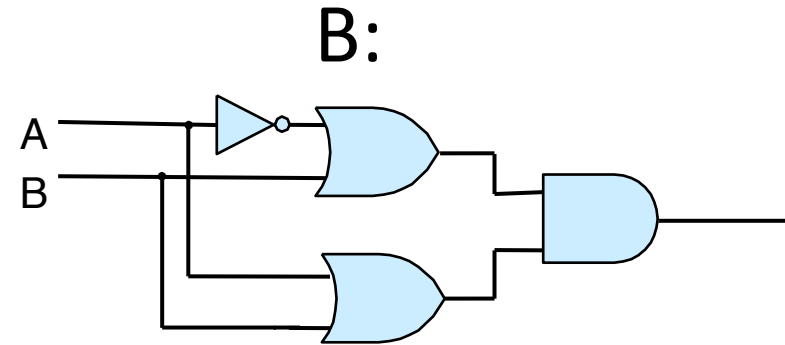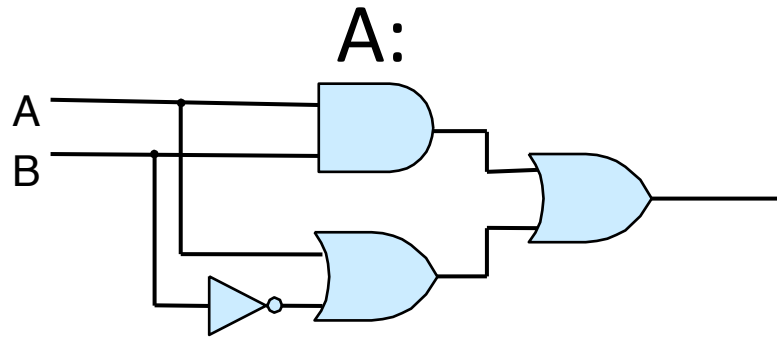

E: None of these are XOR.


# Which of these is an XOR circuit?

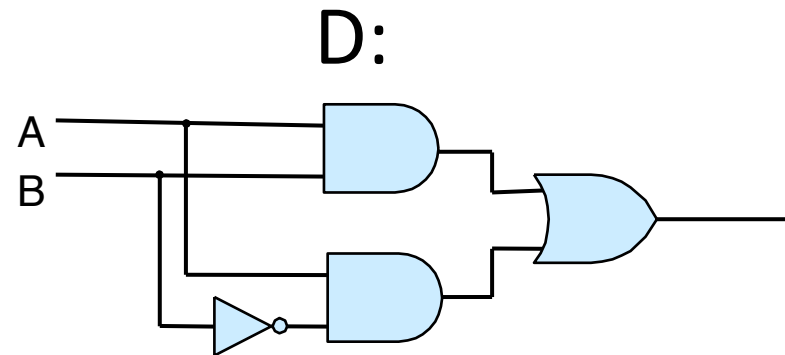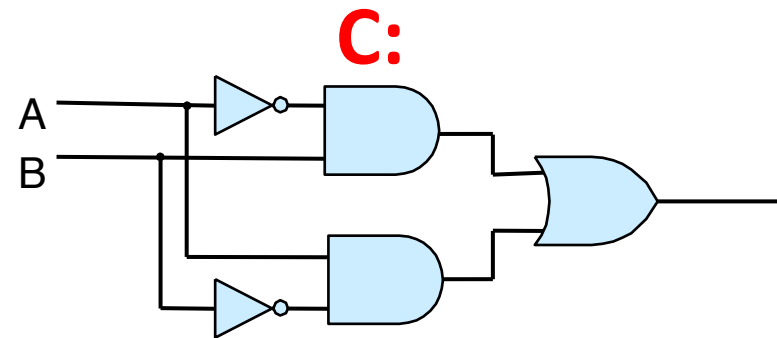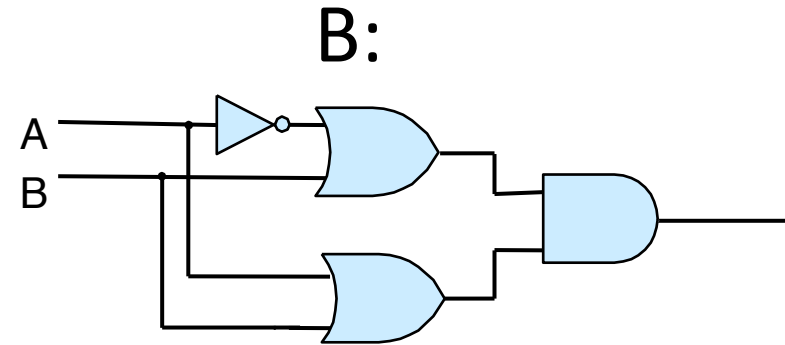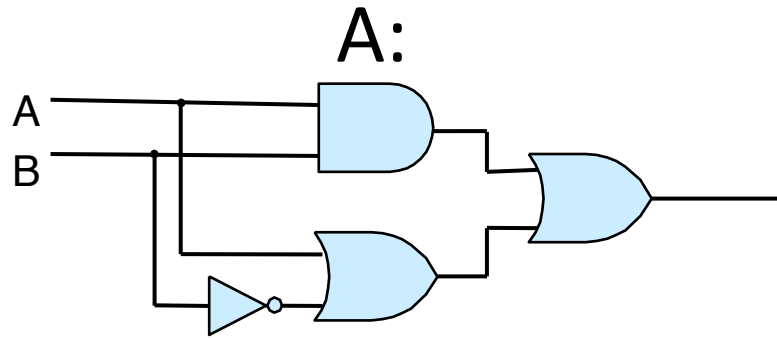

E: None of these are XOR.

# XOR Circuit: Abstraction

$$A \oplus B == (\sim A \ \& \ B) \ | \ (A \ \& \ \sim B)$$

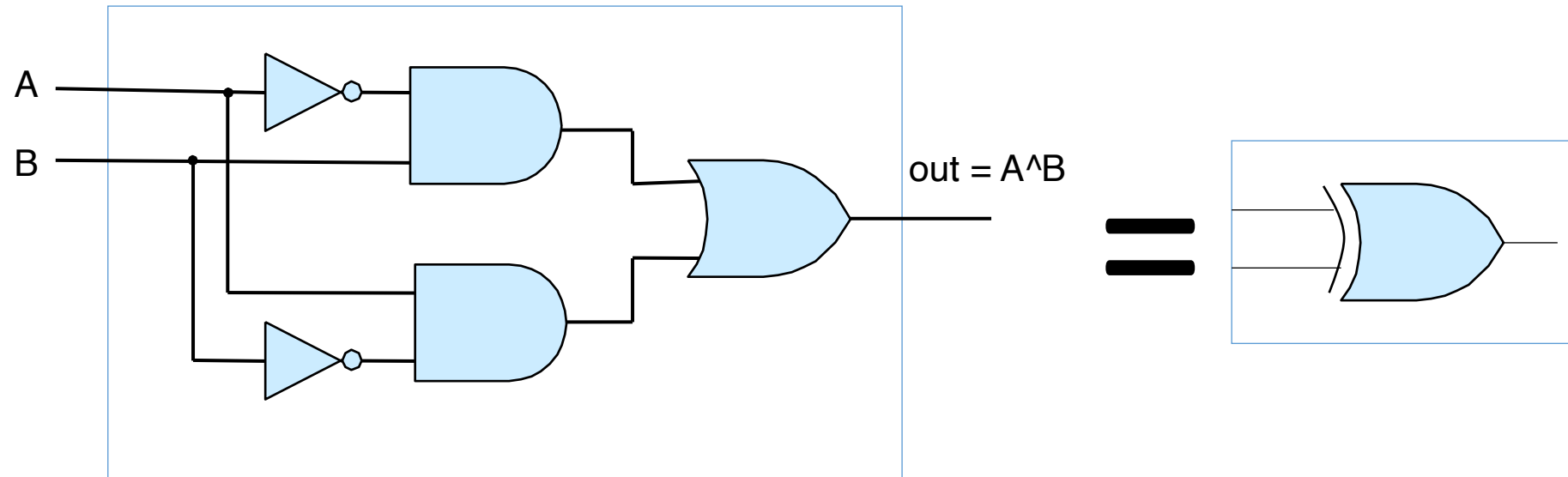

A:0 B:0 A^B:

A:0 B:1 A^B:

A:1 B:0 A^B:


A:1 B:1 A^B:



# Recall Goal: Build a CPU (model)

## Three main classifications of hardware circuits:

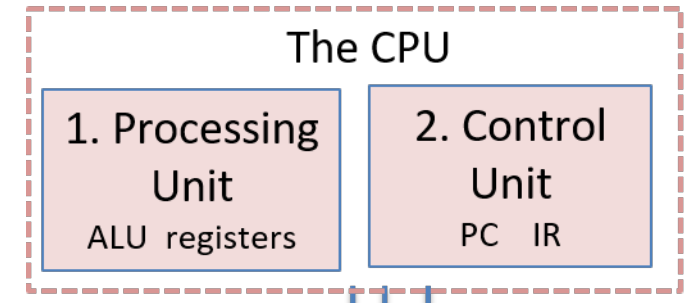1. ALU: implement arithmetic & logic functionality
  - Example: adder circuit to add two values together
2. Storage: to store binary values
  - Example: set of CPU registers (“register file”) to store temporary values
3. Control: support/coordinate instruction execution
  - Example: circuitry to fetch the next instruction from memory and decode it




# Recall Goal: Build a CPU (model)

## Three main classifications of hardware circuits:


1. ALU: implement arithmetic & logic functionality
  - Example: adder circuit to add two values together

Start with ALU components (e.g., adder circuit, bitwise operator circuits)

Combine component circuits into ALU!

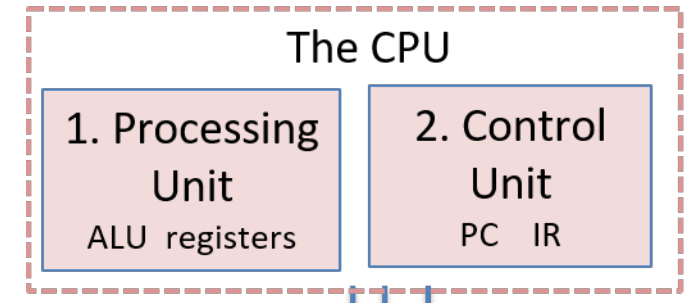

# Abstraction Towards a CPU

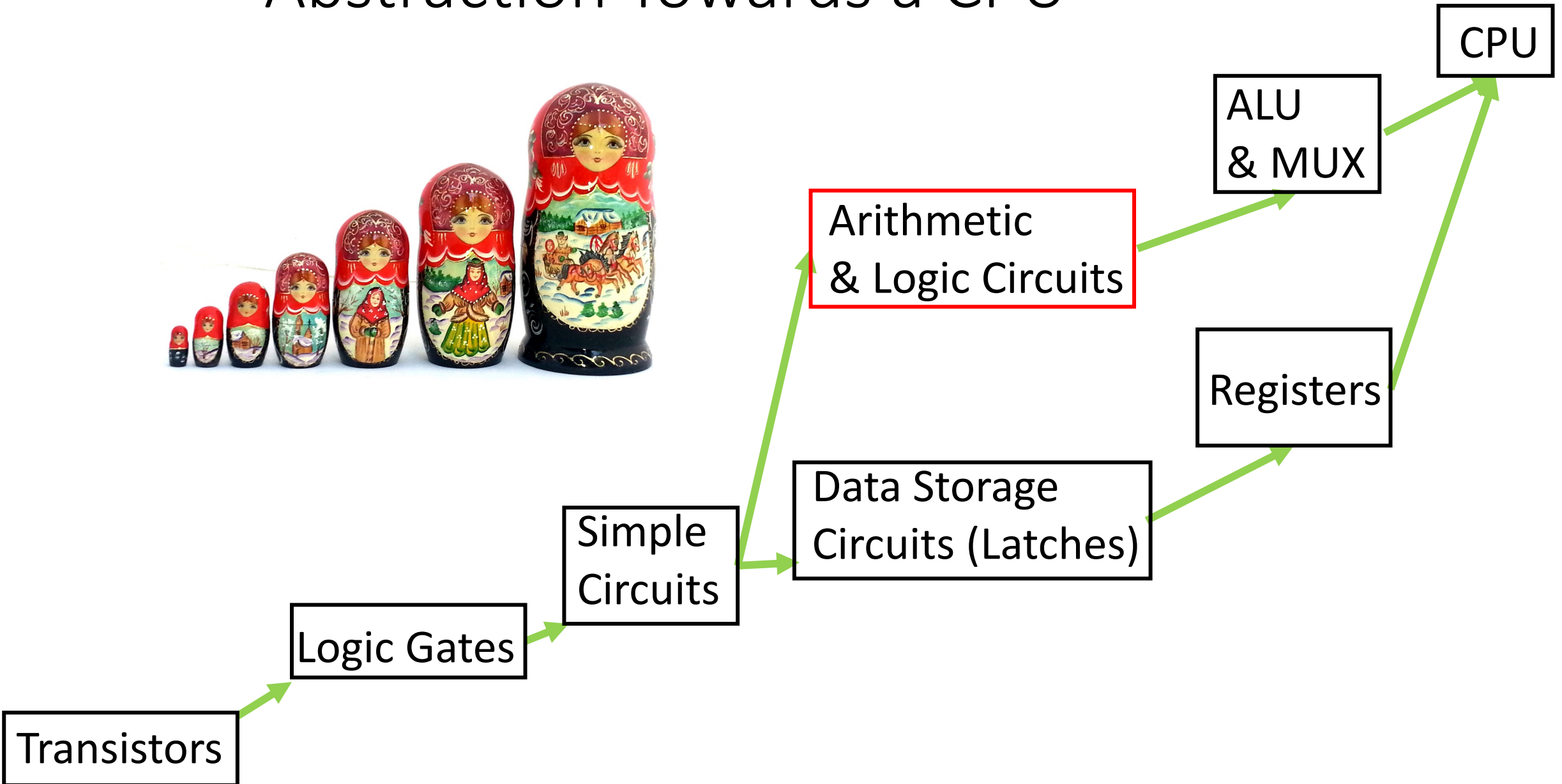





# Arithmetic Circuits

- 1 bit adder:  $A+B$
- Two outputs:
  1. Obvious one: the sum
  2. Other one: ??

A	B	Sum (A + B)	$C_{out}$
0	0		
0	1		
1	0		
1	1		





# Which of these circuits is a one-bit adder?

A	B	Sum (A + B)	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

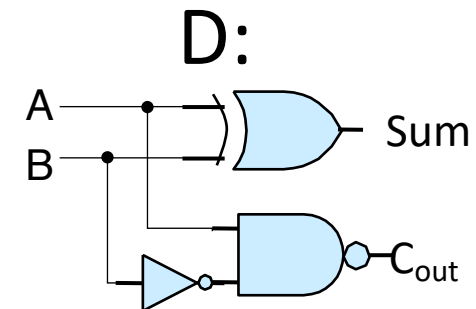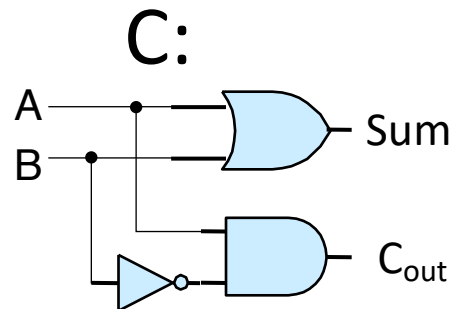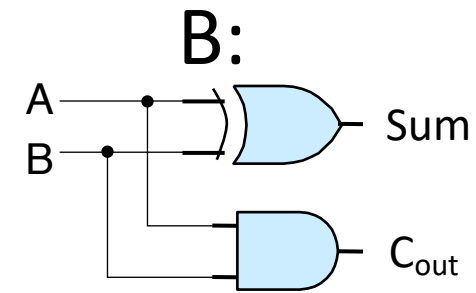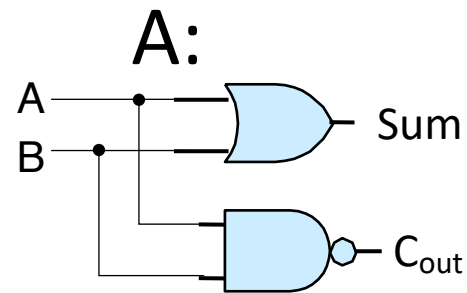

# Which of these circuits is a one-bit adder?

A	B	Sum (A + B)	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

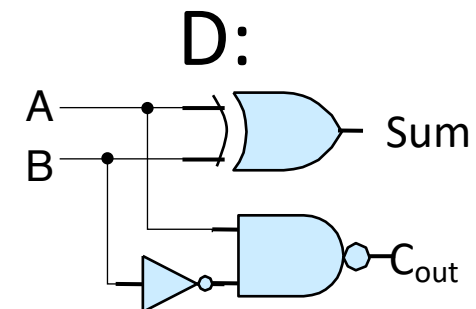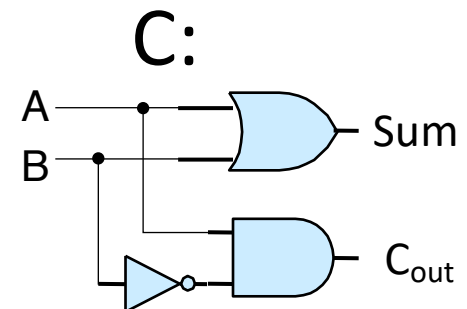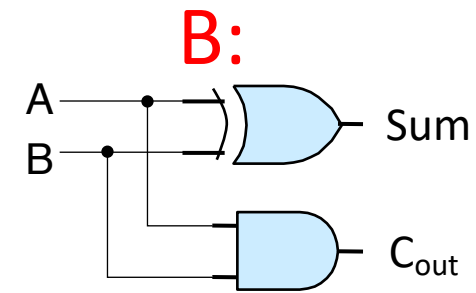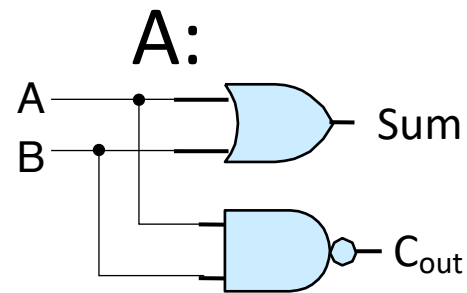

# More than one bit?

- When adding, we sometimes have *carry in* too

$$\begin{array}{r} \phantom{+} \phantom{00} 1111 \\ \phantom{+} 0011010 \\ + \phantom{00} \underline{0001111} \end{array}$$

Write Boolean expressions for  $\text{Sum} = 1$  and  $C_{\text{out}} = 1$

A	B	$C_{\text{in}}$	Sum	$C_{\text{out}}$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

- When is  $\text{Sum}$  1?
- When is  $C_{\text{out}}$  1?



Write Boolean expressions for  $\text{Sum} = 1$  and  $C_{\text{out}} = 1$

A	B	$C_{\text{in}}$	Sum	$C_{\text{out}}$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

- When is **Sum** 1?

$$\sim C_{\text{in}} \ \& \ (A \wedge B) \ | \ C_{\text{in}} \ \& \ \sim (A \wedge B) \ == \ (C_{\text{in}} \ \wedge \ (A \wedge B))$$

- When is  $C_{\text{out}}$  1?

Write Boolean expressions for  $\text{Sum} = 1$  and  $C_{\text{out}} = 1$

A	B	$C_{\text{in}}$	Sum	$C_{\text{out}}$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

- When is **Sum** 1?

$$\sim C_{\text{in}} \ \& \ (A \wedge B) \ | \ C_{\text{in}} \ \& \ \sim (A \wedge B) \ == \ (C_{\text{in}} \ \wedge \ (A \wedge B))$$


- When is  $C_{\text{out}}$  1?

$$(A \ \& \ B) \ | \ ((A \wedge B) \ \& \ C_{\text{in}})$$


# One-bit (full) adder

- Need to include:  
**carry-in** and **carry-out**


A	B	$C_{in}$	Sum	$C_{out}$
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

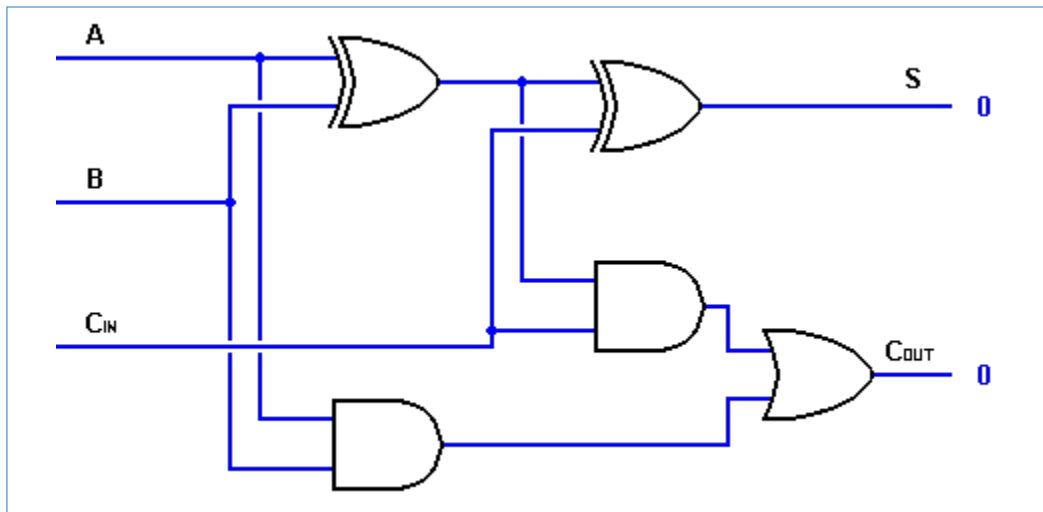

=

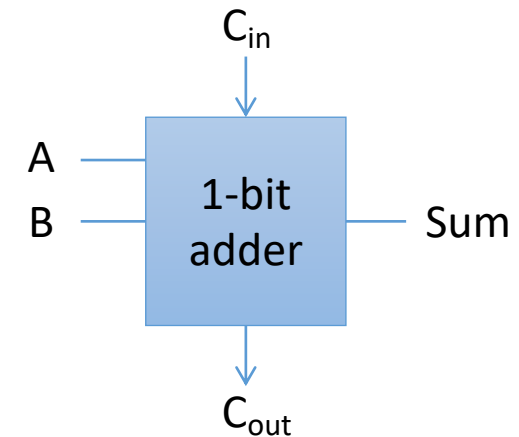


# Multi-bit Adder (Ripple-carry Adder)

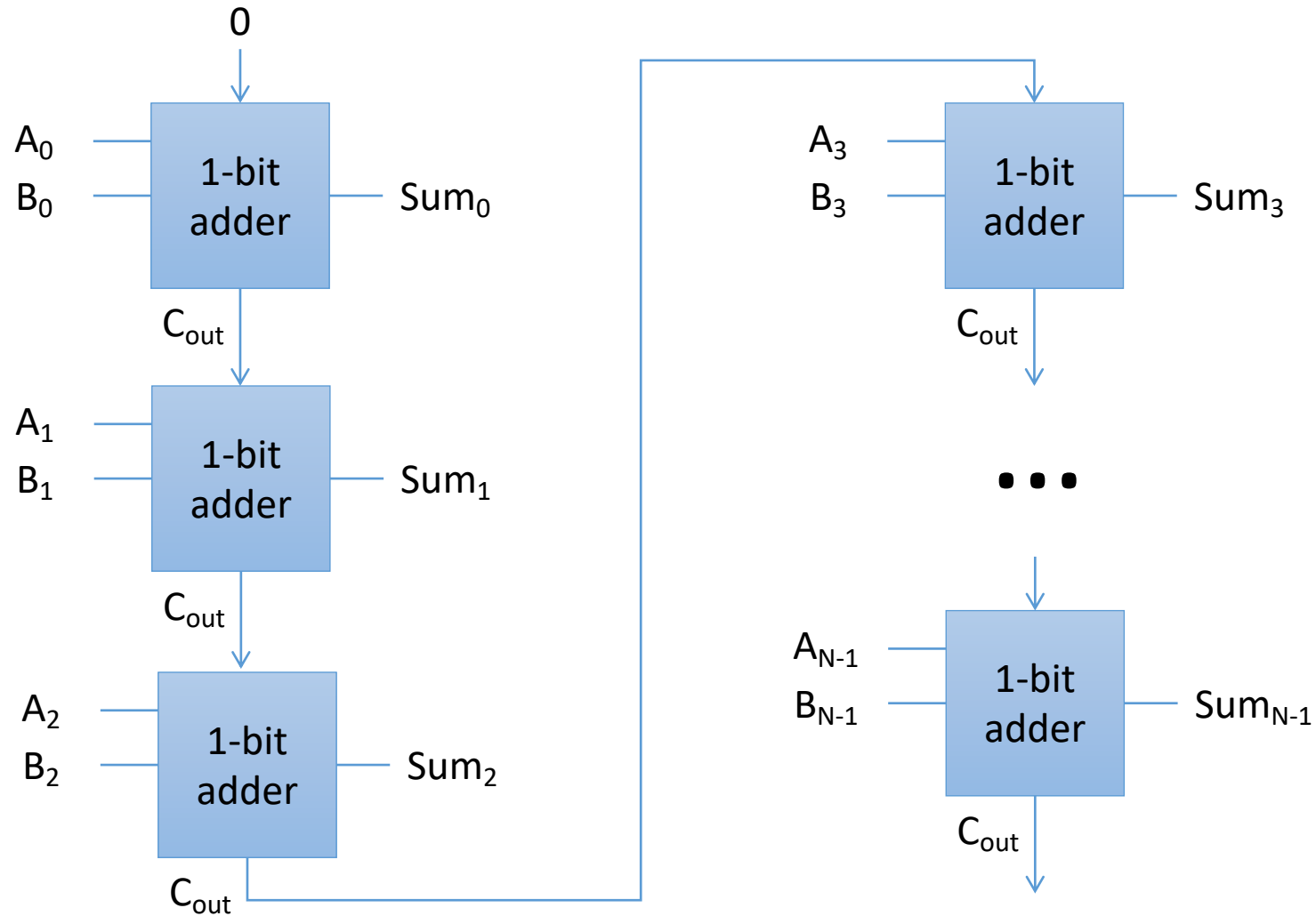

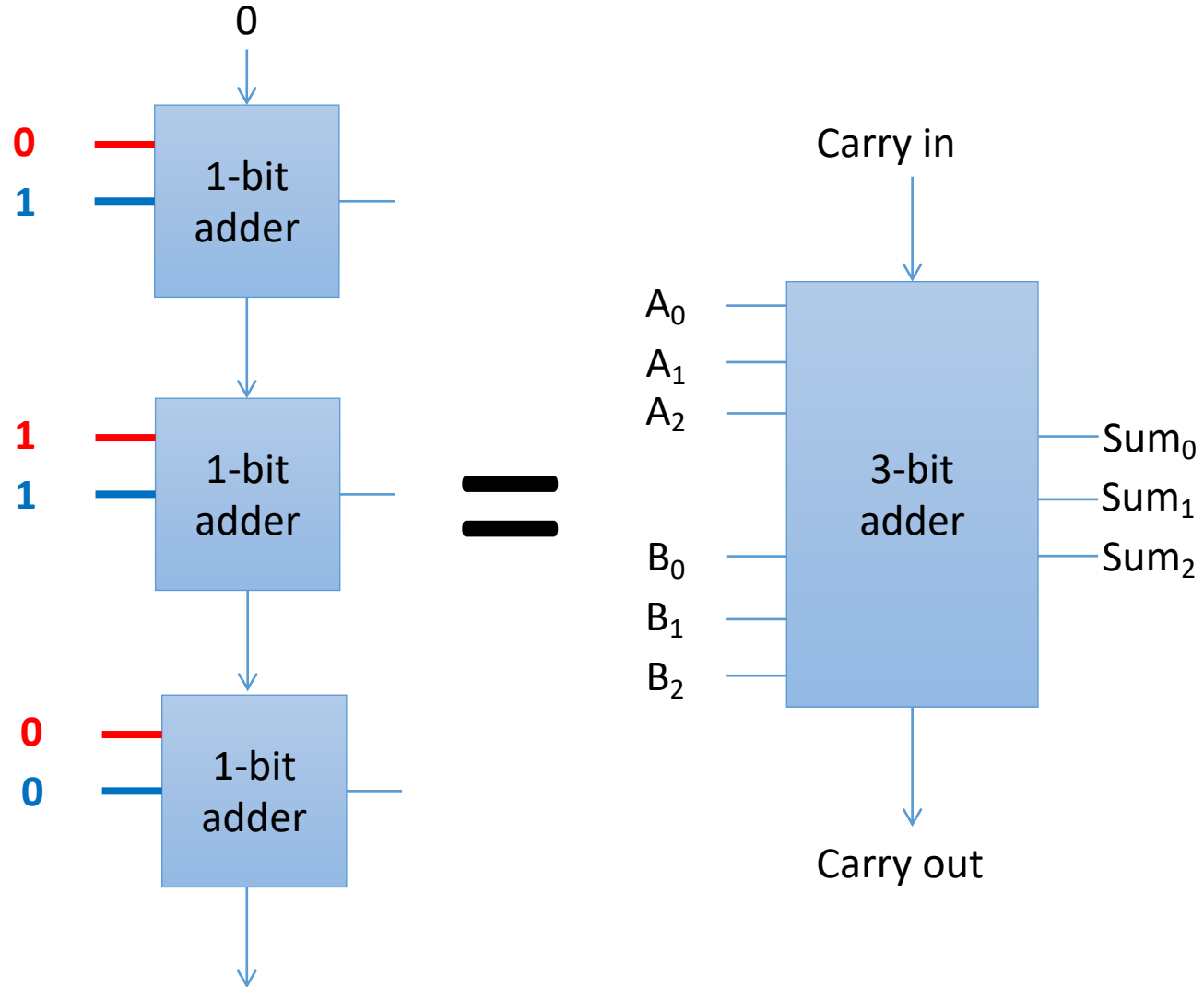
# Three-bit Adder (Ripple-carry Adder)

$$\begin{array}{r} 010 \\ + 011 \\ \hline \end{array}$$



# Abstraction Towards a CPU

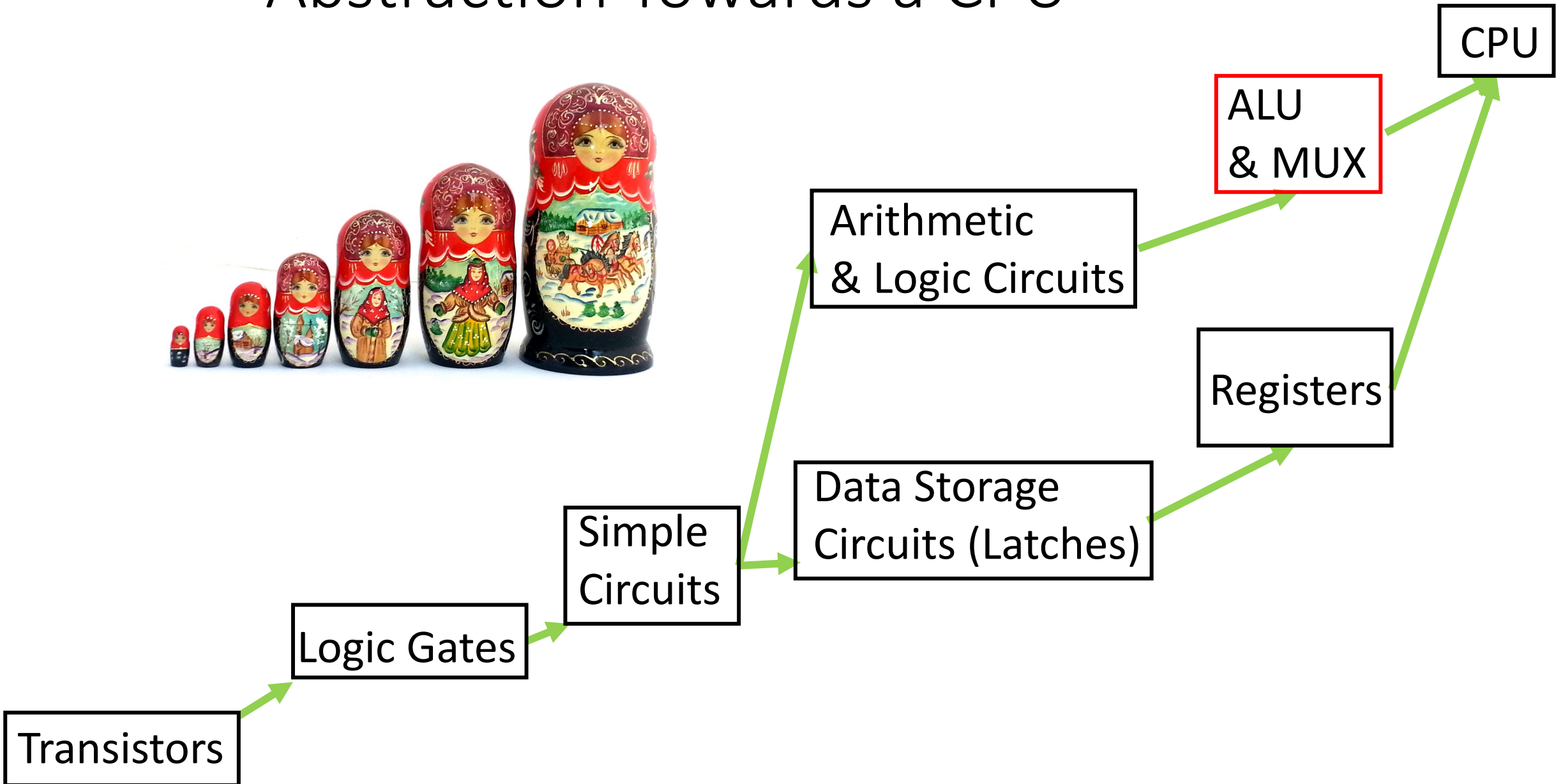

# Arithmetic Logic Unit (ALU)

- One component that knows how to manipulate bits in multiple ways
  - Addition
  - Subtraction
  - Multiplication / Division
  - Bitwise AND, OR, NOT, etc.
- Built by combining components
  - Take advantage of abstraction and sharing/reusing hardware when possible (e.g., subtraction using adder)

# Simple 3-bit ALU: Add and bitwise OR

3-bit inputs

A and B:

$A_0$

$A_1$

$A_2$

$B_0$


$B_1$

$B_2$

$Out_0$

$Out_1$

$Out_2$

 




# Simple 3-bit ALU: Add and bitwise OR

3-bit inputs

A and B:

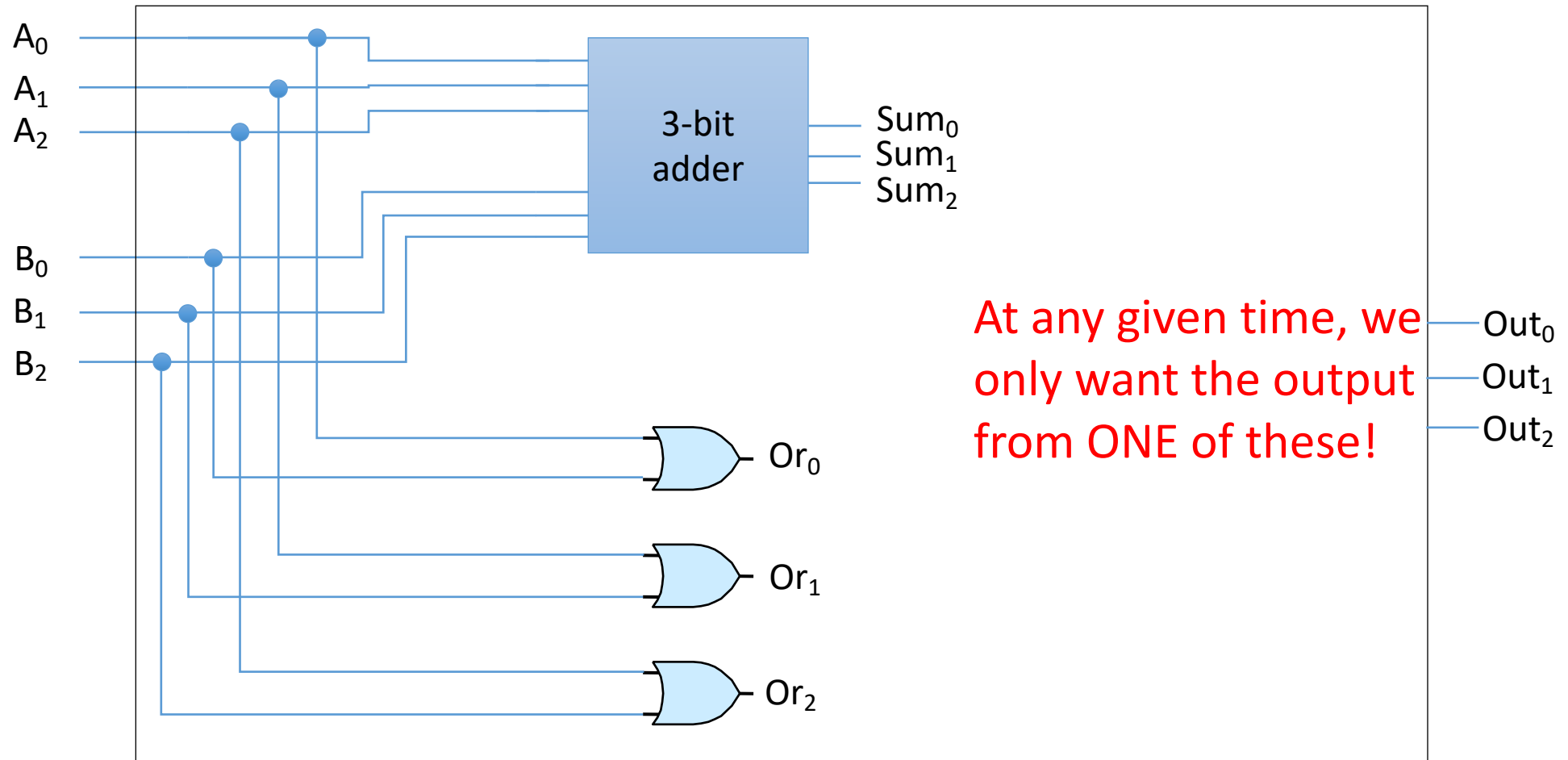


# Simple 3-bit ALU: Add and bitwise OR




3-bit inputs

A and B:



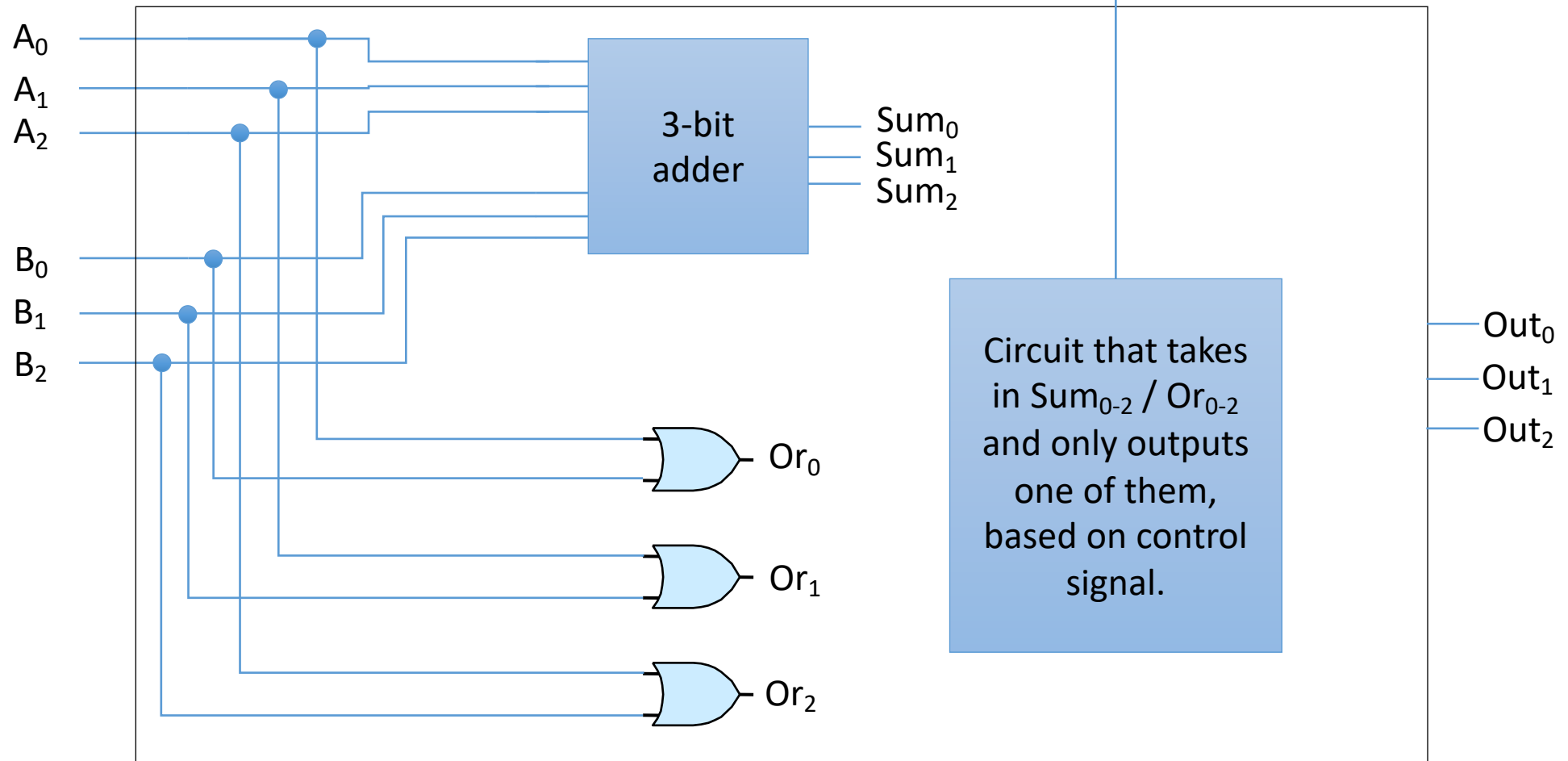
Extra input: control signal to select Sum vs. OR


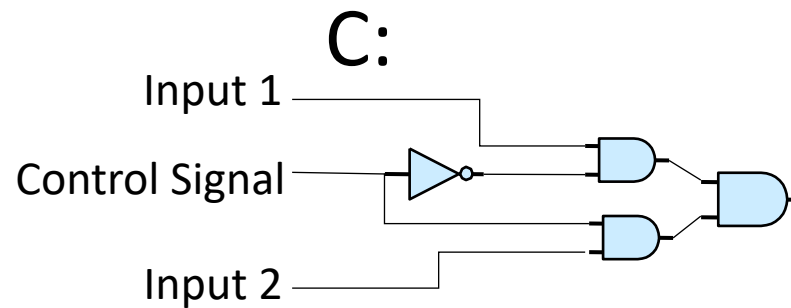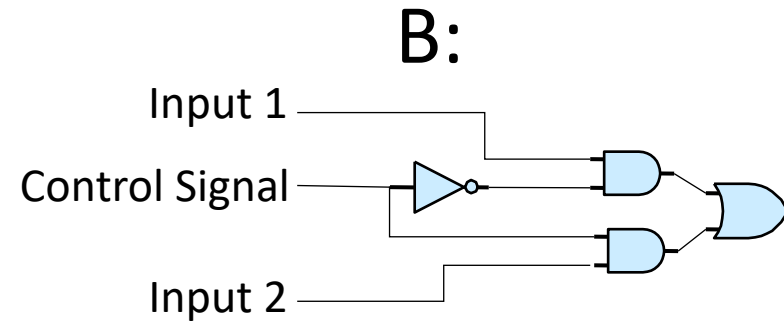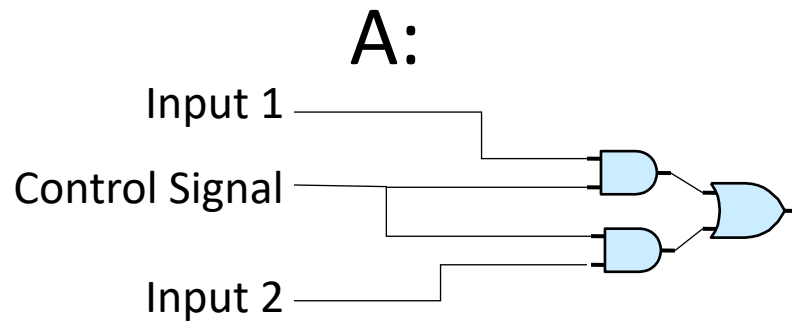
# Which of these circuits lets us select between two inputs?



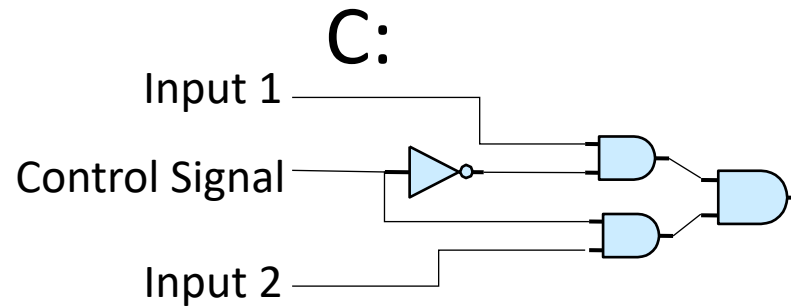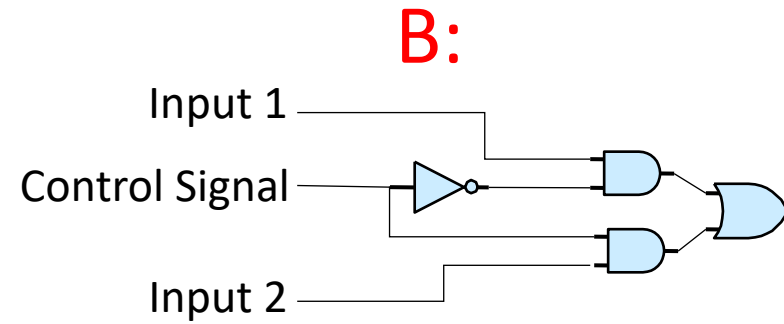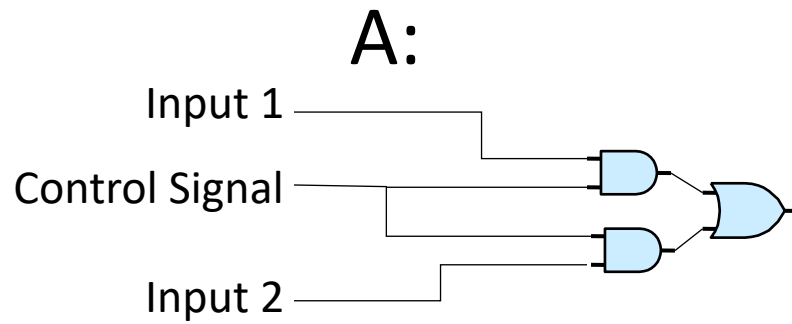
# Which of these circuits lets us select between two inputs?


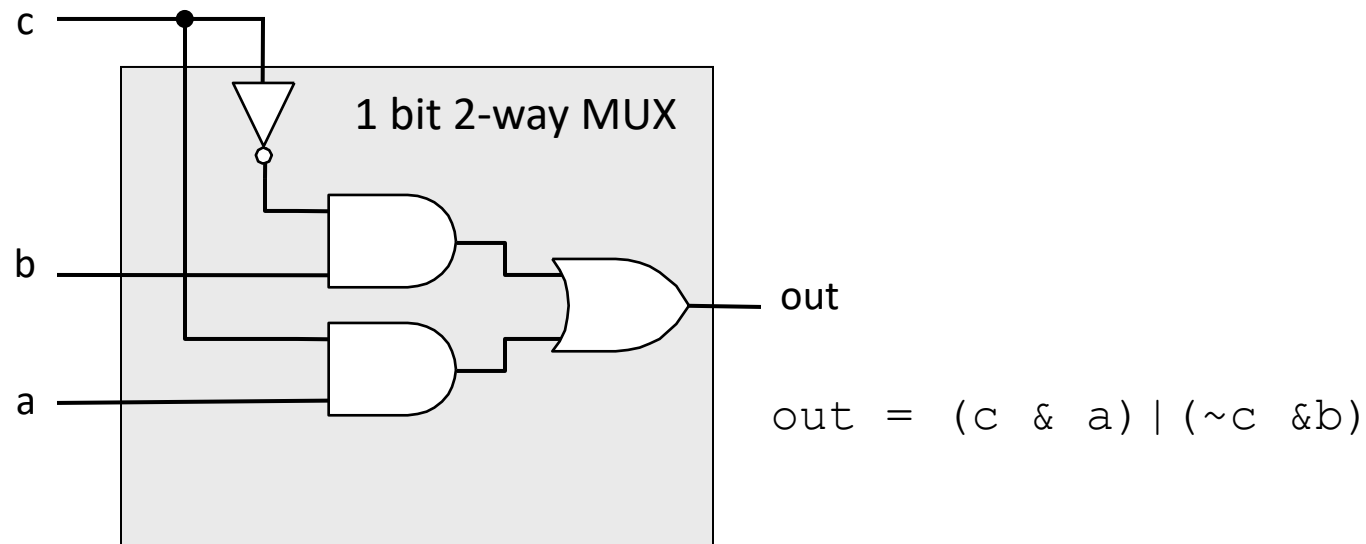
# Multiplexor: Chooses an input value

Inputs:  $2^N$  data inputs,  $N$  signal bits


Output: is one of the  $2^N$  input values




- Control signal  $c$ , chooses the input for output
  - When  $c$  is 1: choose  $a$ , when  $c$  is 0: choose  $b$
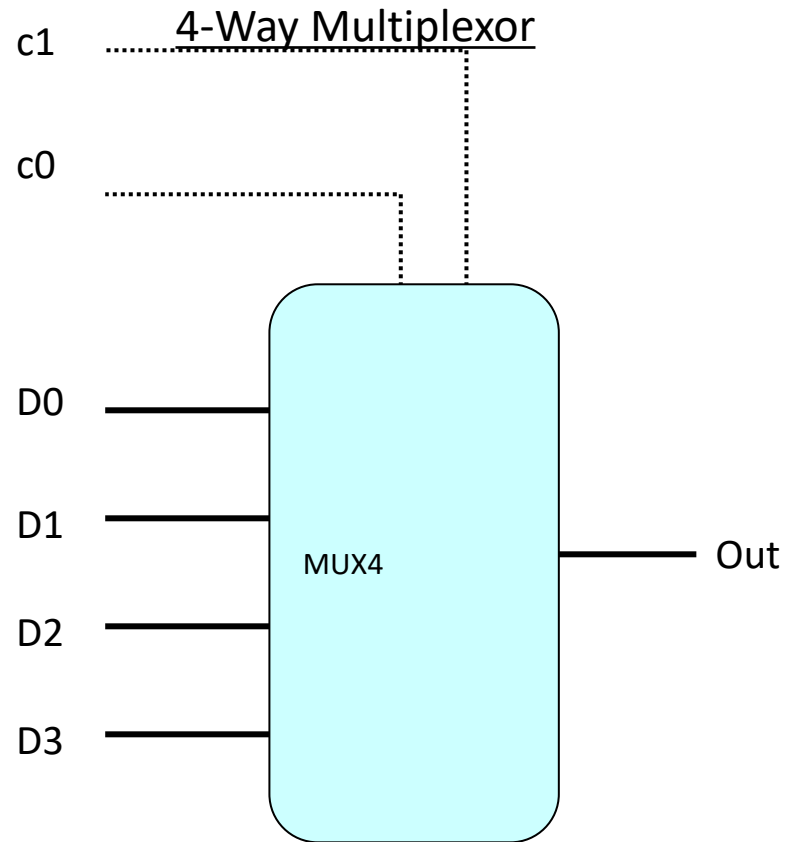
# N-Way Multiplexor

Choose one of N inputs, need  $\log_2 N$  select bits




$c_1$	$c_2$	Output
0	0	D0
0	1	D1
1	0	D2
1	1	D3

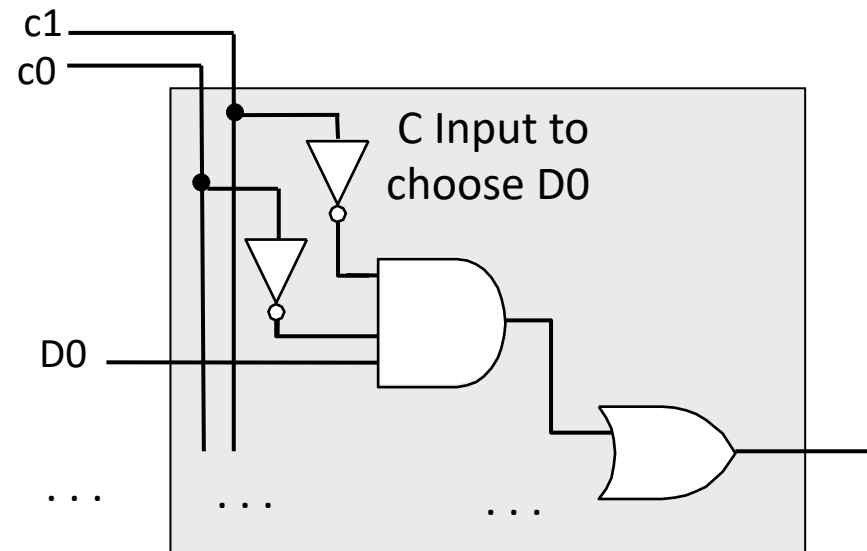

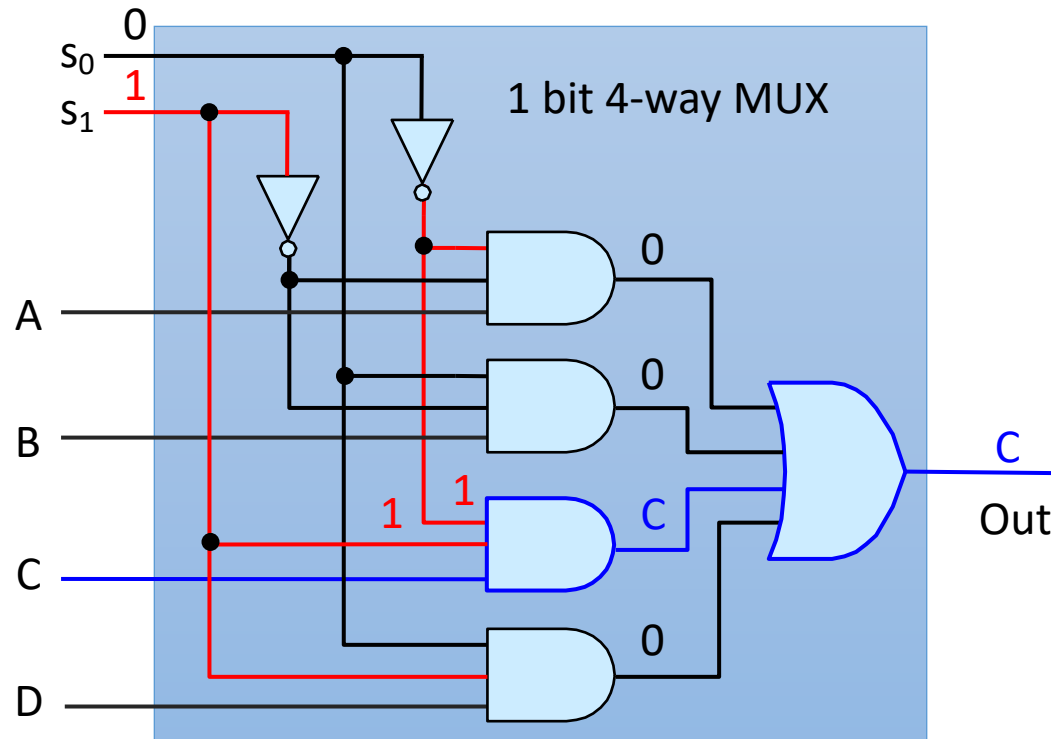
# Example 1-bit, 4-way MUX

- When select input is 2 (0b10): C chosen as output



=

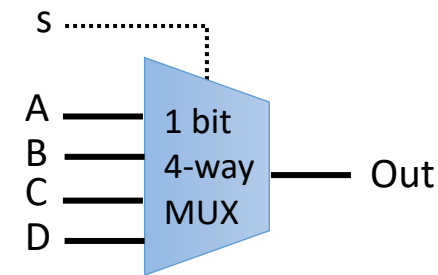


S		Out
00	0	A
01	1	B
10	2	C
11	3	D

# Simple 3-bit ALU: Add and bitwise OR

3-bit inputs


A and B:

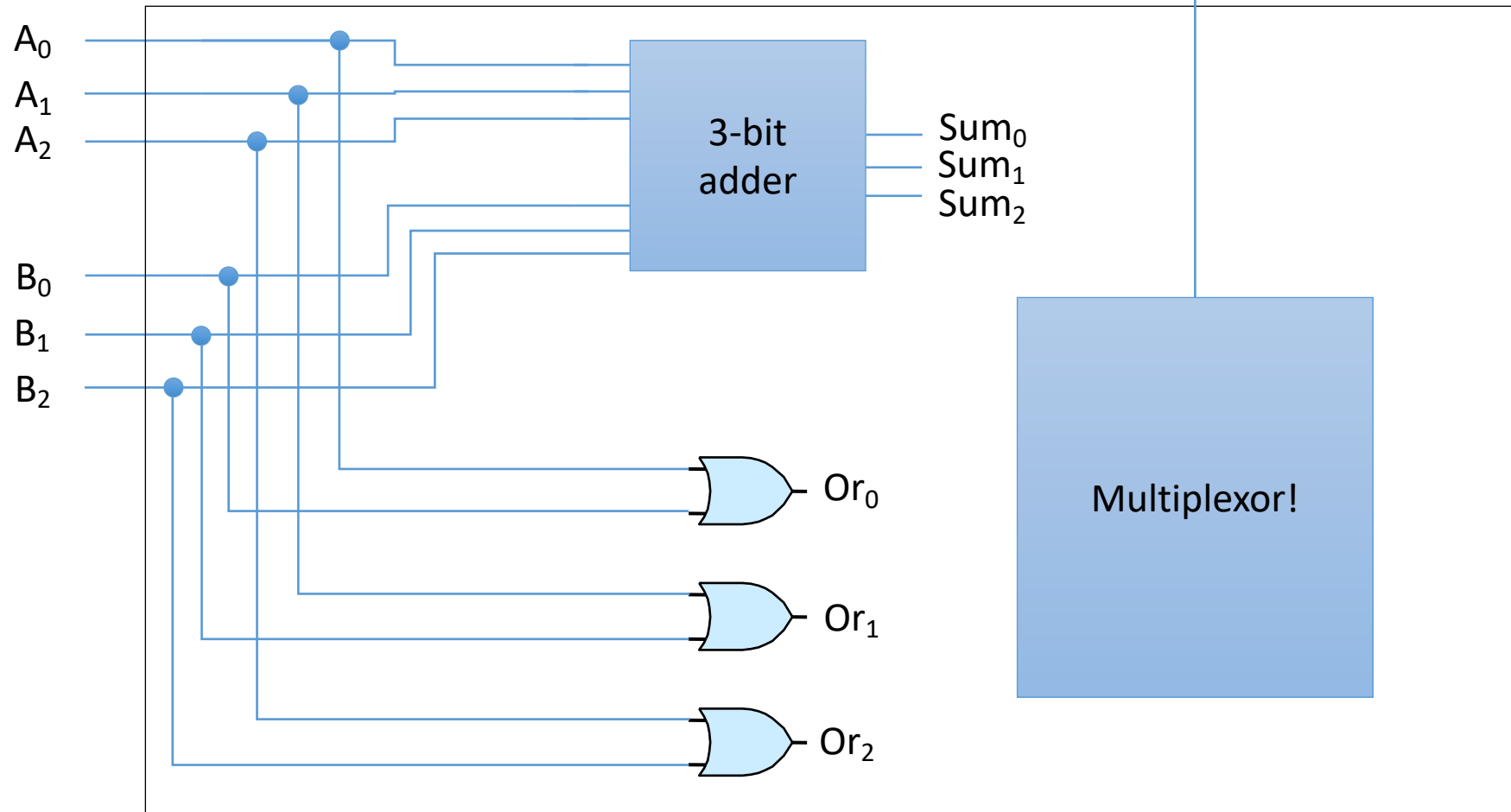Extra input: control signal to select Sum vs. OR





# ALU: Arithmetic Logic Unit

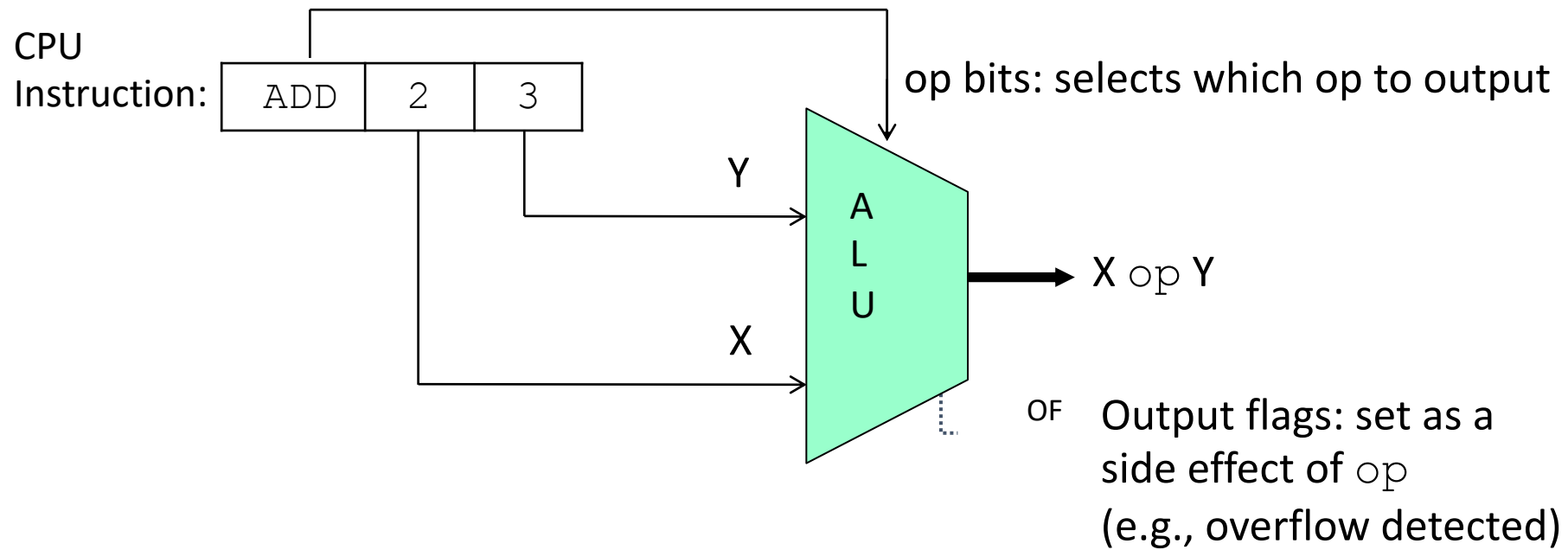


- Arithmetic and logic circuits: ADD, SUB, NOT, ...
- Control circuits: use op bits to select output
- Circuits around ALU:
  - Select input values X and Y from instruction or register
  - Select op bits from instruction to feed into ALU
  - Feed output somewhere

# Goal: Build a CPU (model)

## Three main classifications of hardware circuits:

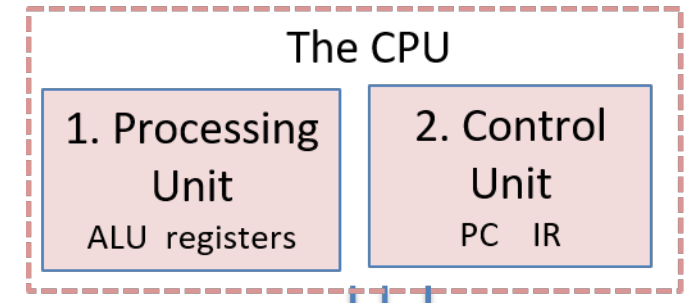1. ALU: implement arithmetic & logic functionality
  - Example: adder circuit to add two values together
2. Storage: to store binary values
  - Example: set of CPU registers (“register file”) to store temporary values
3. Control: support/coordinate instruction execution
  - Example: circuitry to fetch the next instruction from memory and decode it




# Goal: Build a CPU (model)

## Three main classifications of hardware circuits:

### 2. Storage: to store binary values

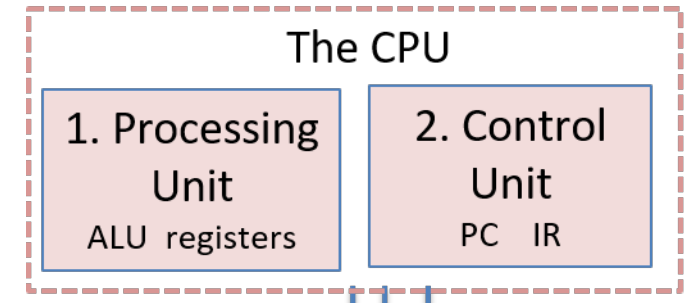
- Example: set of CPU registers (“register file”) to store temporary values

Give the CPU a “scratch space” to perform calculations and keep track of the state its in.



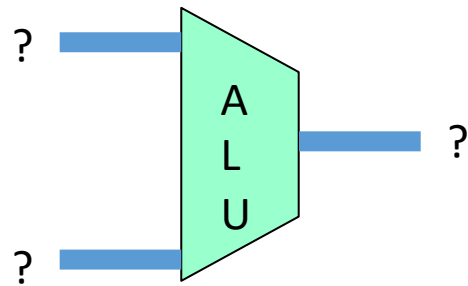
# CPU so far...

- We can perform arithmetic!
- Storage questions:
  - Where do the ALU input values come from?
  - Where do we store the result?
  - What does this “register” thing mean?



# Abstraction Towards a CPU

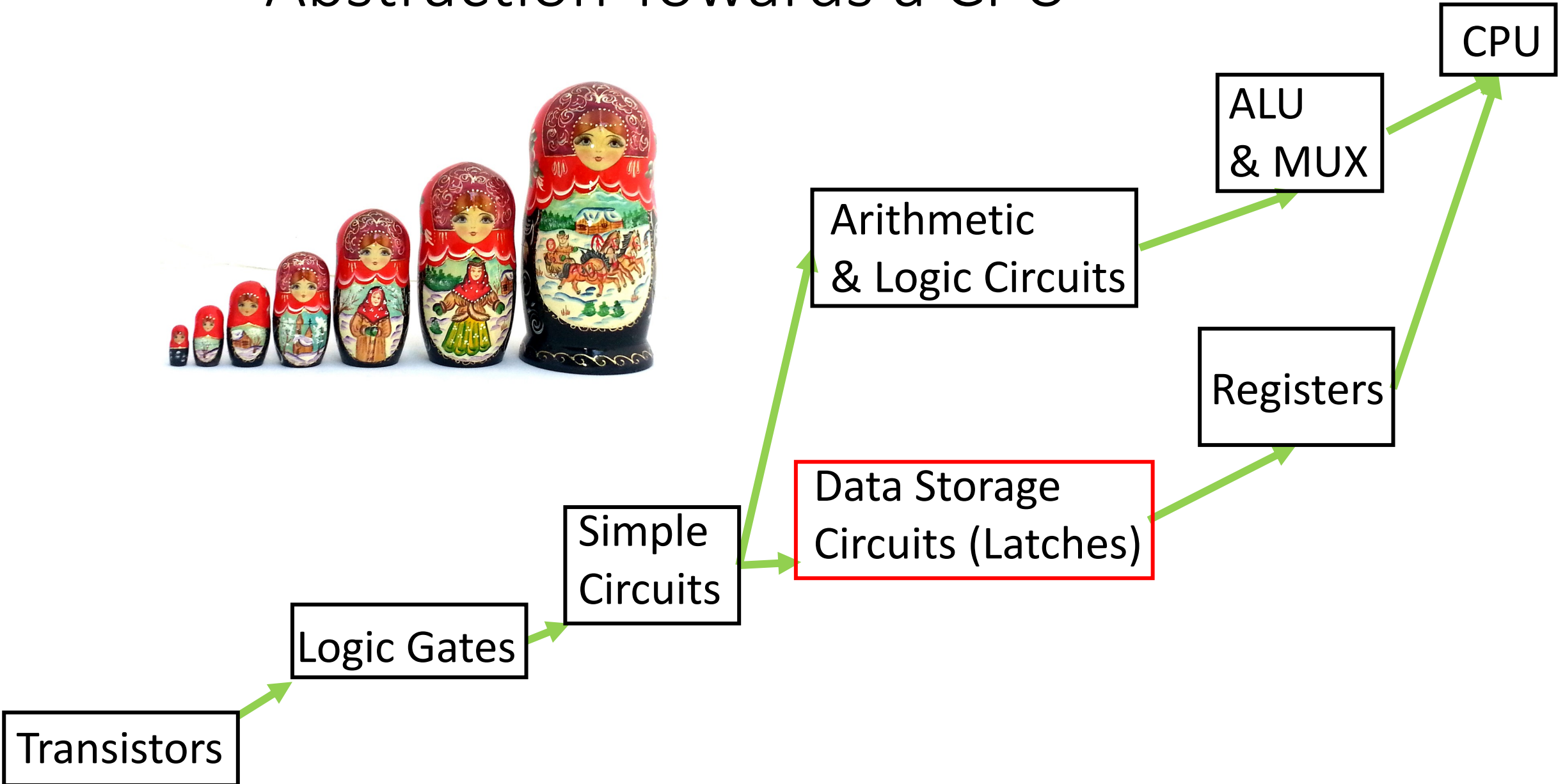


# Memory Circuit Goals: Starting Small

- Store a 0 or 1
- Retrieve the 0 or 1 value on demand (read)
- Set the 0 or 1 value on demand (write)

# R-S Latch: Stores Value Q

When R and S are both 1: Maintain a value


R and S are never both simultaneously 0

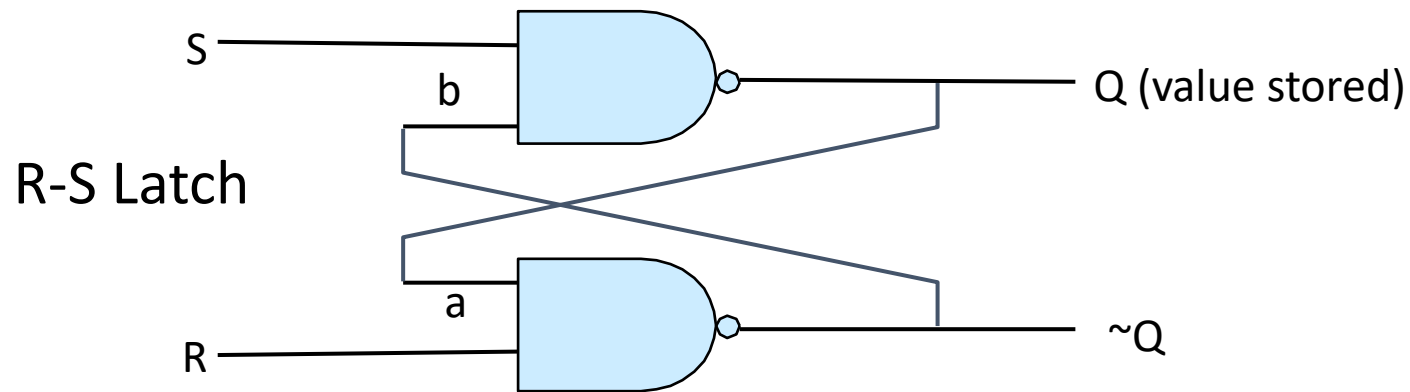

- To write a new value:
  - Set S to 0 momentarily (R stays at 1): to write a 1
  - Set R to 0 momentarily (S stays at 1): to write a 0
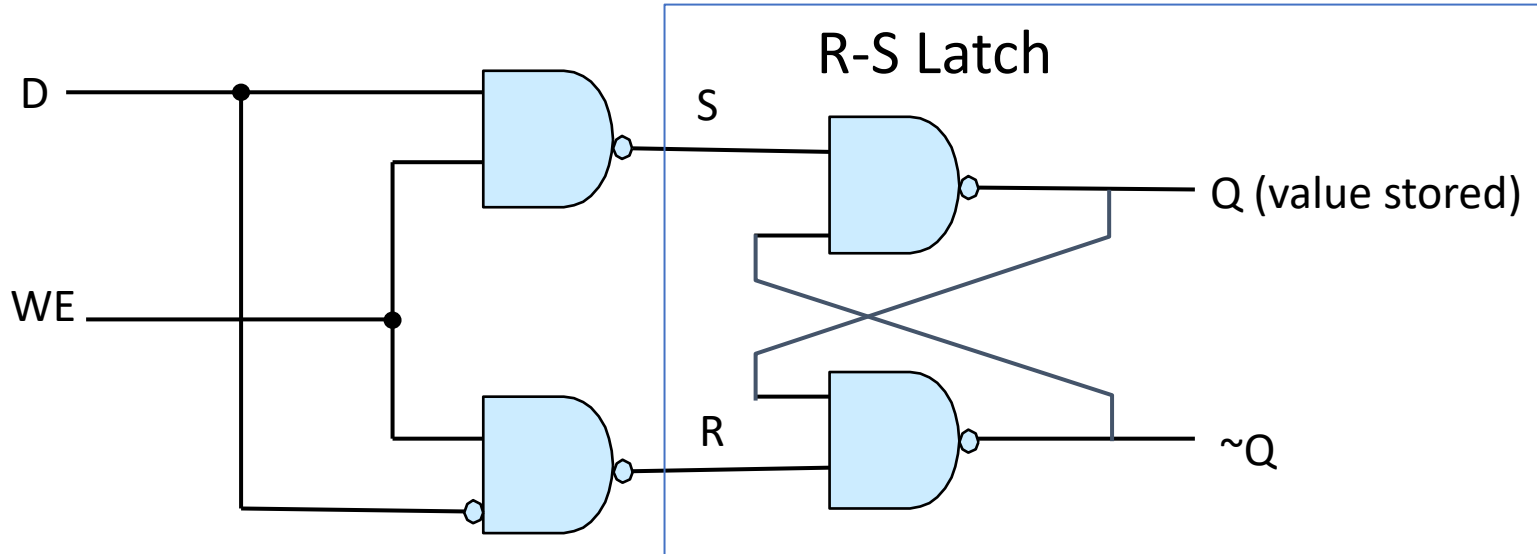
# Gated D Latch

Controls S-R latch writing, ensures S & R never both 0




D: into top NAND,  $\sim$ D into bottom NAND

WE: write-enabled, when set, latch is set to value of D

Latches used in registers (up next) and SRAM (caches, later)

Fast, not very dense, expensive


DRAM: capacitor-based:

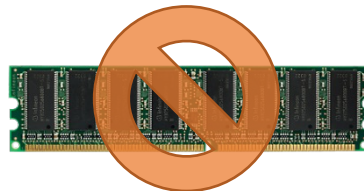



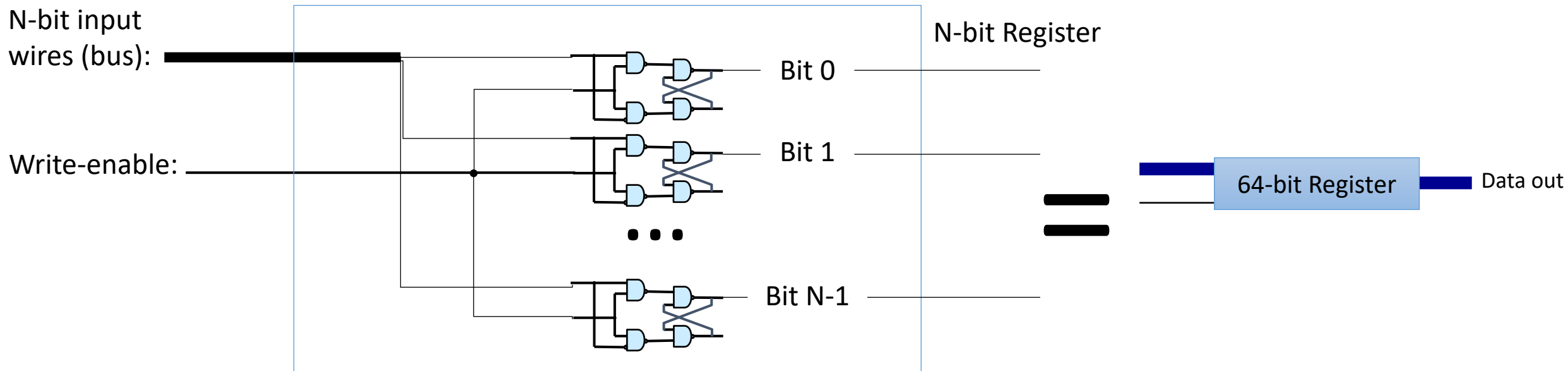
# An N-bit Register

- Fixed-size storage (8-bit, 32-bit, 64-bit, etc.)
- Gated D latch lets us store one bit
  - Connect N of them to the same write-enable wire!



# Abstraction Towards a CPU

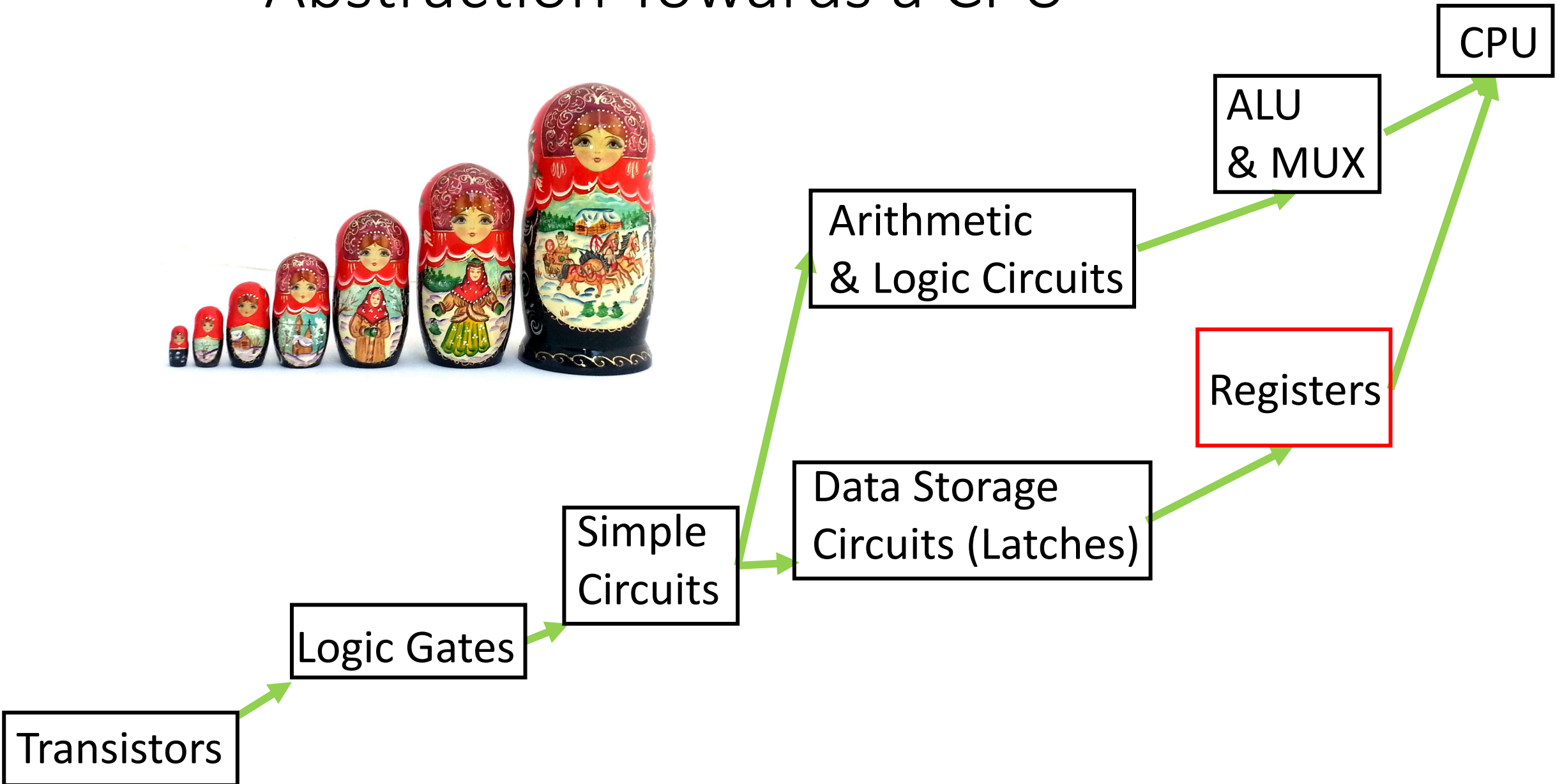


# “Register file”

- A set of registers for the CPU to store temporary values.

- This is (finally) something you will interact with!

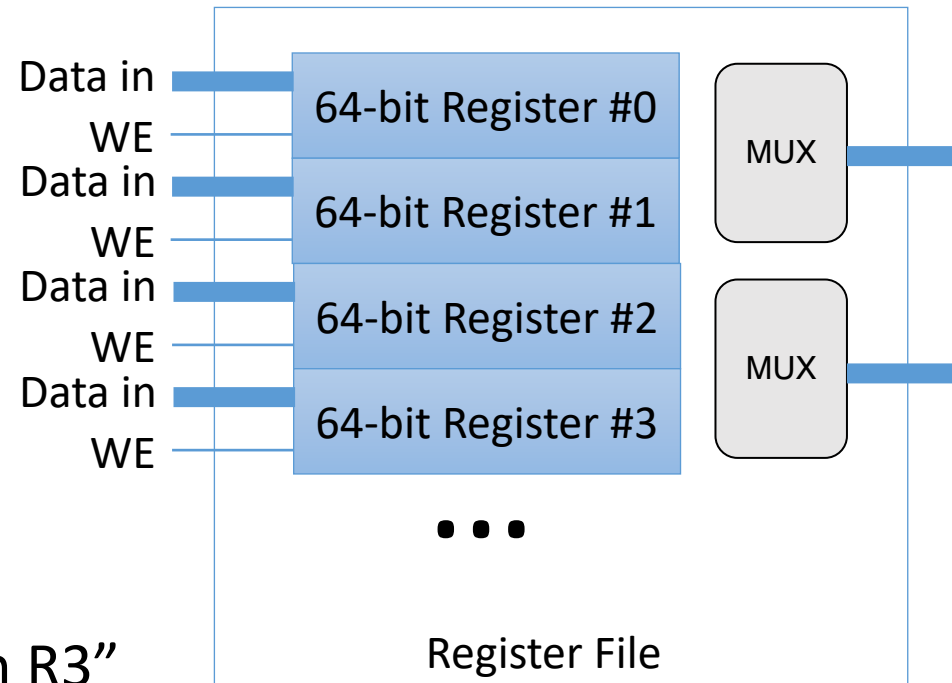- Instructions of form:
  - “add R1 + R2, store result in R3”



# Memory Circuit Summary

- Lots of abstraction going on here!
  - Gates hide the details of transistors.
  - Build R-S Latches out of gates to store one bit.
  - Combining multiple latches gives us N-bit register.
  - Grouping N-bit registers gives us register file.
- Register file's simple interface:
  - Read  $R_x$ 's value, use for calculation
  - Write  $R_y$ 's value to store result

# CPU so far...

We know how to store data (in register file).

We know how to perform arithmetic on it, by feeding it to ALU.


Remaining questions:

Which register(s) do we use as input to ALU?

Which operation should the ALU perform?

To which register should we store the result?

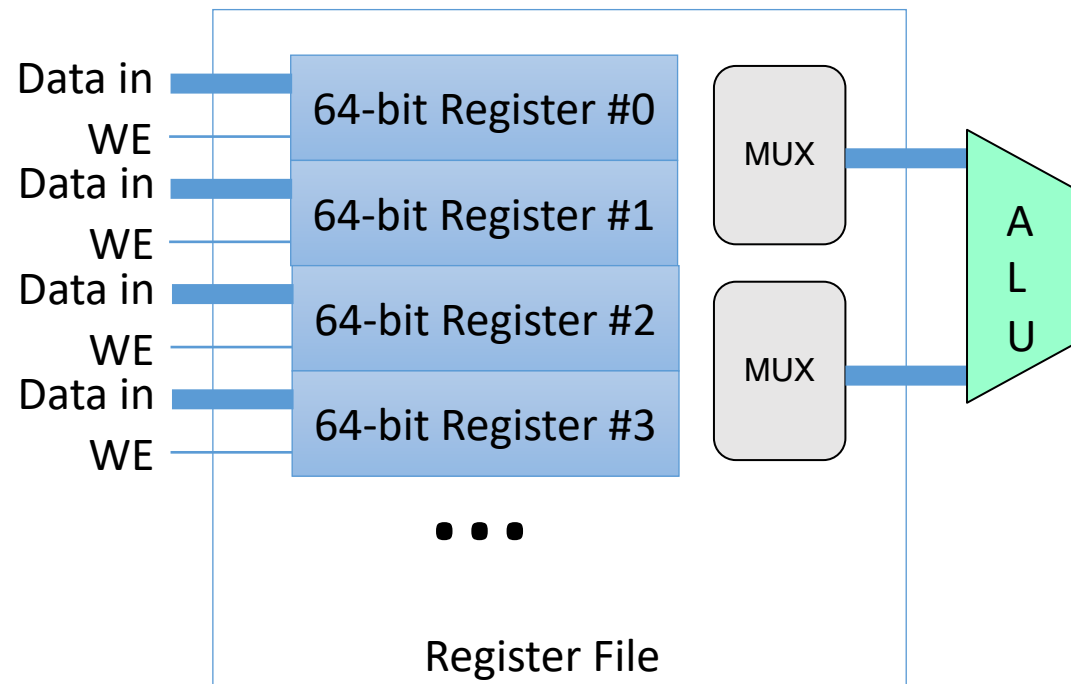
All this info comes from  
our program:  
a series of instructions.



# Goal: Build a CPU (model)

## Three main classifications of hardware circuits:

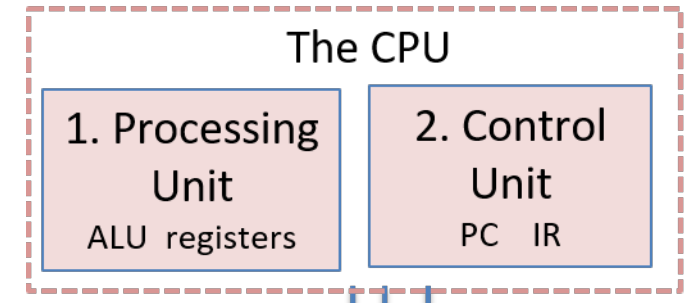1. ALU: implement arithmetic & logic functionality
  - Example: adder circuit to add two values together
2. Storage: to store binary values
  - Example: set of CPU registers (“register file”) to store temporary values
3. Control: support/coordinate instruction execution
  - Example: circuitry to fetch the next instruction from memory and decode it



# Goal: Build a CPU (model)


## Three main classifications of hardware circuits:

### 3. Control: support/coordinate instruction execution

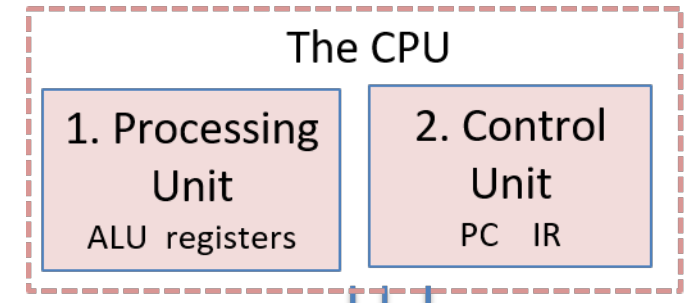
- Example: circuitry to fetch the next instruction from memory and decode it

Keep track of where we are in the program.

Execute an instruction, move on to the next...



# Recall: Von Neumann Model

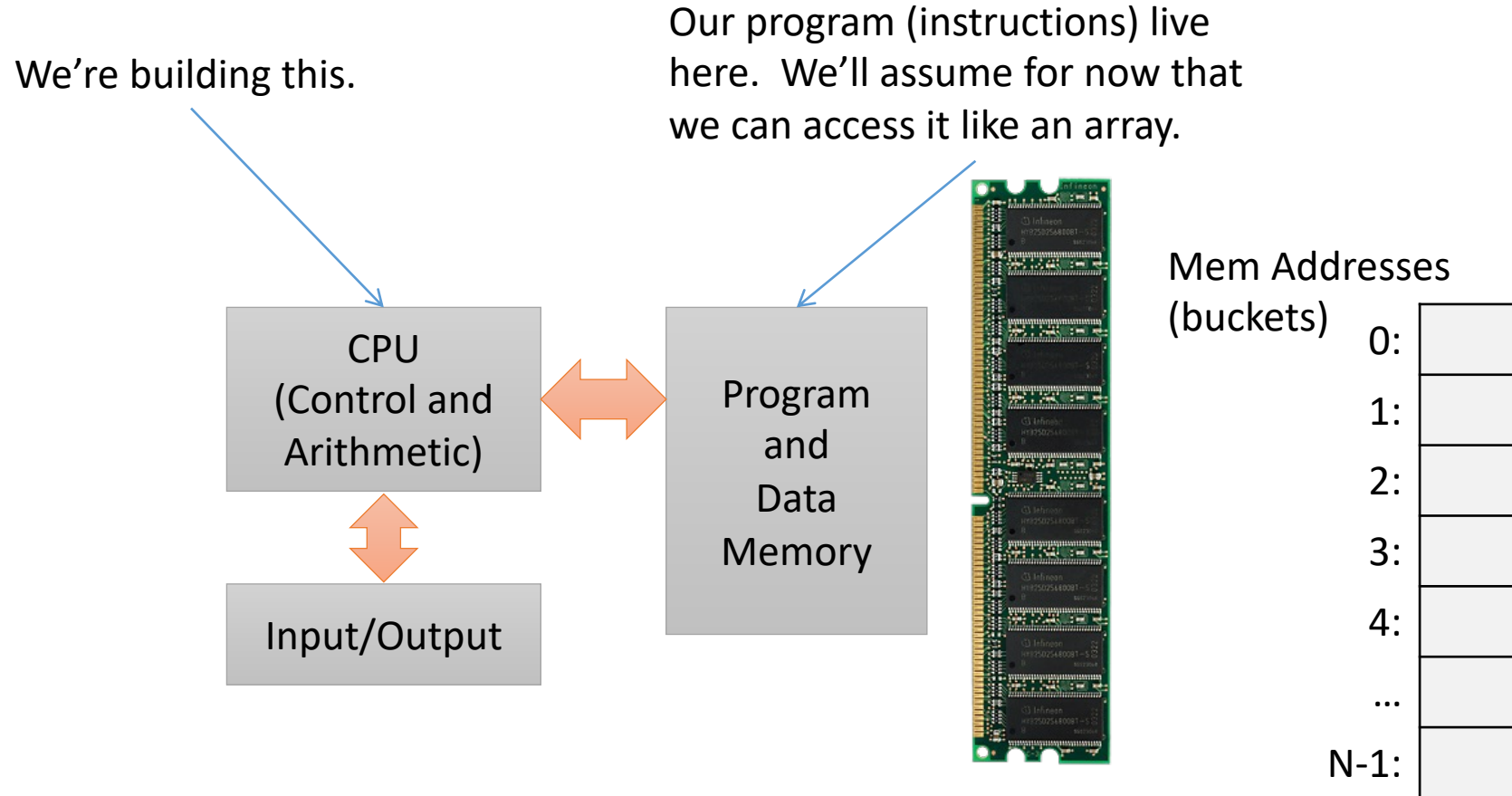



# CPU Game Plan



- **Fetch** instruction from memory
- **Decode** what the instruction is telling us to do
  - Tell the ALU what it should be doing
  - Find the correct operands
- **Execute** the instruction (arithmetic, etc.)
- **Store** the result

# Program State

Let's add **two more special registers** (not in register file) to keep track of the program.

**Program Counter (PC):** Memory address of next instr

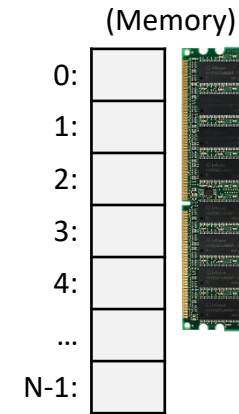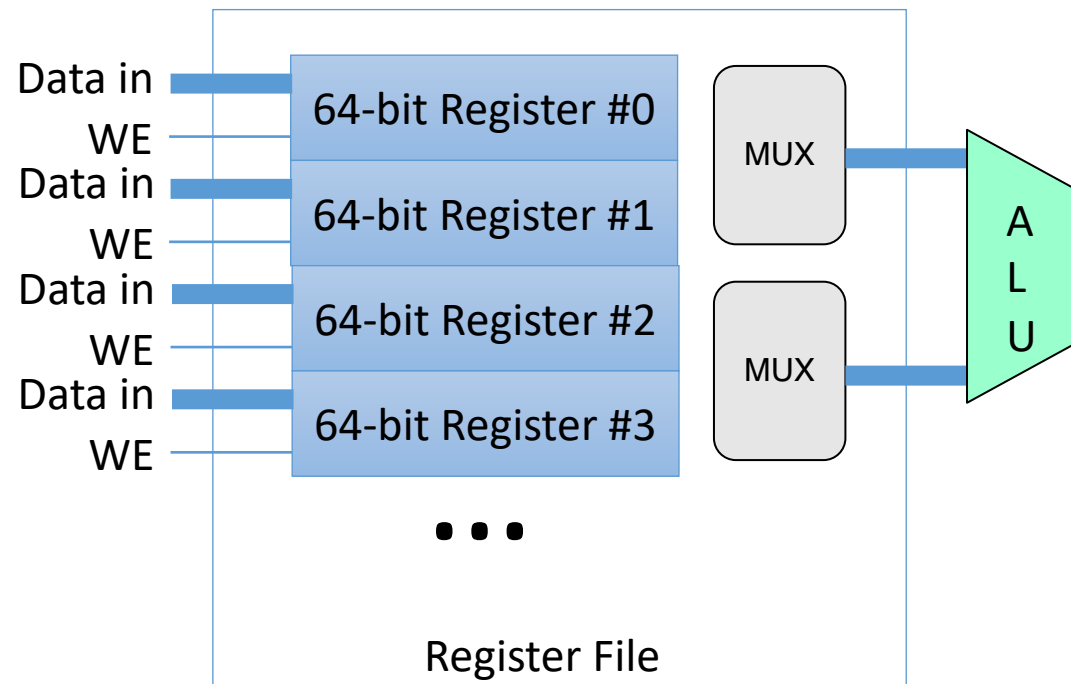**Instruction Register (IR):** Instruction contents (bits)



# To Recap:

- OR, AND, NOT, XOR gates
- Boolean expressions
- 1-N-bit adders
- 2-N-way multiplexors (MUXs not... MUK)
- ALUs
- Registers



# Your TODO List

- **HW2, Lab 2**
- **The next 11 weeks:** Read the readings before class

# Fetching instructions.



Load IR with the contents of memory at the address stored in the PC.

**Program Counter (PC):**

**Address 0**

**Instruction Register (IR):**

**Instruction at Address 0**

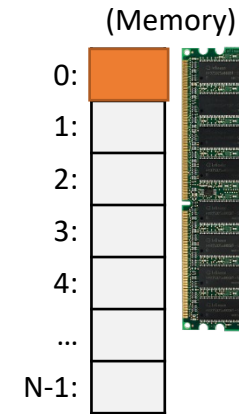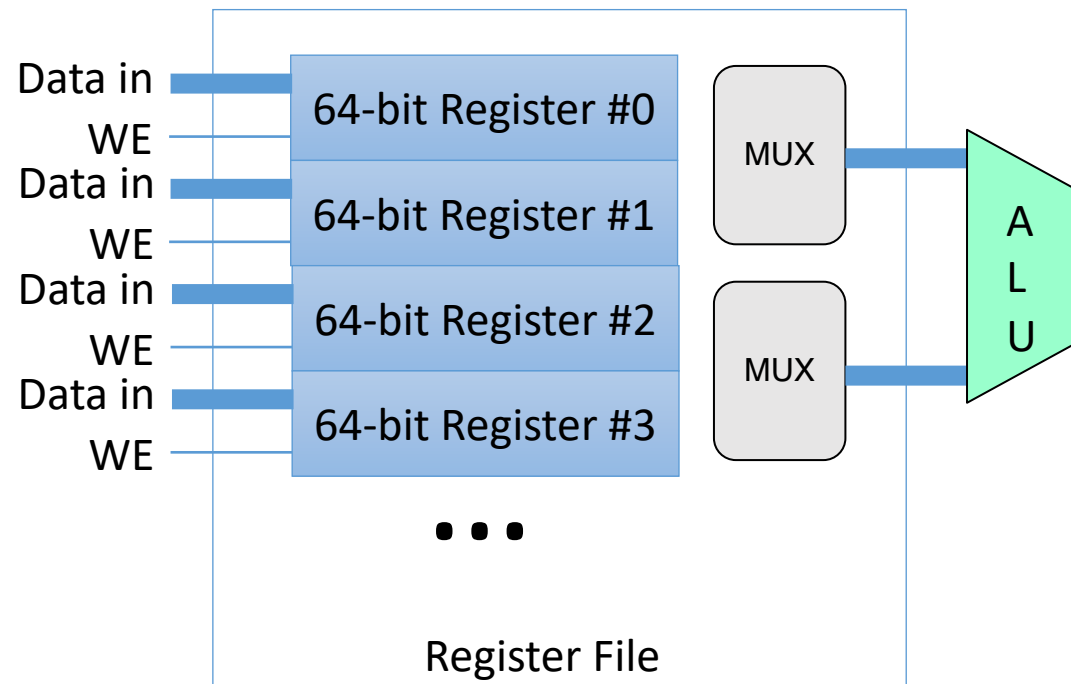

# Decoding instructions.



Interpret the instruction bits: What operation? Which arguments?

**Program Counter (PC):**

**Address 0**


**Instruction Register (IR):**

OP Code | Reg A | Reg B | Result

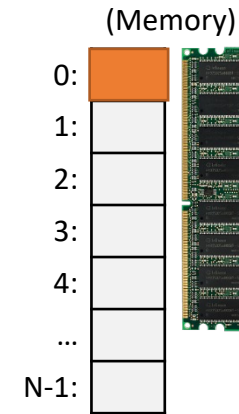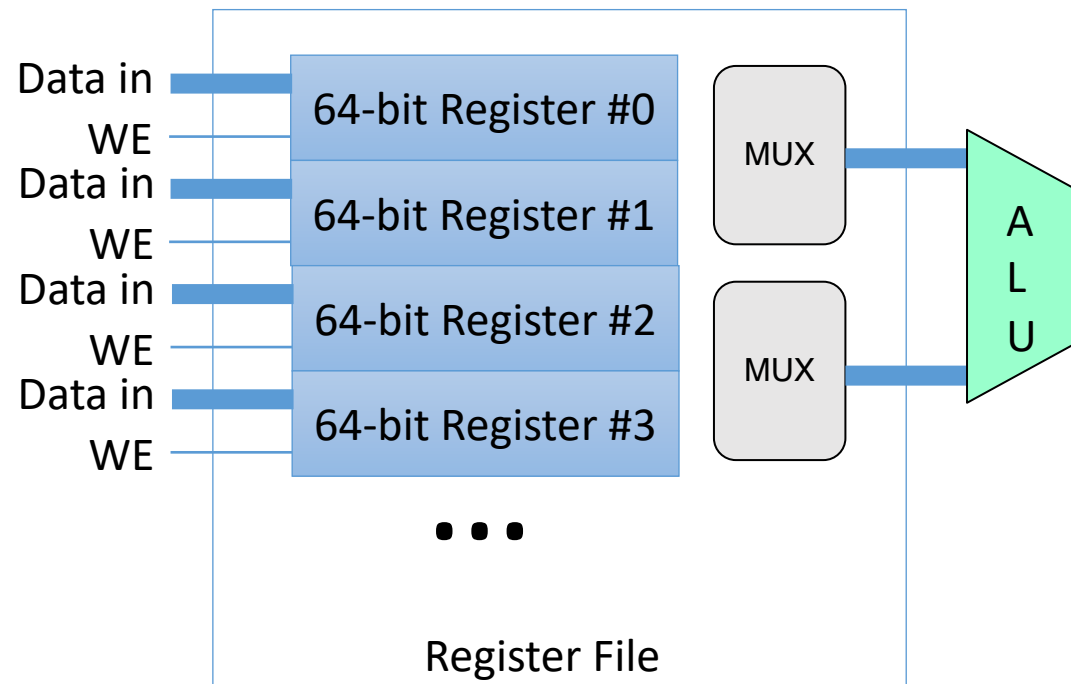

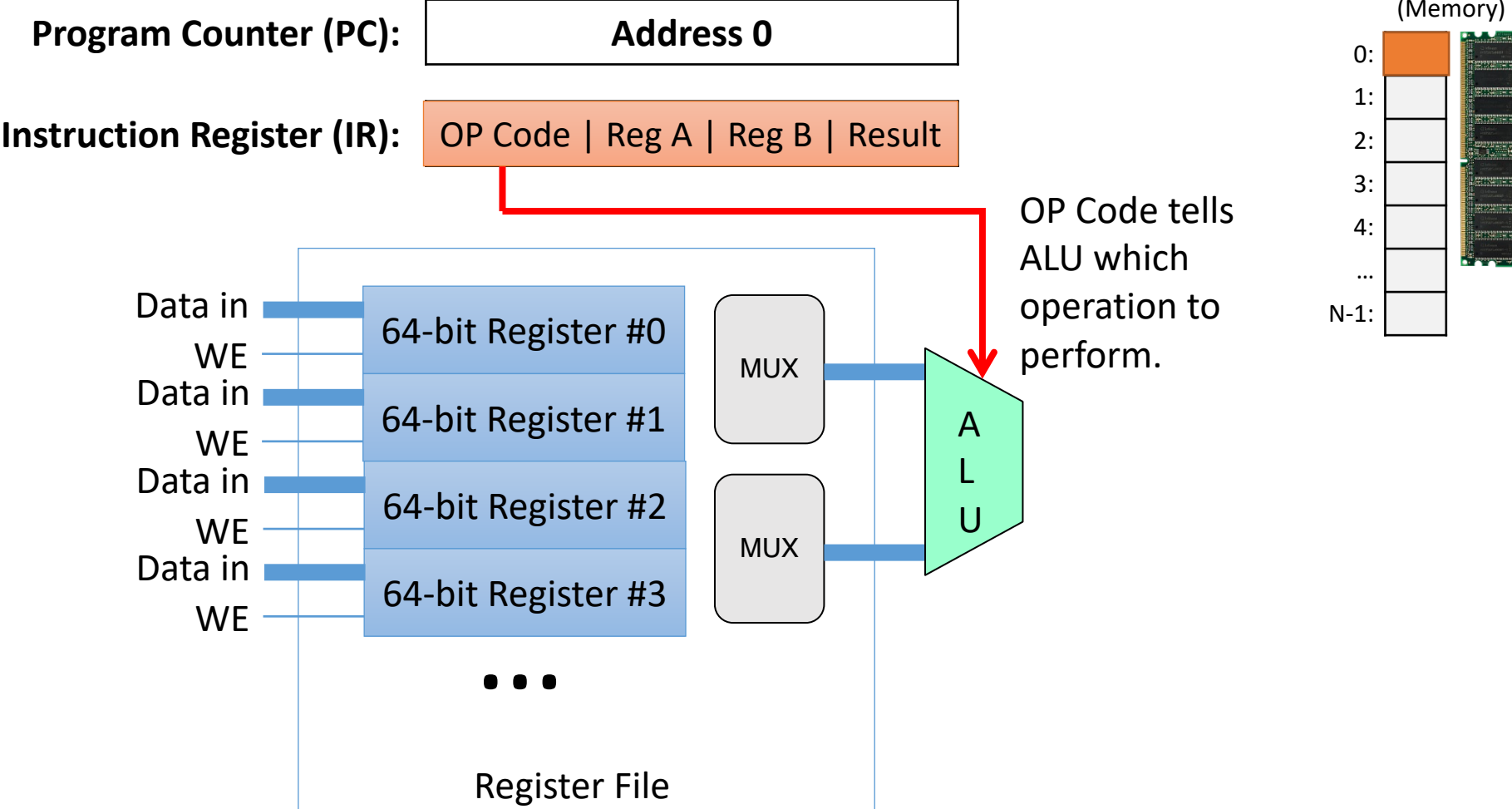
# Decoding instructions.

Interpret the instruction bits: What operation? Which arguments?


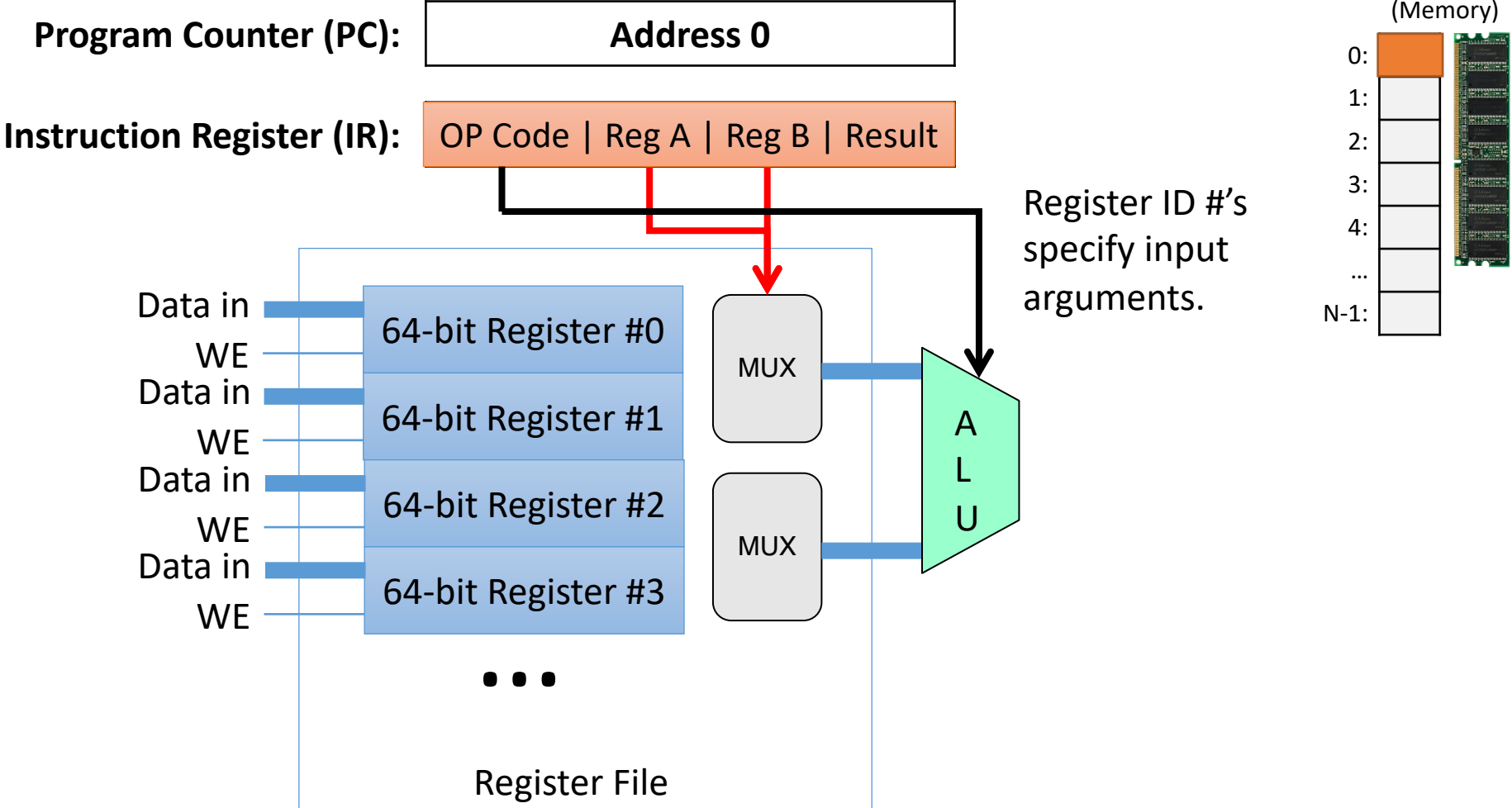
# Decoding instructions.


Interpret the instruction bits: What operation? Which arguments?





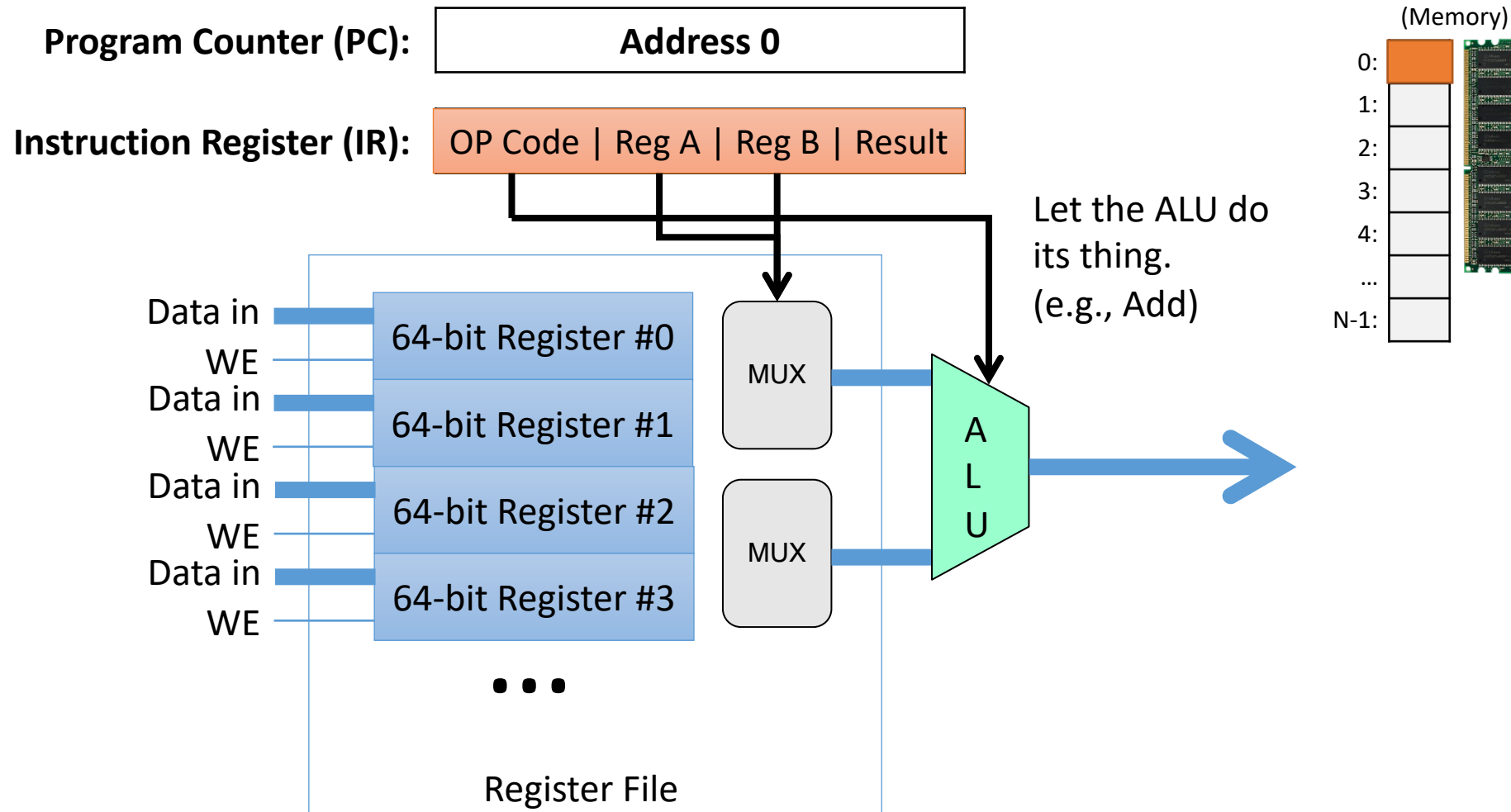
# Executing instructions.

Interpret the instruction bits: What operation? Which arguments?



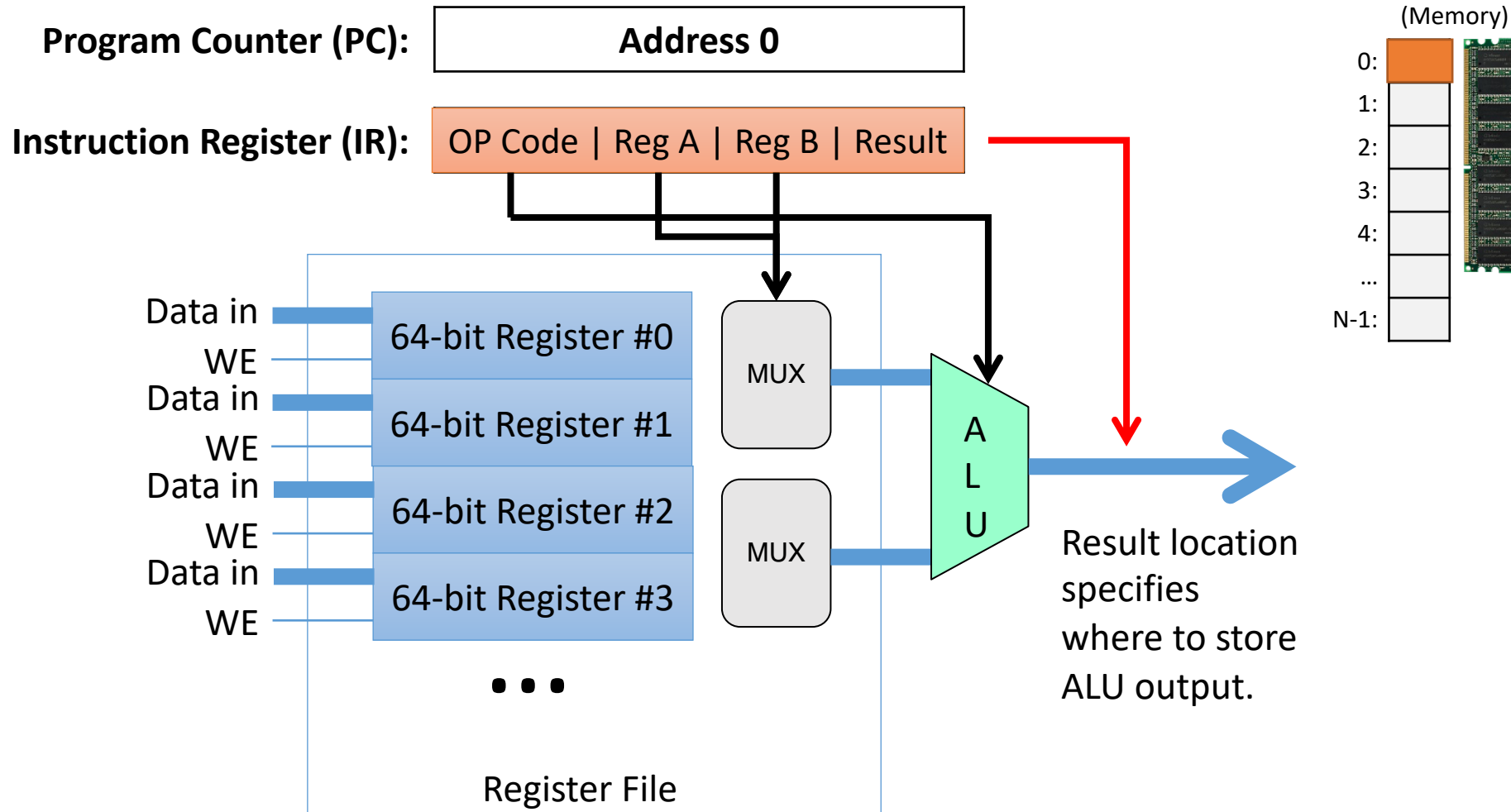
# Storing results.

We've just computed something. Where do we put it?


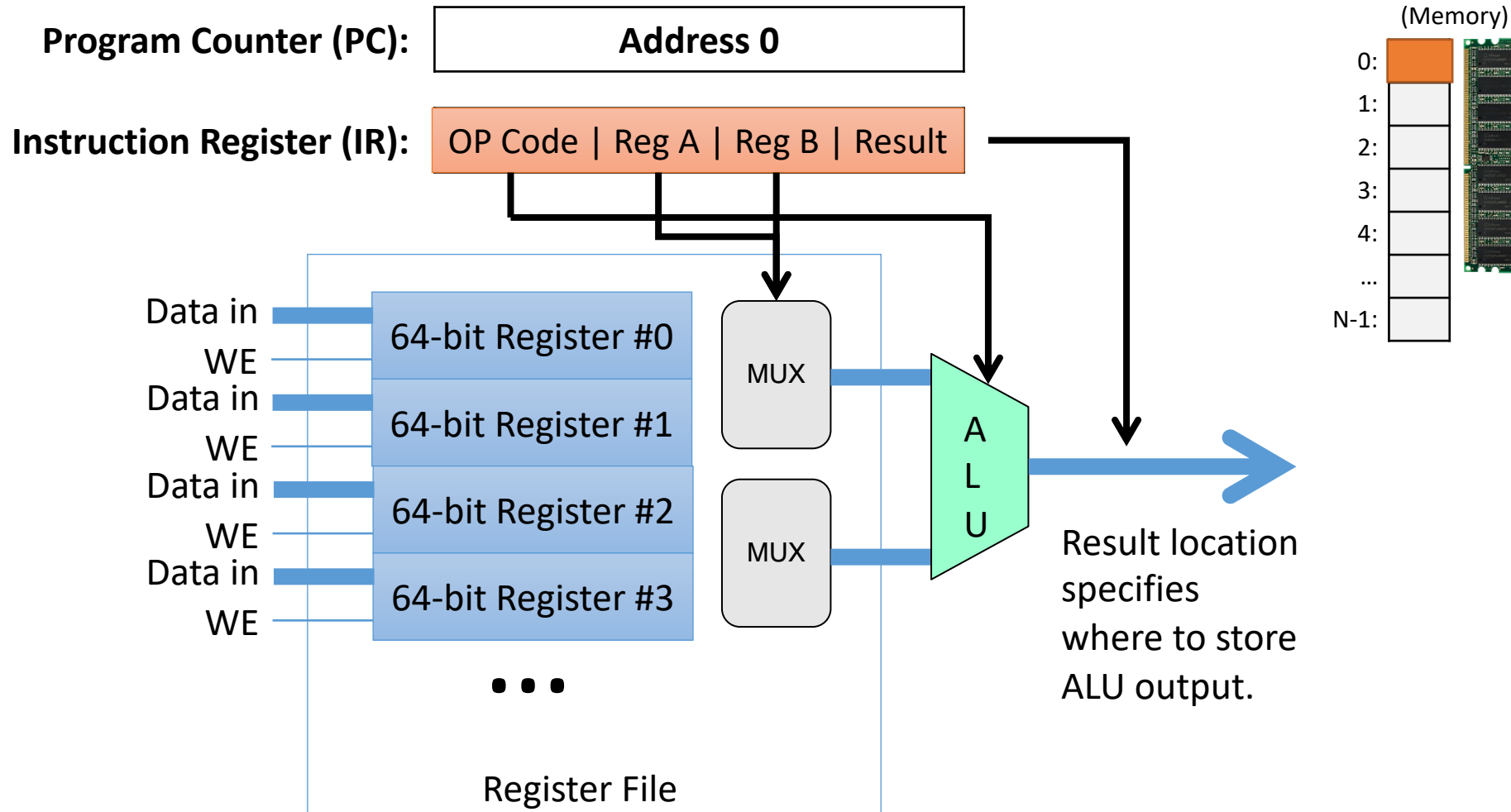
# Questions so far?

We've just computed something. Where do we put it?



Why do we need a program counter? Can't we just start executing instruction at address 0 and count up one at a time from there?


- A. We don't, it's there for convenience.
- B. Some instructions might skip the PC forward by more than one.
- C. Some instructions might adjust the PC backwards.
- D. We need the PC for some other reason(s).

Why do we need a program counter? Can't we just start executing instruction at address 0 and count up one at a time from there?

- A. We don't, it's there for convenience.
- B. Some instructions might skip the PC forward by more than one.
- C. Some instructions might adjust the PC backwards.
- D. We need the PC for some other reason(s).
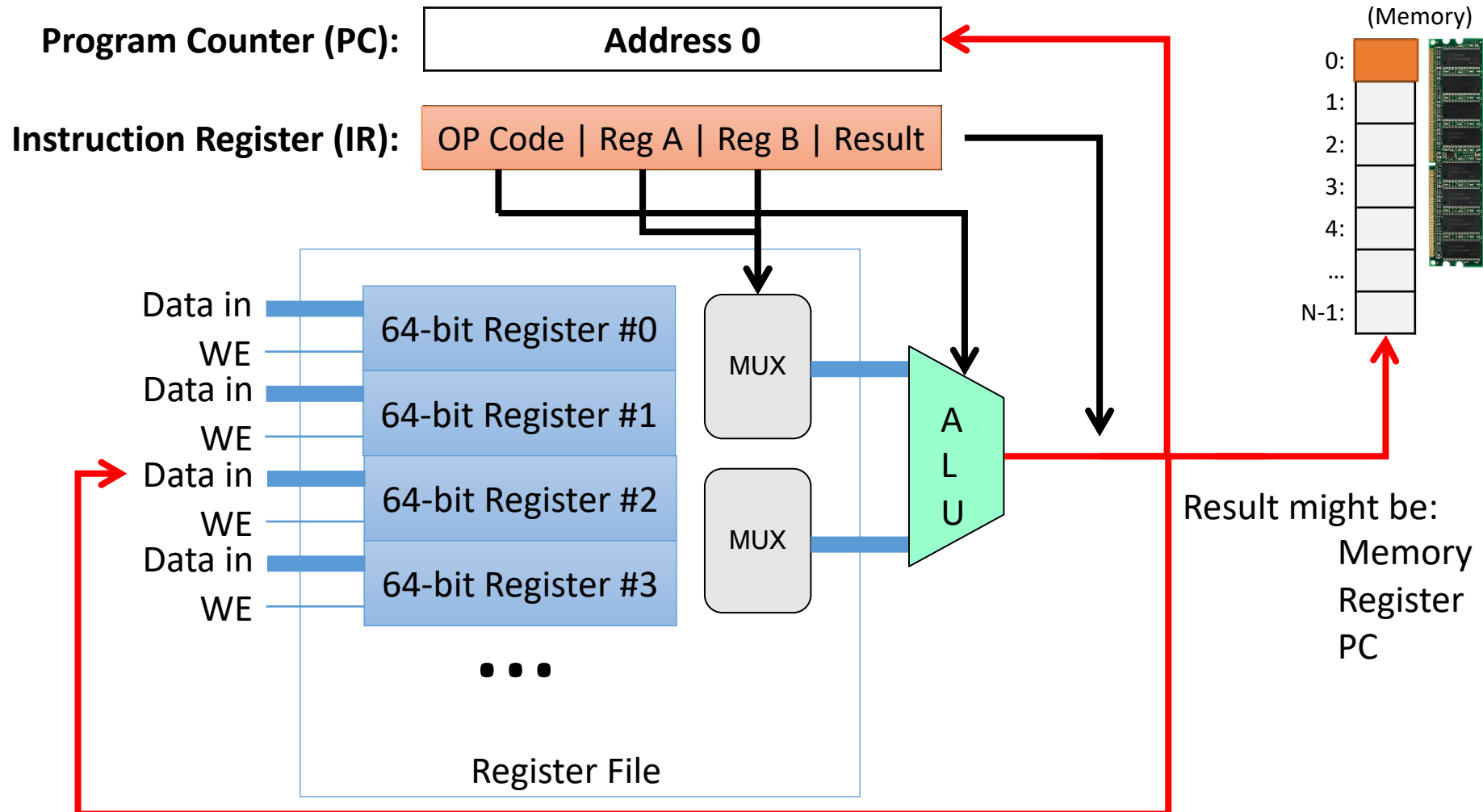
# Storing results.

Interpret the instruction bits: What operation? Which arguments?





# Recap CPU Model

Four stages: fetch instruction, decode instruction, execute, store result

**Program Counter (PC):** Memory address of next instr

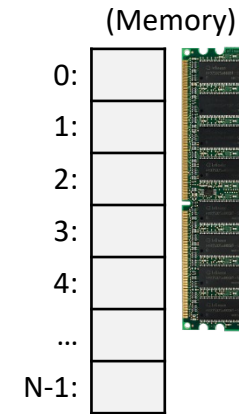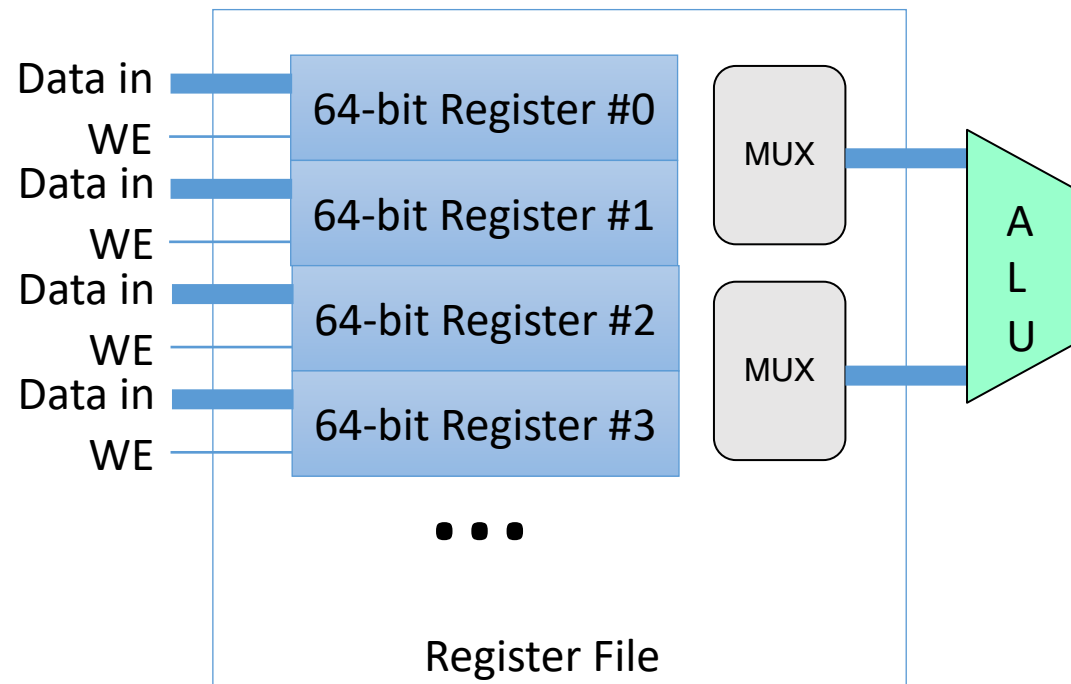**Instruction Register (IR):** Instruction contents (bits)



# Fetching instructions.



Load IR with the contents of memory at the address stored in the PC.

**Program Counter (PC):**

**Address 0**

**Instruction Register (IR):**

**Instruction at Address 0**

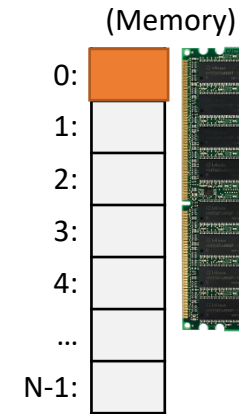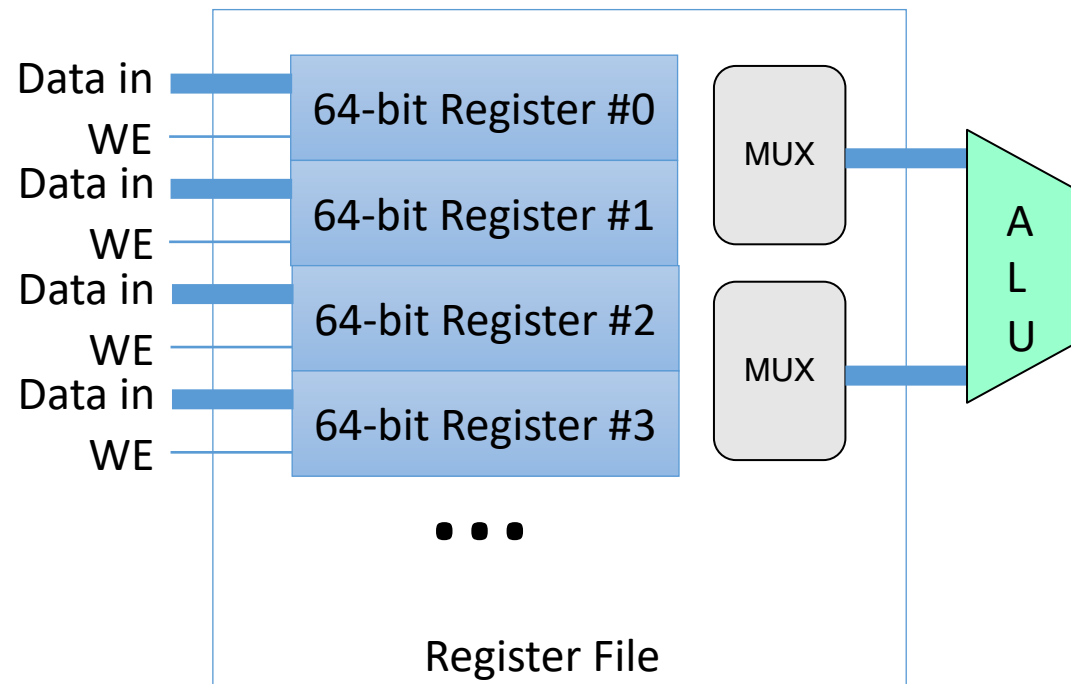



# Decoding instructions.



Interpret the instruction bits: What operation? Which arguments?

**Program Counter (PC):**

**Address 0**


**Instruction Register (IR):**

OP Code | Reg A | Reg B | Result

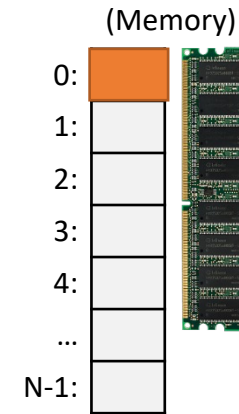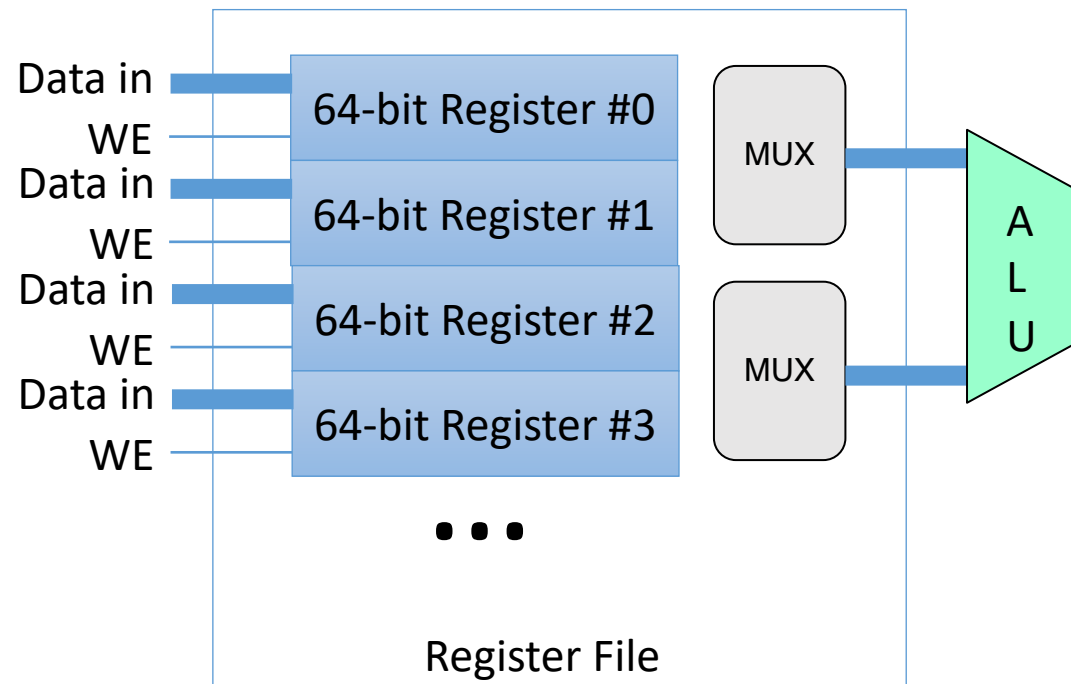

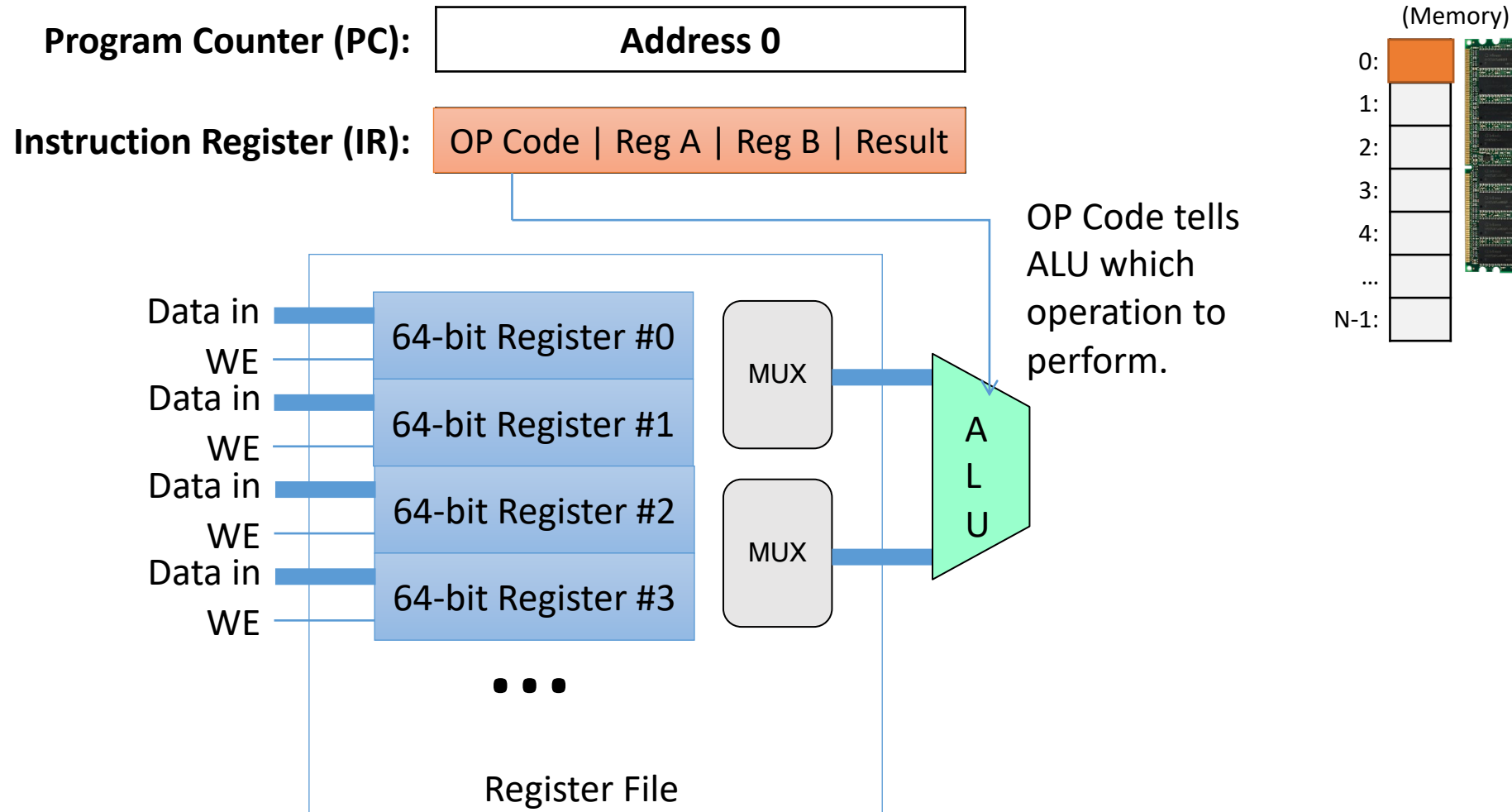
# Decoding instructions.

Interpret the instruction bits: What operation? Which arguments?



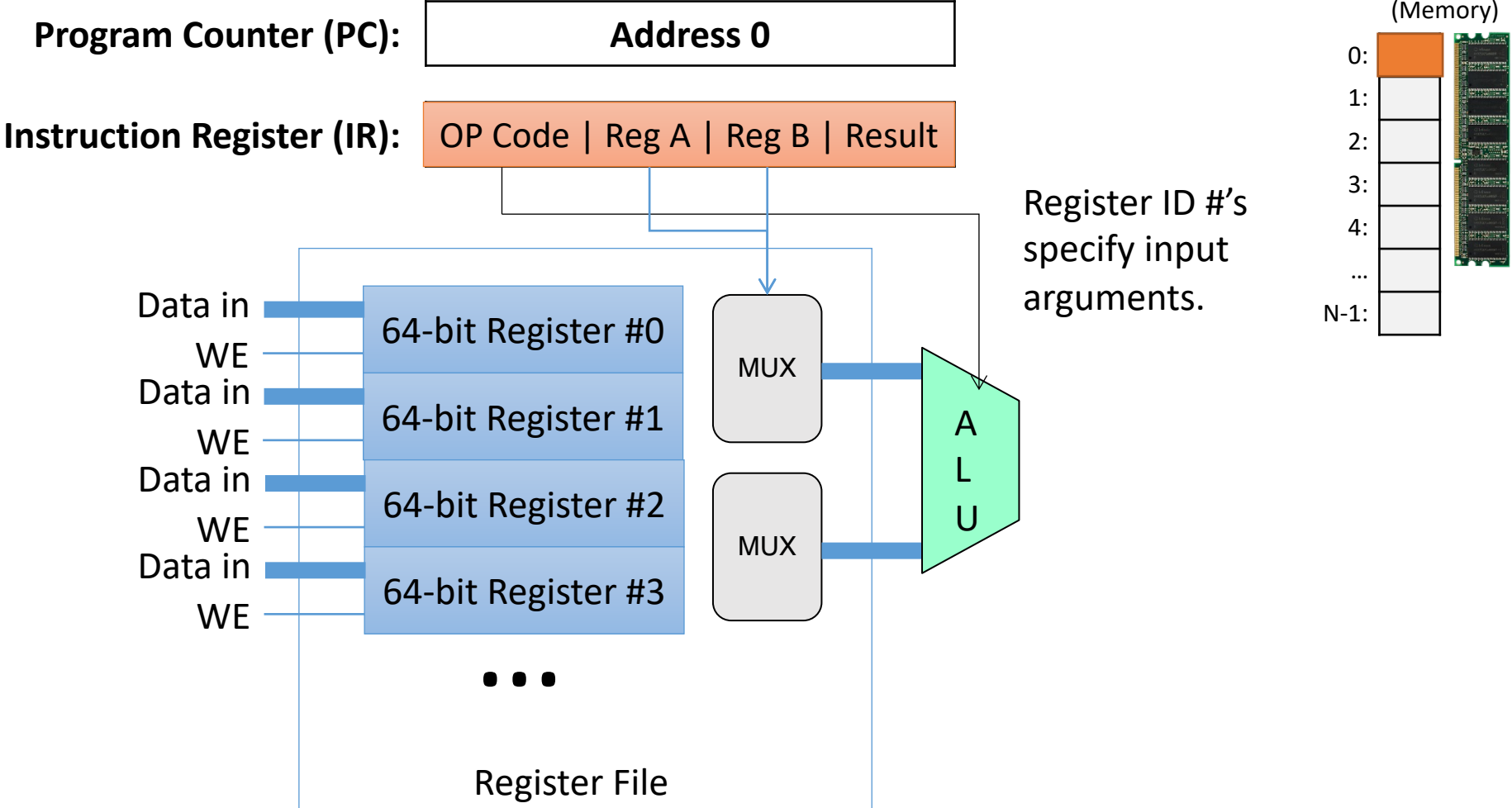
# Decoding instructions.

Interpret the instruction bits: What operation? Which arguments?



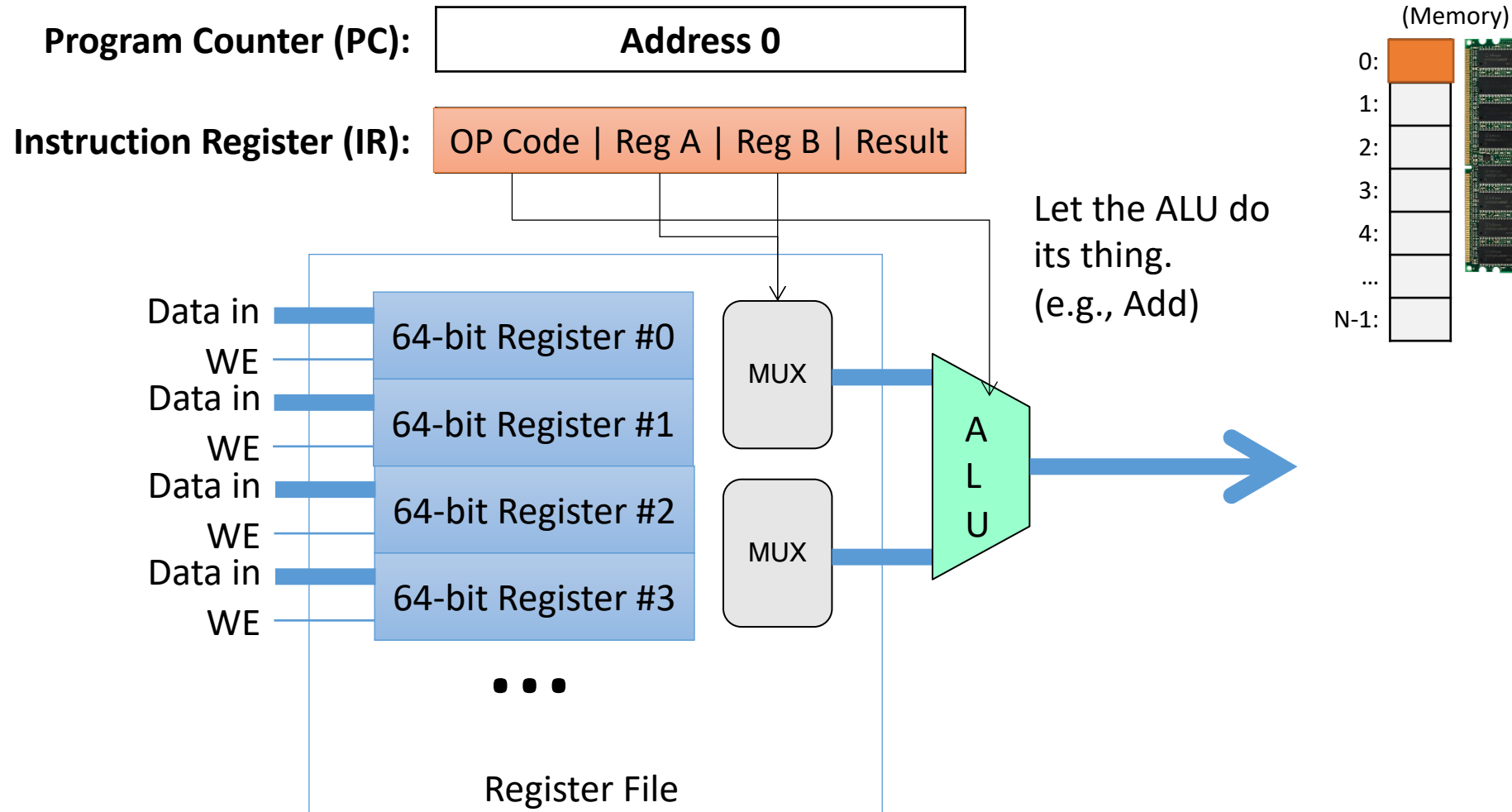
# Executing instructions.

Interpret the instruction bits: What operation? Which arguments?


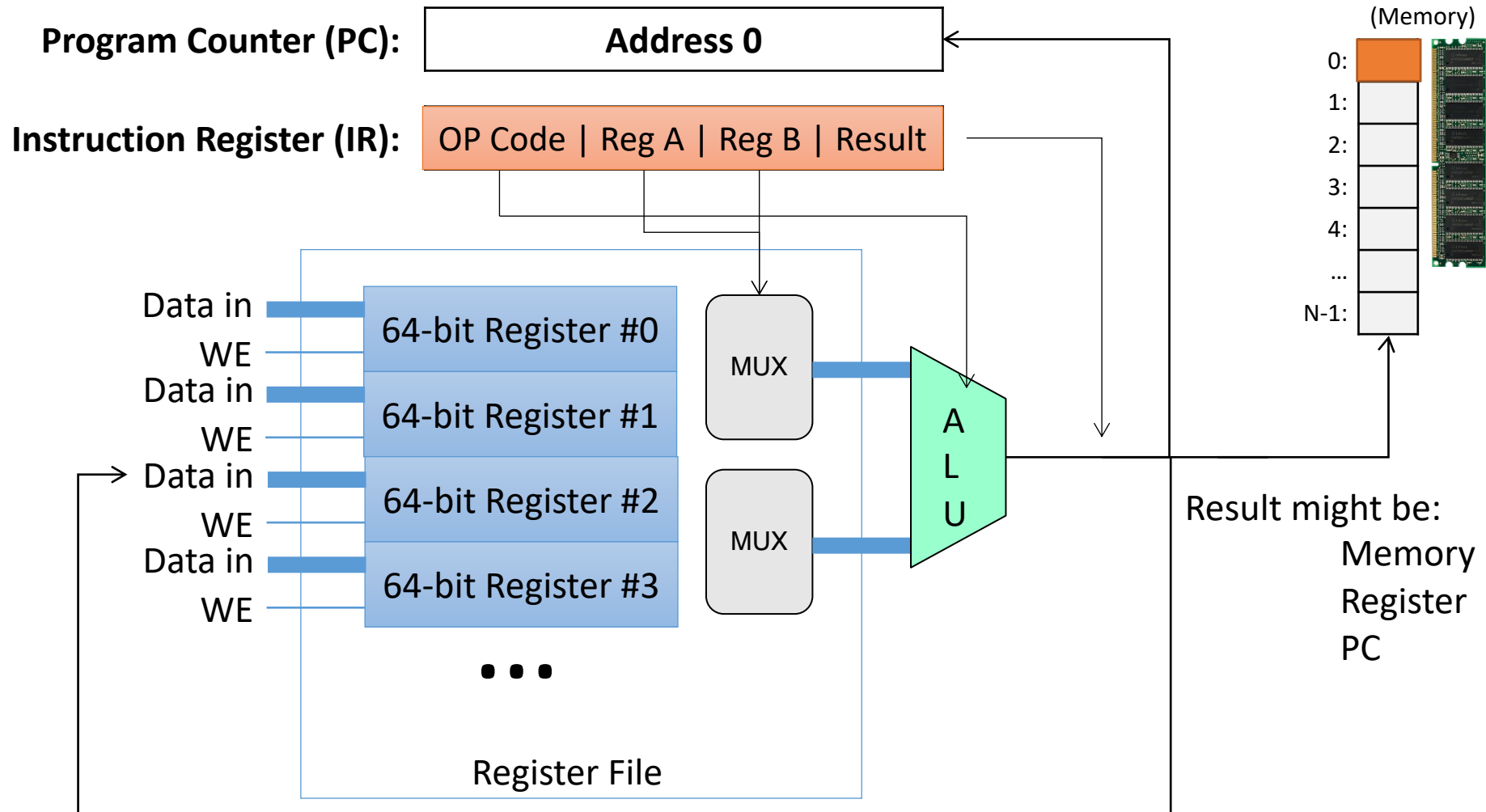
# Storing results.

Interpret the instruction bits: Store result in register, memory, PC.




# Clocking

- Need to periodically transition from one instruction to the next.
- It takes time to fetch from memory, for signal to propagate through wires, etc.
  - Too fast: don't fully compute result
  - Too slow: waste time
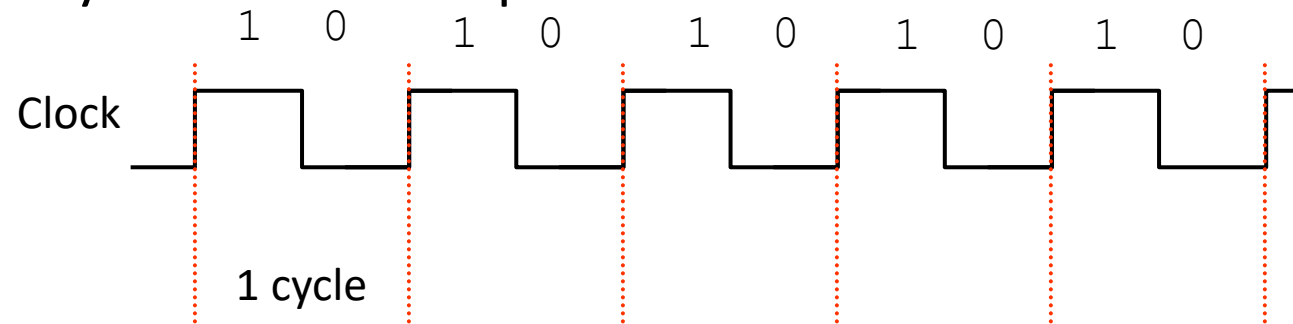
# Clock Driven System


- Everything in a CPU is driven by a discrete clock
  - clock: an oscillator circuit, generates hi low pulse
  - clock cycle: one hi-low pair



- Clock determines how fast system runs
  - Processor can only do one thing per clock cycle
    - Usually just one part of executing an instruction
  - 1GHz processor:  
1 billion cycles/second → 1 cycle every nanosecond
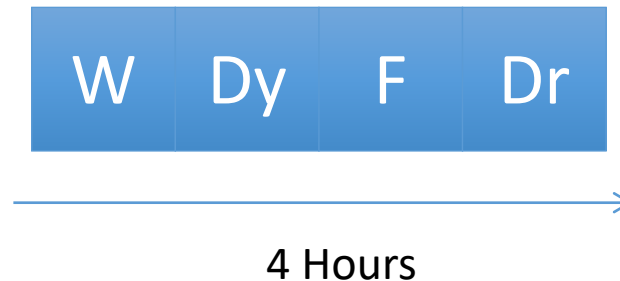
# Cycle Time: Laundry Analogy



- Discrete stages: fetch, decode, execute, store
- Analogy (laundry): washer, dryer, folding, dresser



You have big problems if you have millions of loads of laundry to do....




# Laundry

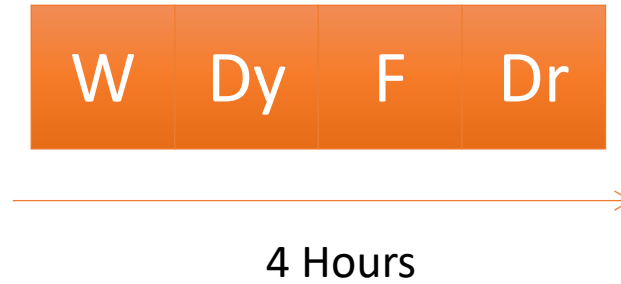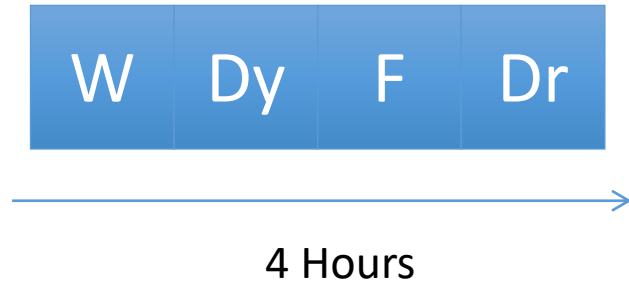


4-hour cycle time.

Finishes a laundry load every cycle.

(6 laundry loads per day)

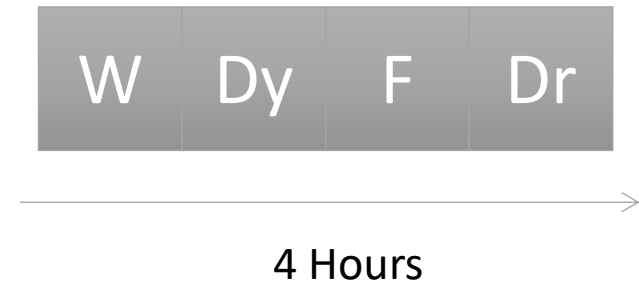


# Pipelining (Laundry)

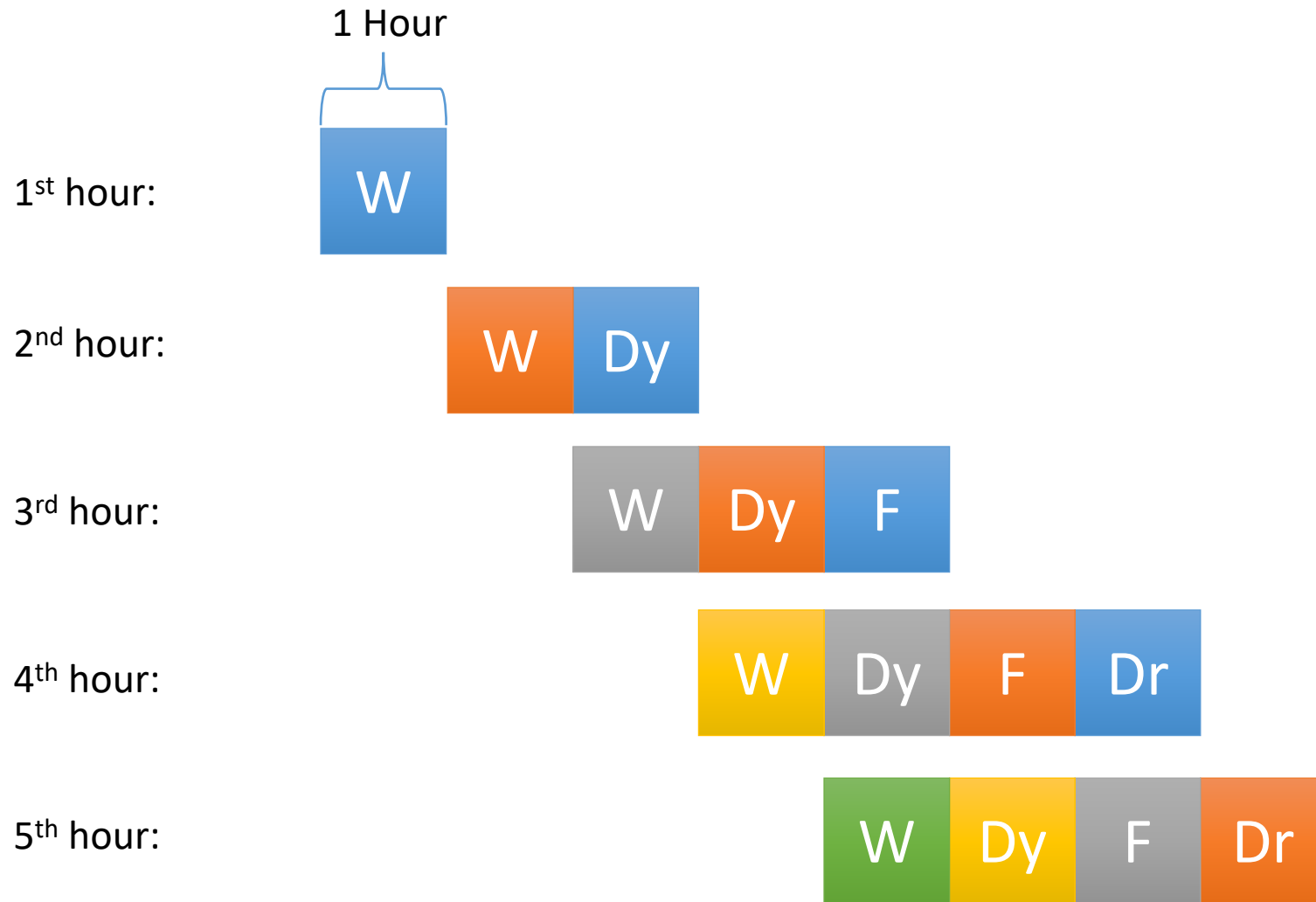

Steady state: One load finishes every hour!  
(Not every four hours like before.)

# Pipelining (CPU)

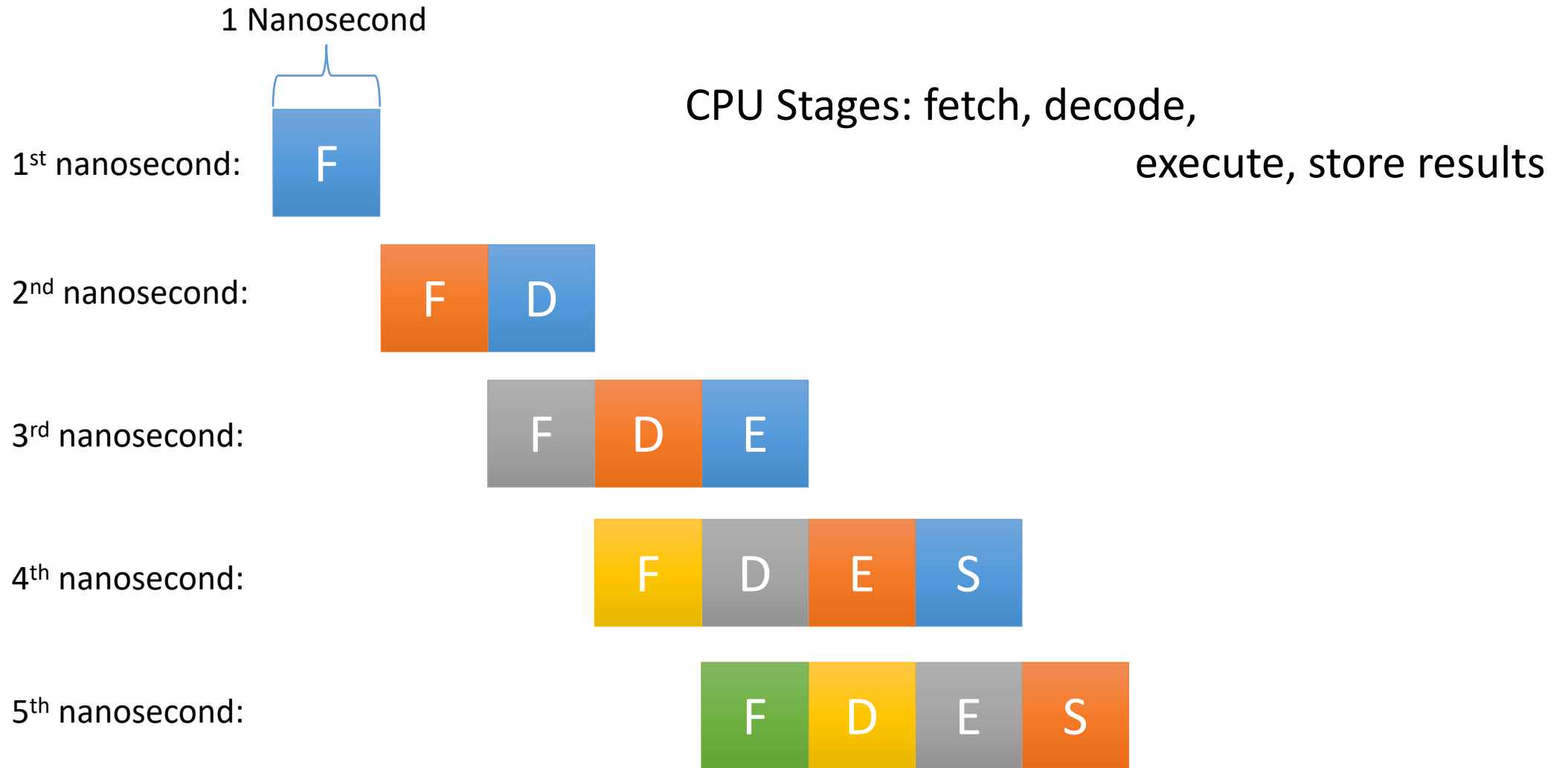

Steady state: One instruction finishes every nanosecond!  
(Clock rate can be faster.)

# Pipelining

(For more details about this and the other things we talked about here, take architecture.)

# Up next

- Talking to the CPU: Assembly language